

AUDIT COURSE ELECTRONIC CIRCUITS 1: SIMULATION BASED STUDY

LAB 12

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 8/9/2020

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of WEEK 6 DAY 2 is 40 MINUTES


Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.

Follow these instruction strictly:


- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of WEEK 6 DAY 2

You are entitled for 1 CREDIT per Lab only if you follow above instruction to the details


STUDENTS WORK AREA STARTS HERE

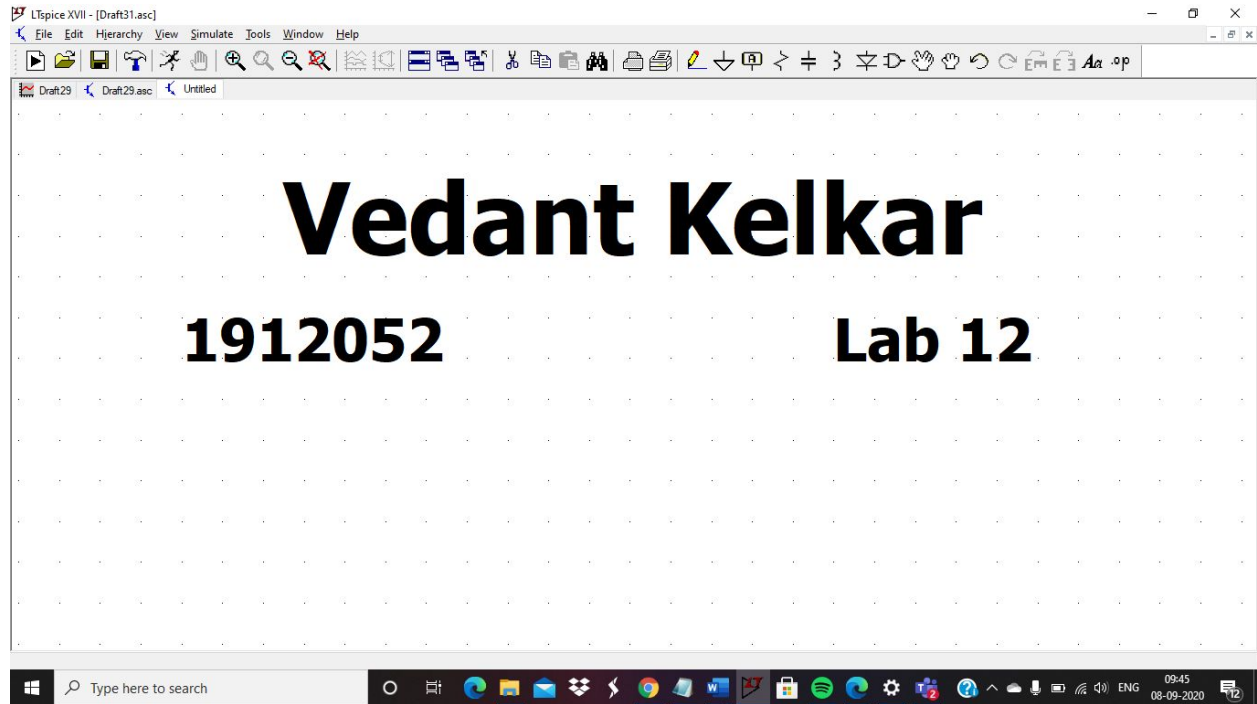

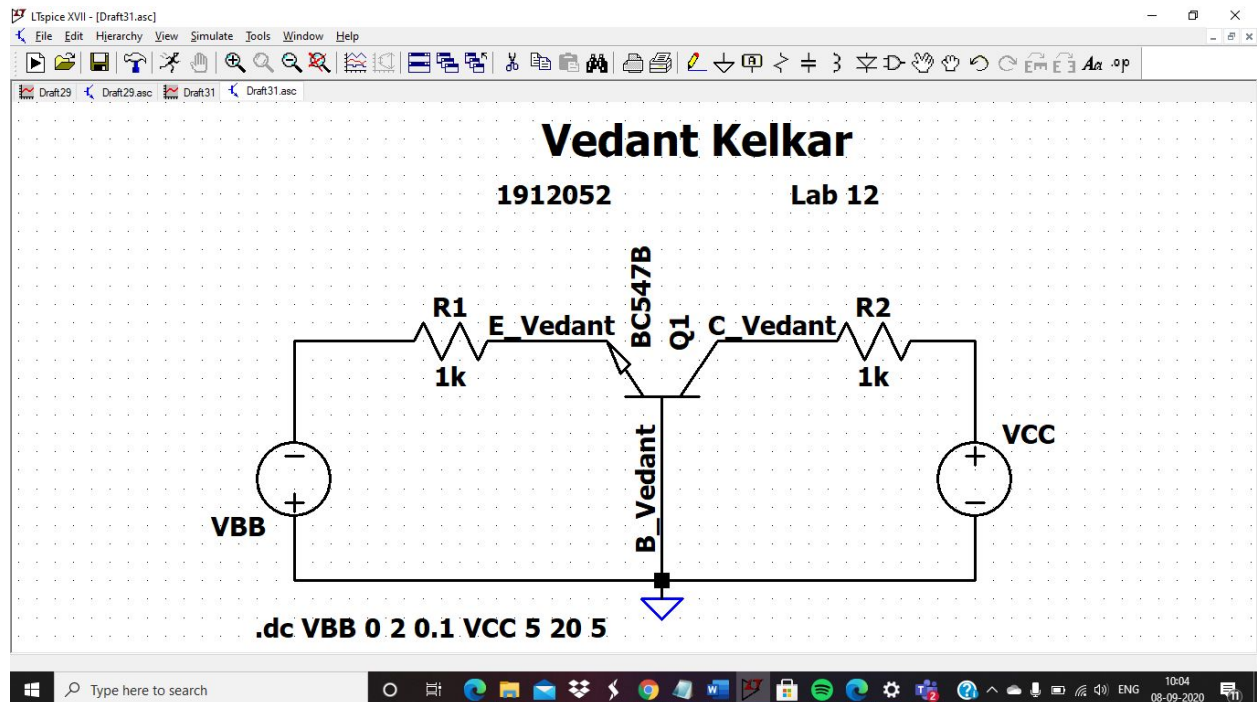
NPN BJT INPUT CHARACTERISTICS common base



VBB vs Ie

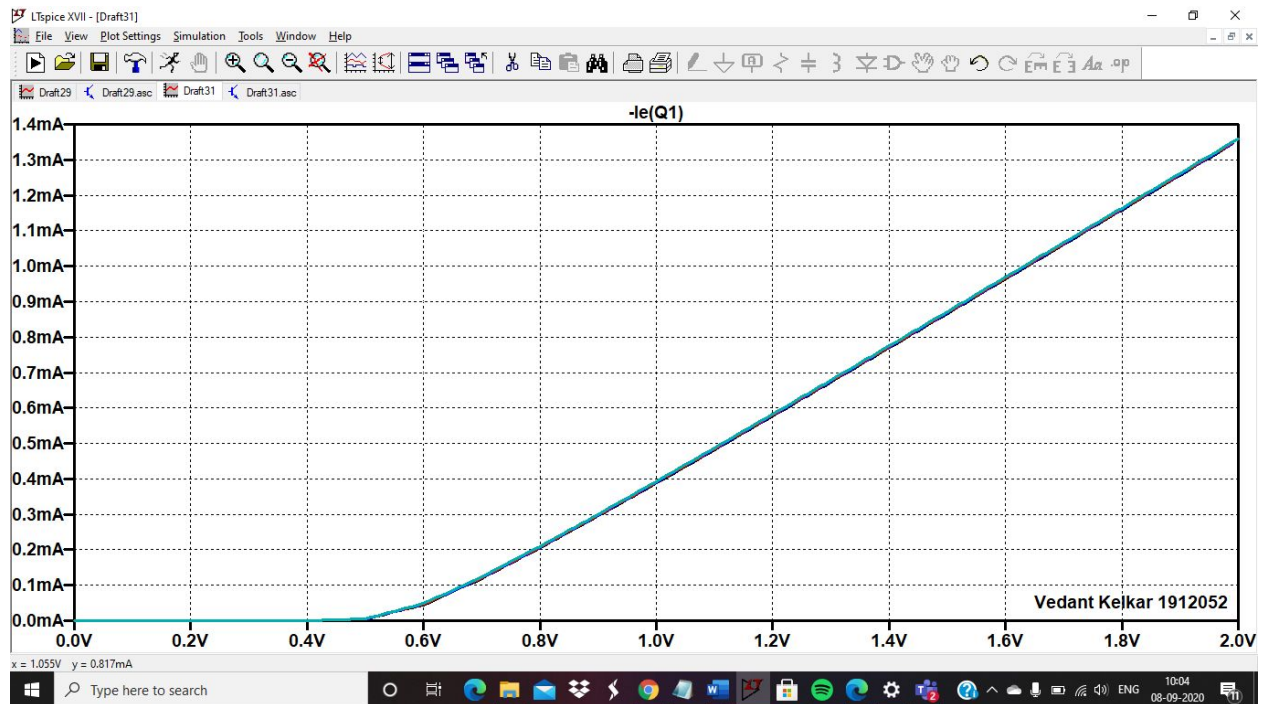

VBE vs Ie

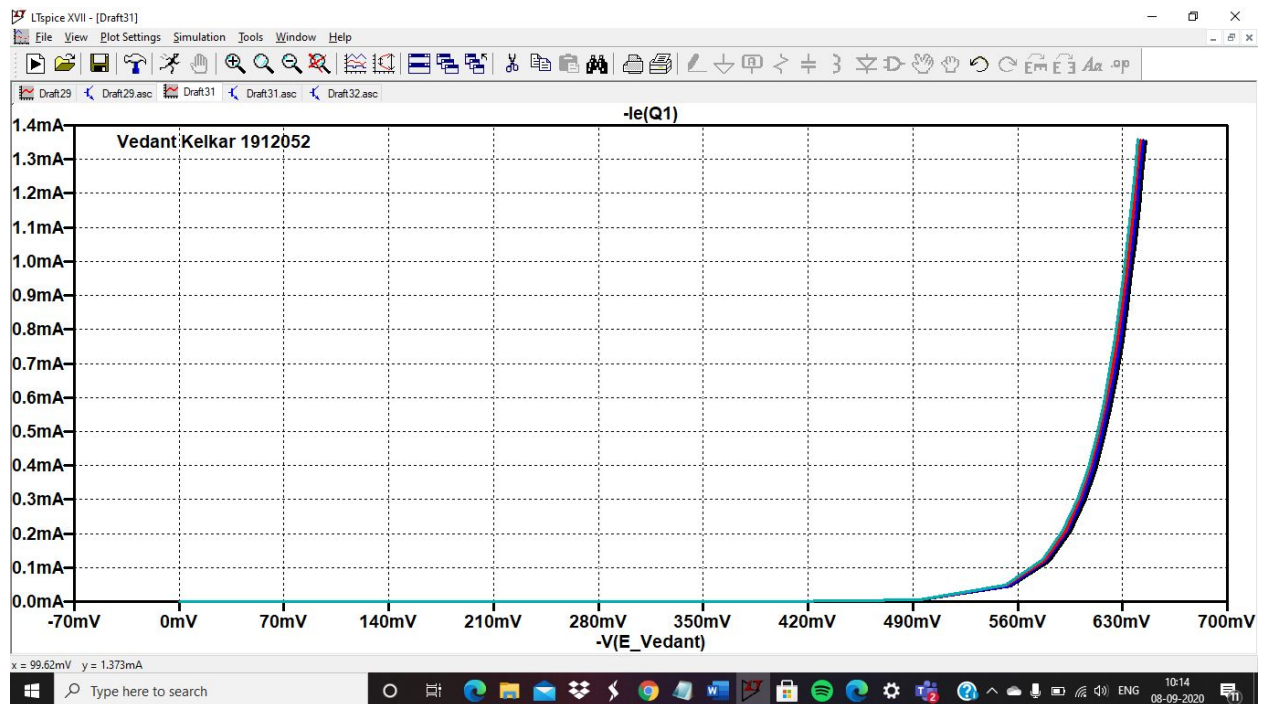


VBE


IE

0	0
200mV	60.106pA
400mV	160.400nA
500mV	7.790uA
550mV	40.595uA
580mV	117.602uA
600mV	252.560uA
620mV	528.620uA

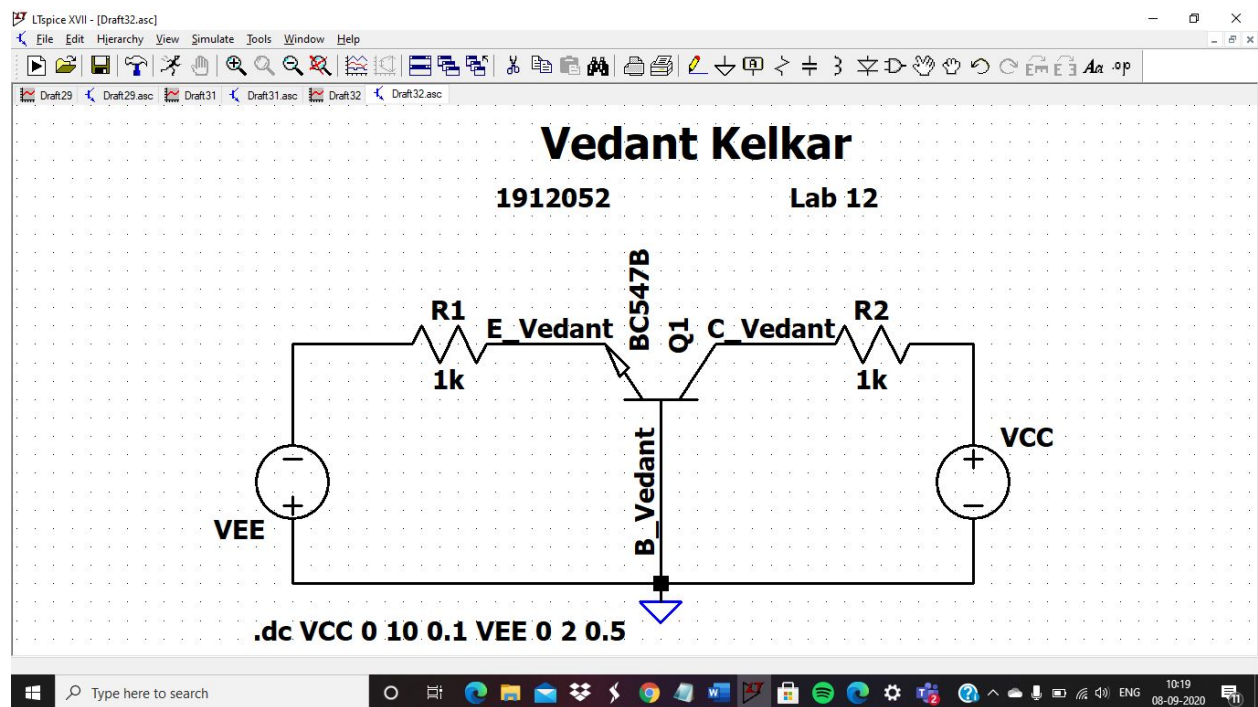BJT NPN OUTPUT CHARACTERISTICS common base




VCB vs Ic

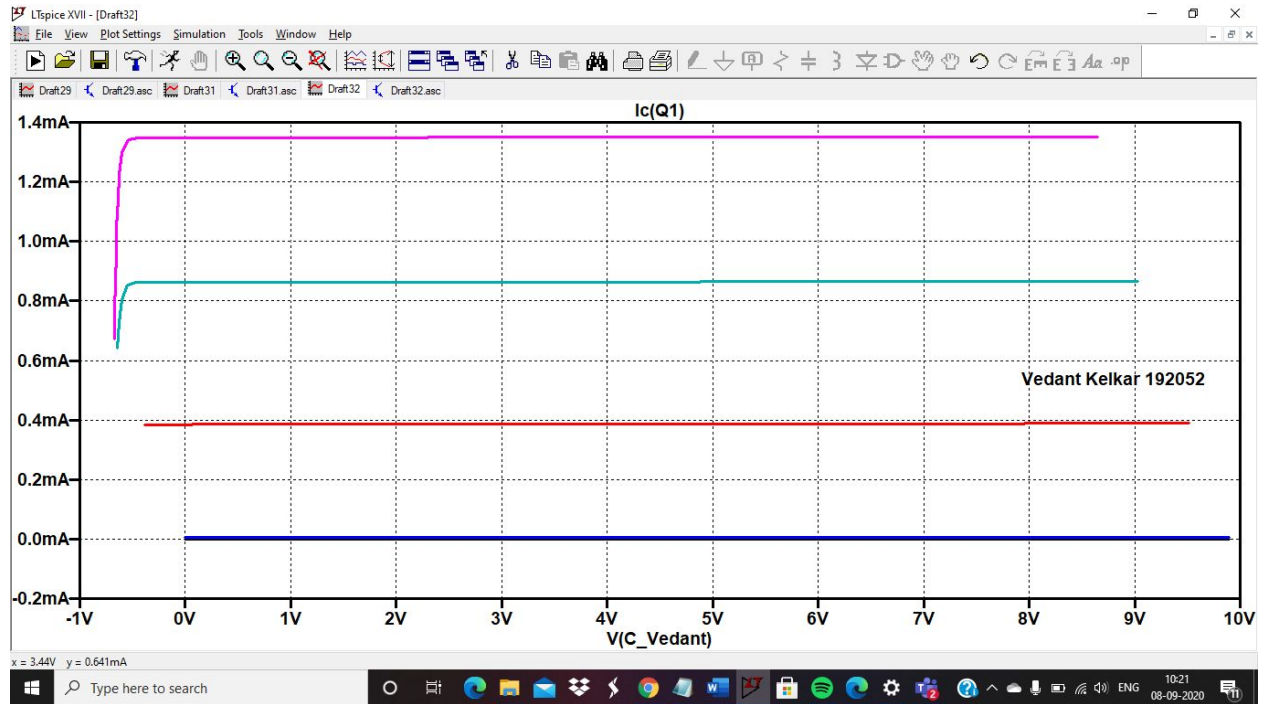

VCB	IC
-500mV	0.856mA
-300mV	0.867mA
-100mV	0.865mA
0V	0.862mA
1V	0.862mA
3V	0.862mA
5V	0.862mA
8V	0.862mA

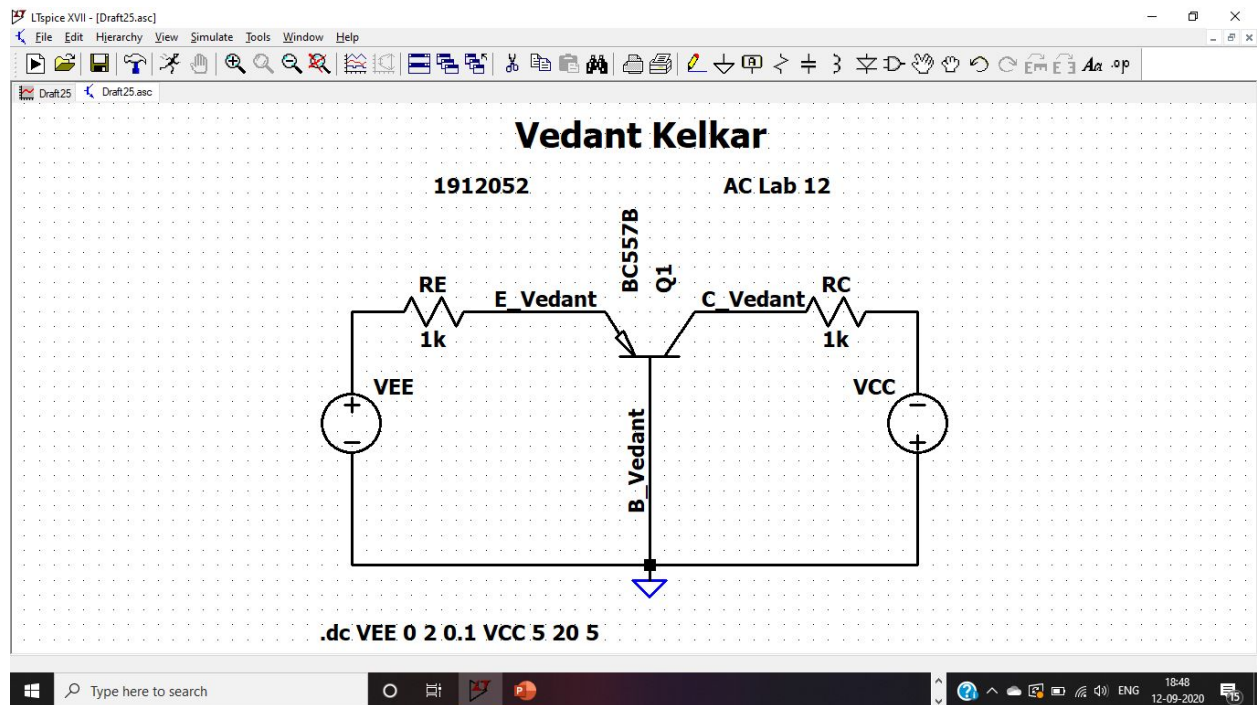
BJT PNP INPUT CHARACTERISTICS common base



VEE vs I_e




VBE vs Ie

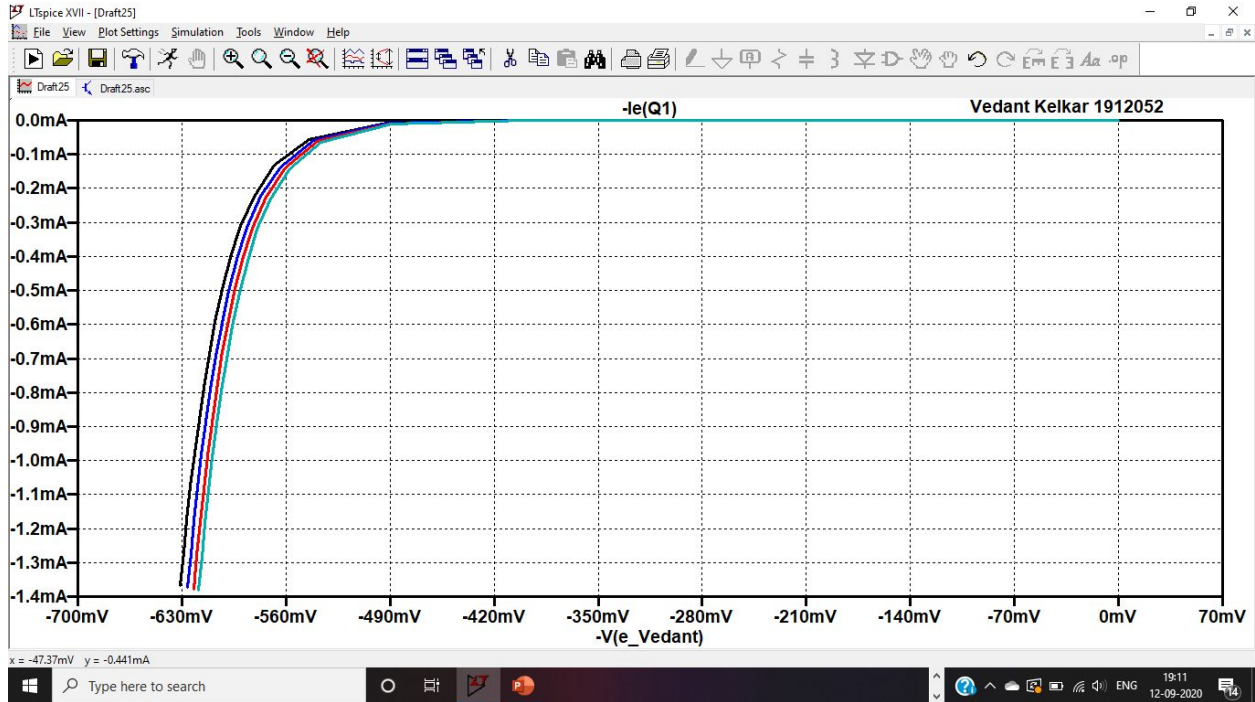


Vbe	Ie
0	0
-200mV	-121.47551pA
-400mV	-240.53726nA
-500mV	-15.177303μA
-550mV	-77.307713μA
-580mV	-217.68856μA
-600mV	-455.58432μA
-620mV	-953.58151μA

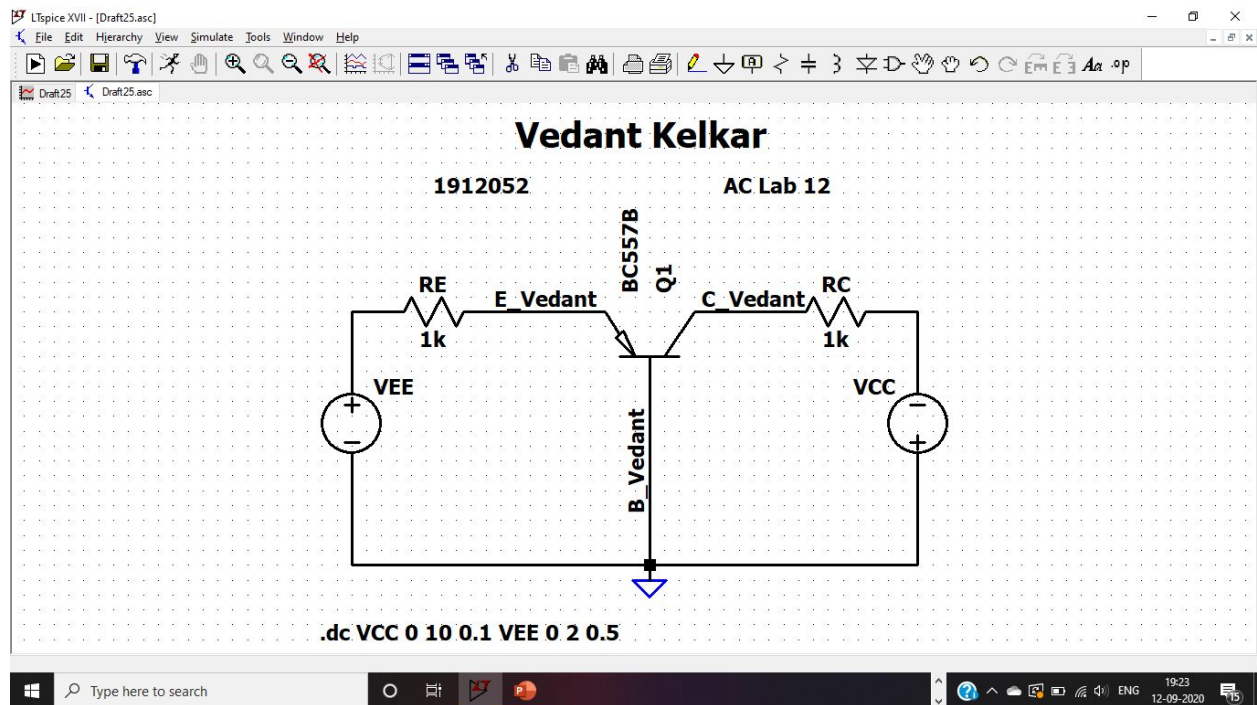
BJT PNP OUTPUT CHARACTERISTICS common base



Ic vs VCC

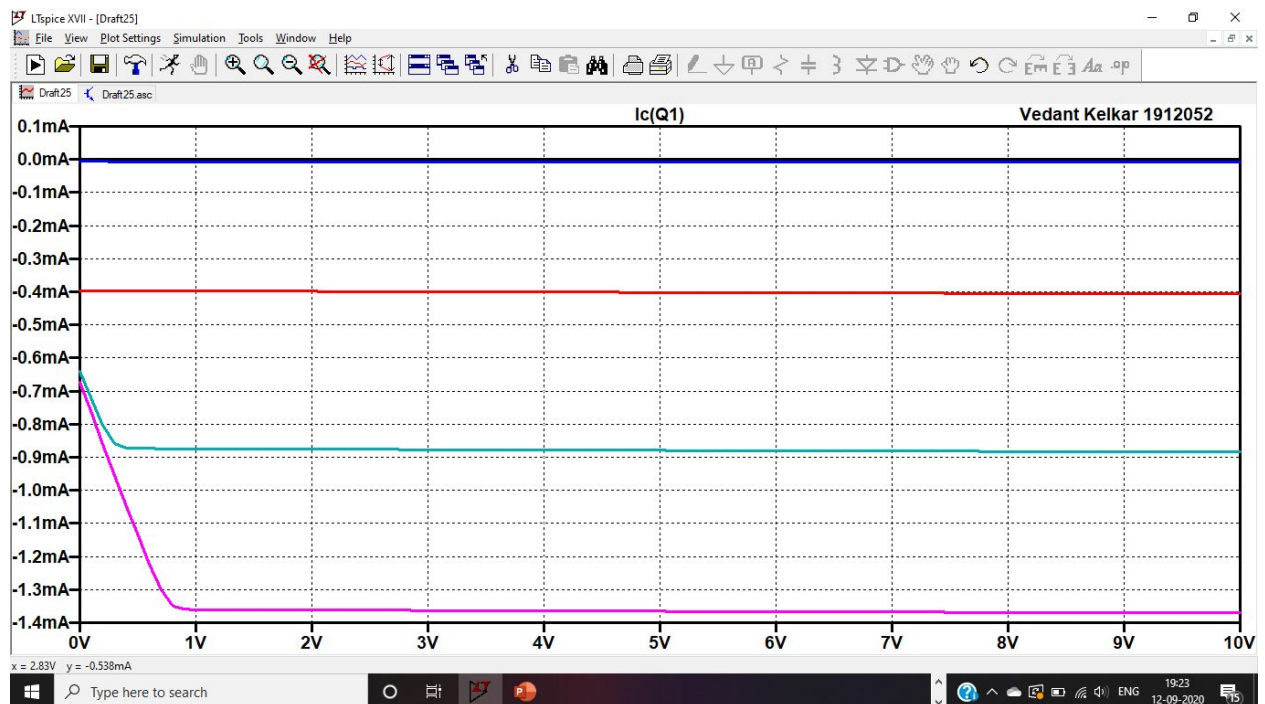

Ic vs VCB

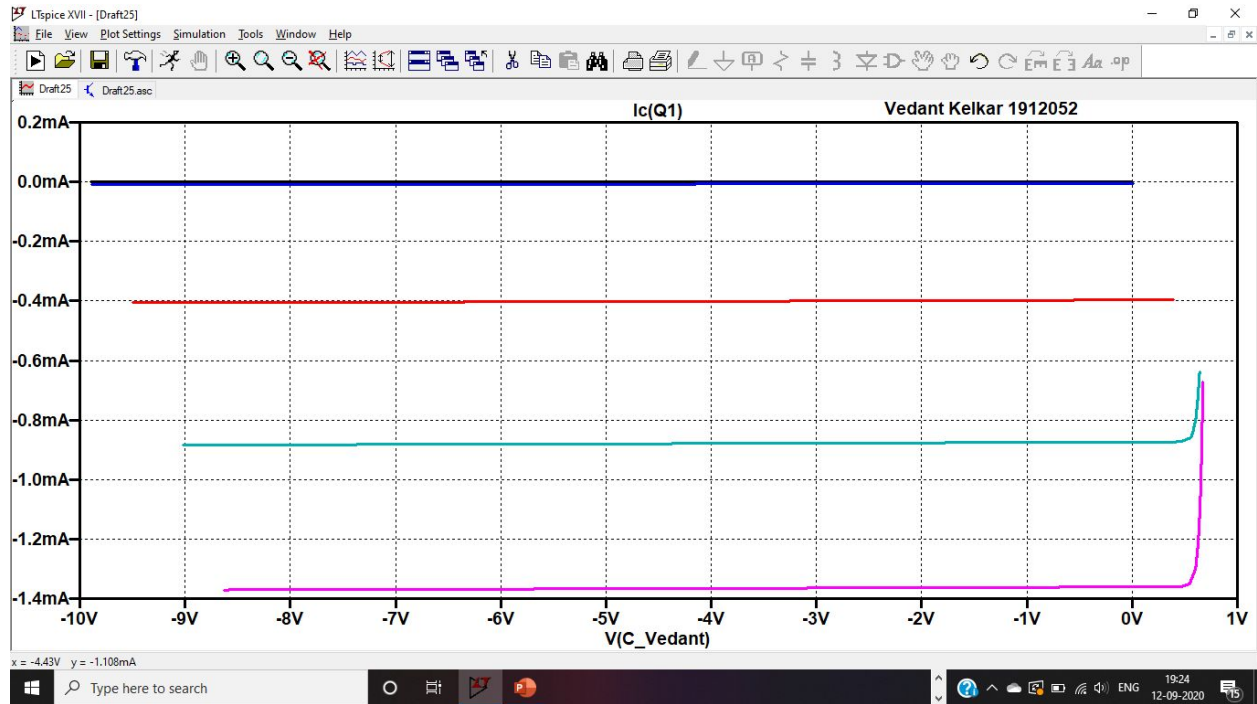

Vcb	Ic
500mV	-0.399mA
300mV	-0.399mA
100mV	-0.399mA
0V	-0.399mA
-1V	-0.399mA
-3V	-0.399mA
-5V	-0.402mA
-8V	-0.411mA

I HAVE MADE THE SUGGESTED CHANGES

**Suggestions: Mention which characteristics and which configurations for above
printscreens:**

AC LAB 12 is approved with suggestions: Inderjit Singh Dhanjal