

## **Audit Course Session 13**

### **AUDIT COURSE ELECTRONIC CIRCUITS 2: SIMULATION BASED STUDY**

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

**Date: 2/3/2021**

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

**Time slot allotted to you all for the completion of Session 13 is 40 MINUTES**



**Kindly upload your work (only circuit schematic & waveform in LTspice) in the shared google doc between this time slot only.**

**Follow these instruction strictly:**



- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen ( time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of Session 13

**You are entitled for 10 points per session only if you follow above instruction to the details**

**STUDENTS WORK AREA STARTS HERE**

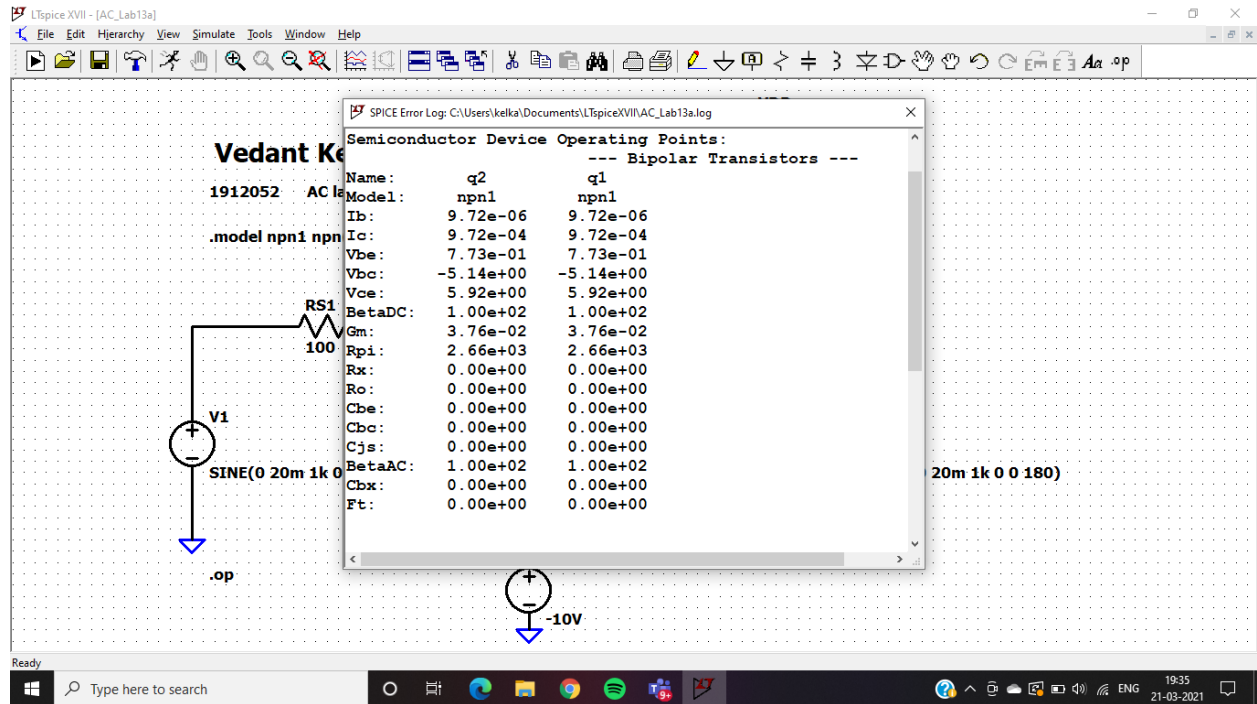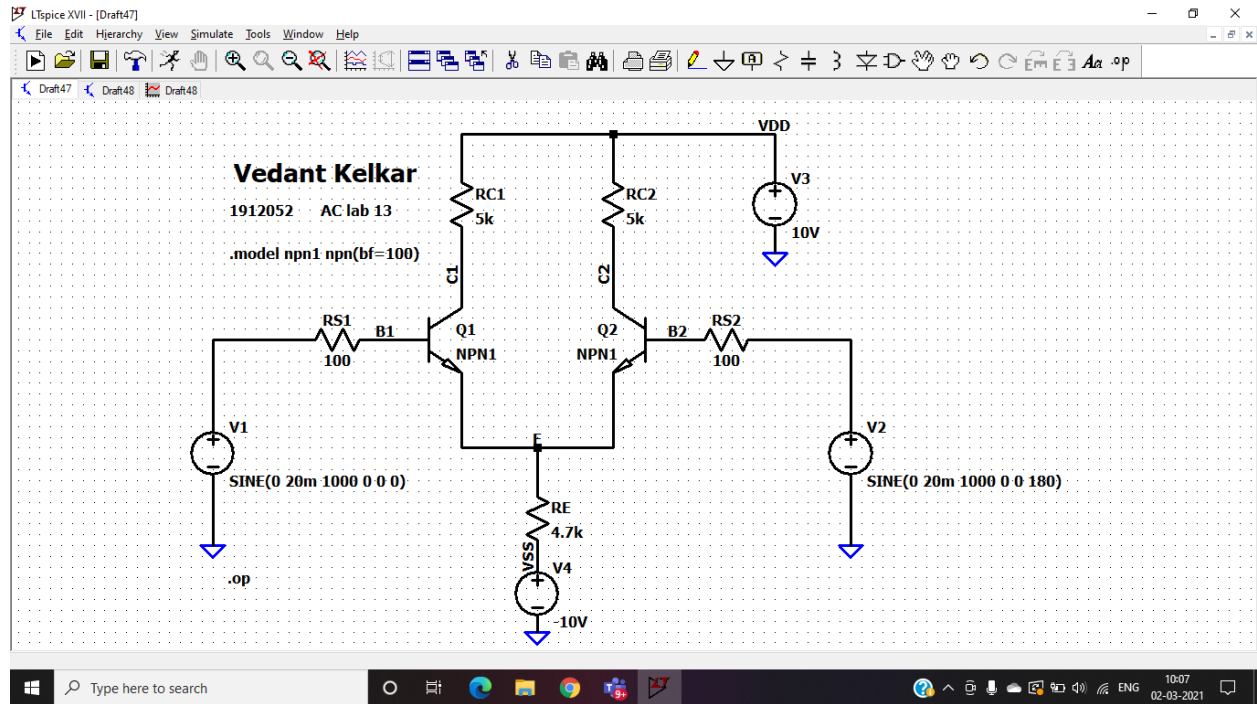

AC

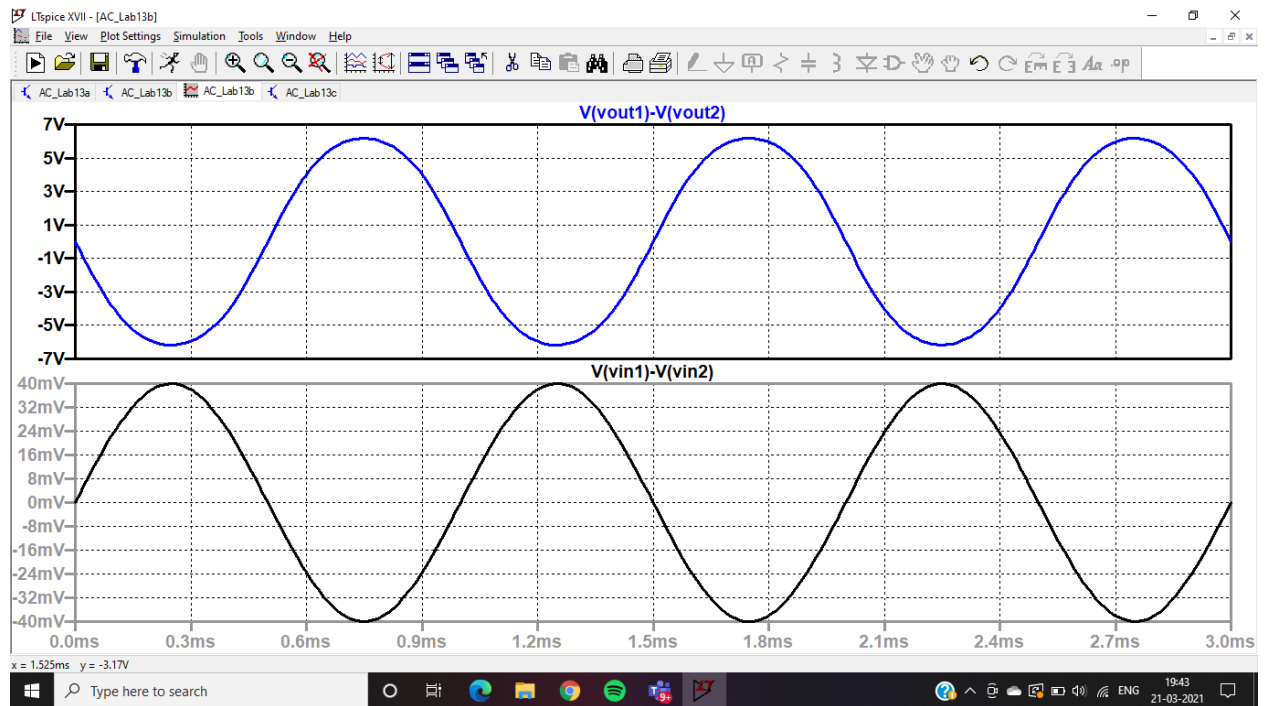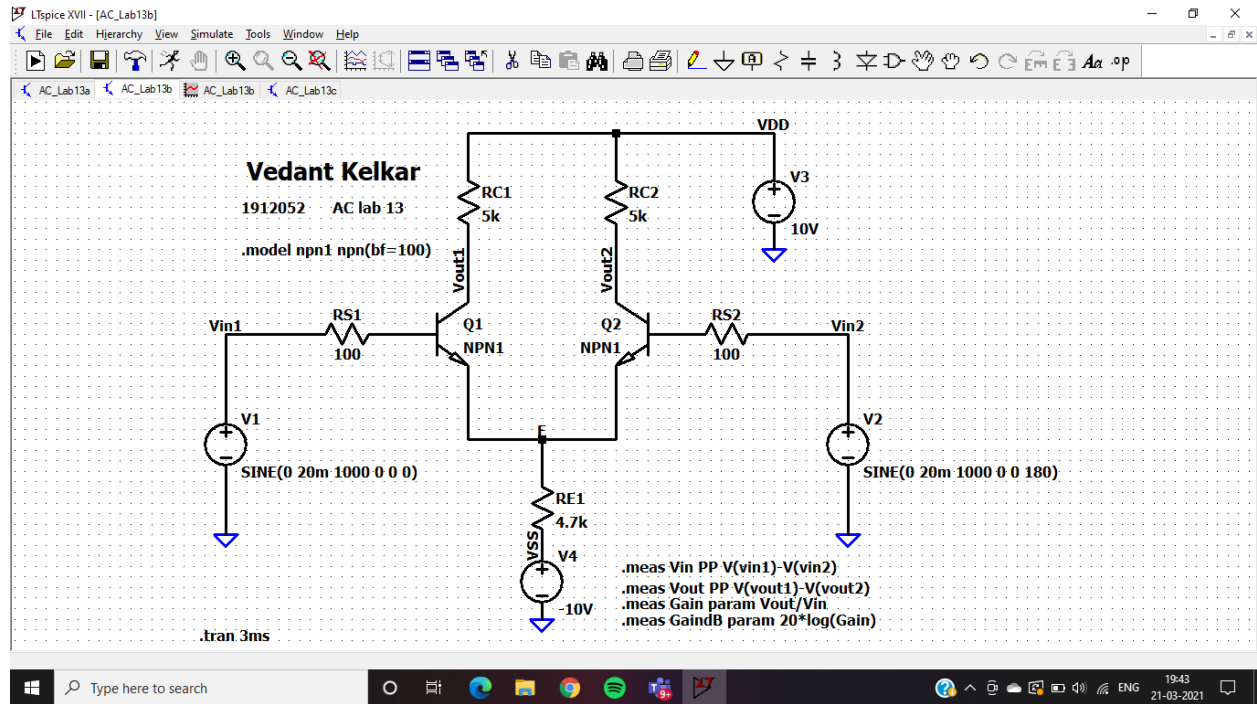

LTspice XVII - [AC\_Lab13b]

File Edit Hierarchy View Simulate Tools Window Help

AC\_Lab13a AC\_Lab13b AC\_Lab13c

**Vedant**

1912052 A

.model npn1

Vin1

V1

SINE(0 20m 1

10m 1000 0 0 180)

.tran 3ms

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC\_Lab13b.log

Circuit: \* C:\Users\kelka\Documents\LTspiceXVII\AC\_

Direct Newton iteration for .op point succeeded.

vin: PP(v(vin1)-v(vin2))=0.079943 FROM 0 TO 0.003

vout: PP(v(vout1)-v(vout2))=12.3561 FROM 0 TO 0.003

gain: vout/vin=154.561

gaindb: 20\*log10(gain)=43.782

Date: Sun Mar 21 19:46:04 2021

Total elapsed time: 0.181 seconds.

tnom = 27

temp = 27

method = modified trap

totiter = 2089

traniter = 2082

tranpoints = 1042

accept = 1042

.meas Vout PP V(vout1)-V(vout2)

.meas Gain param Vout/Vin

.meas GaindB param 20\*log10(Gain)

Ready

Type here to search

19:46 21-03-2021

## For DIUO

LTspice XVII - [AC\_Lab13b]

File Edit Hierarchy View Simulate Tools Window Help

AC\_Lab13a AC\_Lab13b AC\_Lab13c

**Vedant Kelkar**

1912052 AC lab 13

.model npn1 npn(bf=100 is=1e-14)

Vin1

V1

SINE(0 20m 1000 0 0 0)

RC1 5k

RC2 5k

V3 10V

Vout1

Vout2

Q1 NPN1

Q2 NPN1

RS1 100

RS2 100

Vin2

V2

SINE(0 20m 1000 0 0 180)

RE1 4.7k

V4 -10V

.tran 3ms

.meas Vin PP V(vin1)-V(vin2)

.meas Vout PP V(vout2)-5.078835V



.meas Gain param Vout/Vin

.meas GaindB param 20\*log10(Gain)



Ready

Type here to search

19:52 21-03-2021

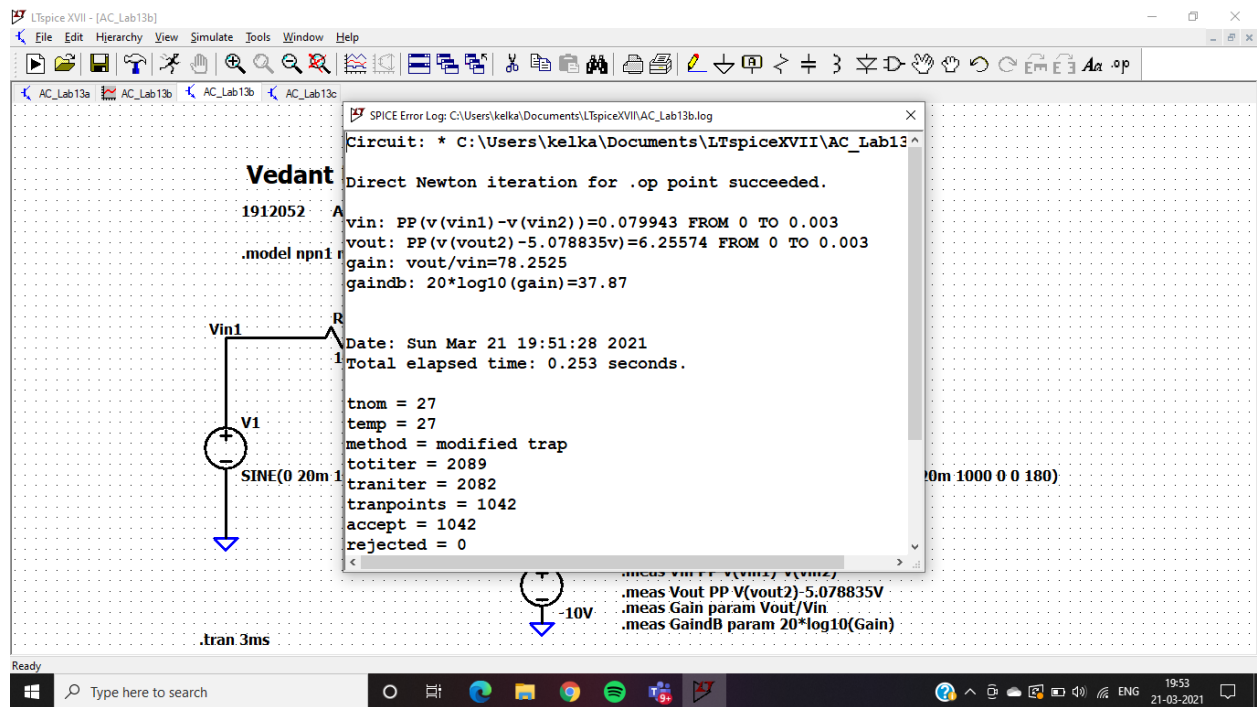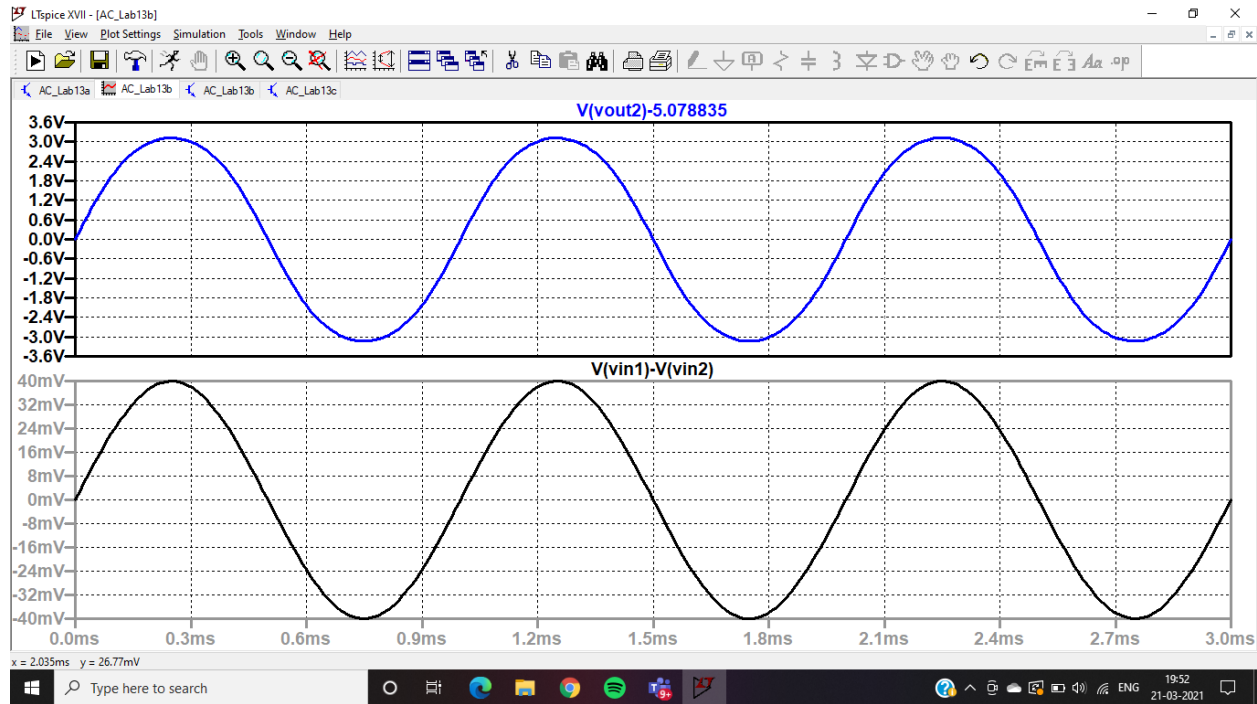

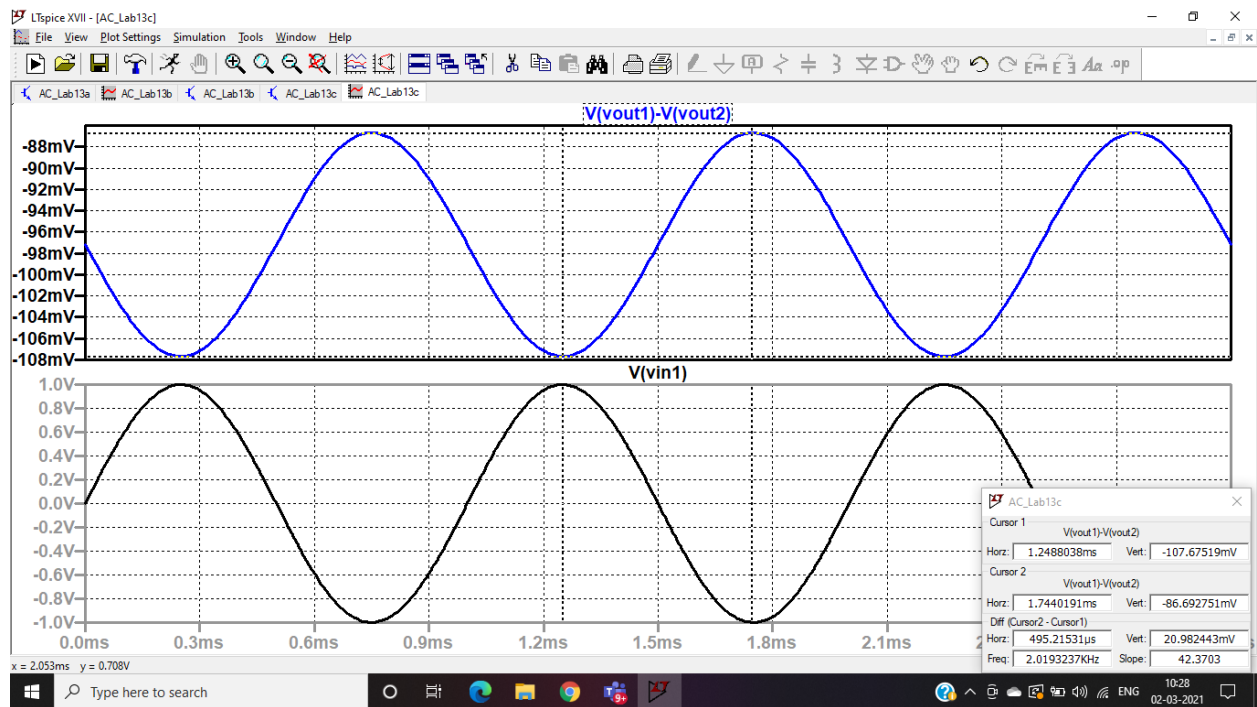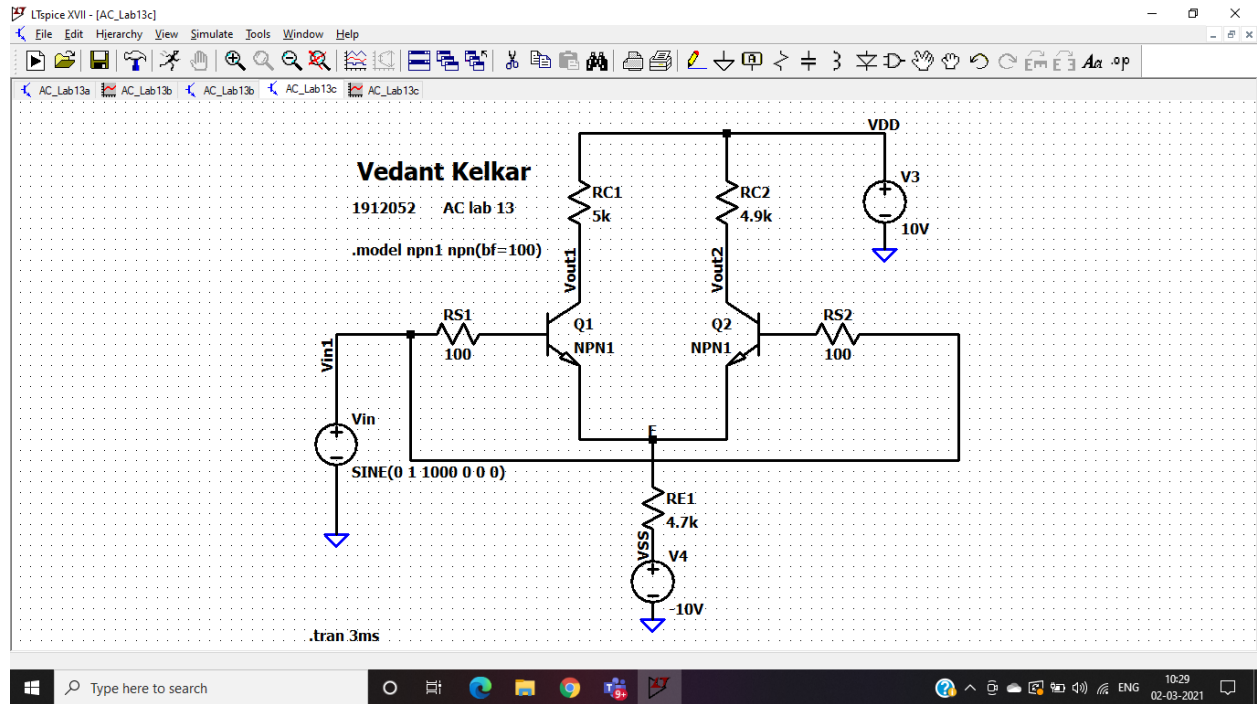o/p-6.1732197V  
ip=80mv  
AD=77.125 DIBO



$o/p = 194.367\text{mV}$   
 $i/p = 2\text{V}$   
 $A_{cm} = 0.0972 \text{ DIBO}$

**AC LAB 13 is approved: Inderjit Singh Dhanjal**