

Audit Course Session 12

AUDIT COURSE ELECTRONIC CIRCUITS 2: SIMULATION BASED STUDY

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 1/3/2021

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of Session 12 is 40 MINUTES



Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.

Follow these instruction strictly:



- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of Session 12

You are entitled for 10 points per session only if you follow above instruction to the details

STUDENTS WORK AREA STARTS HERE

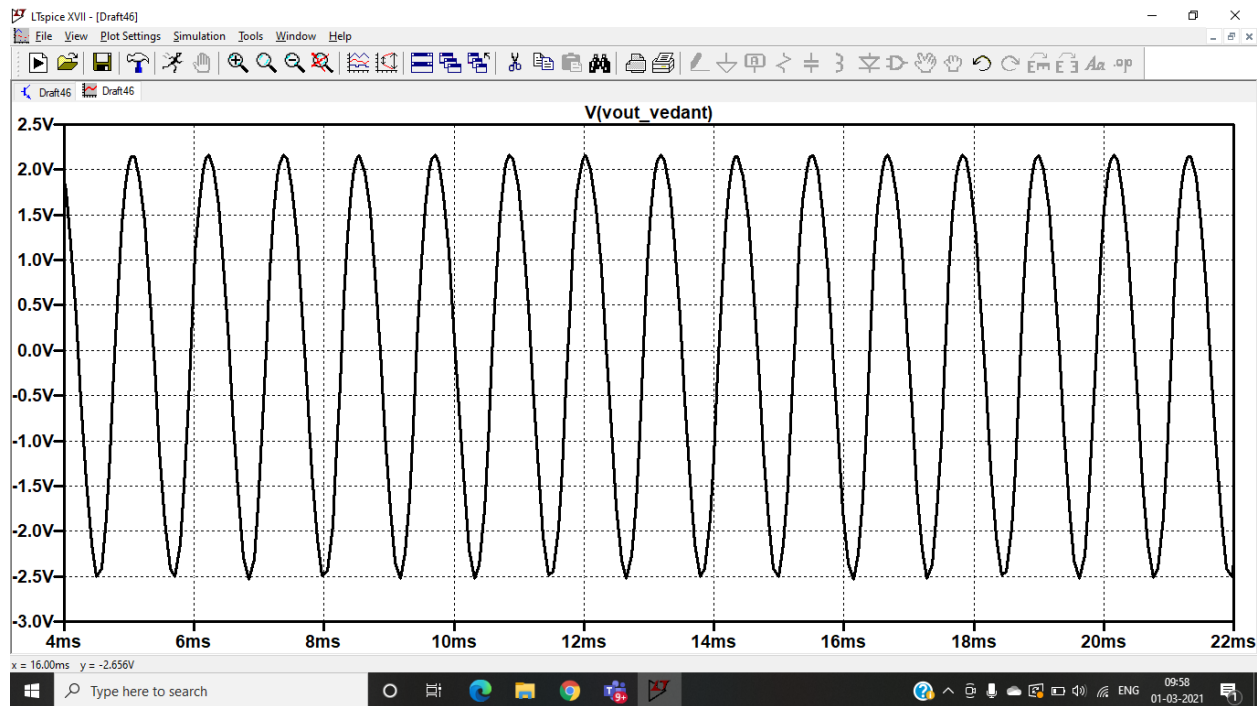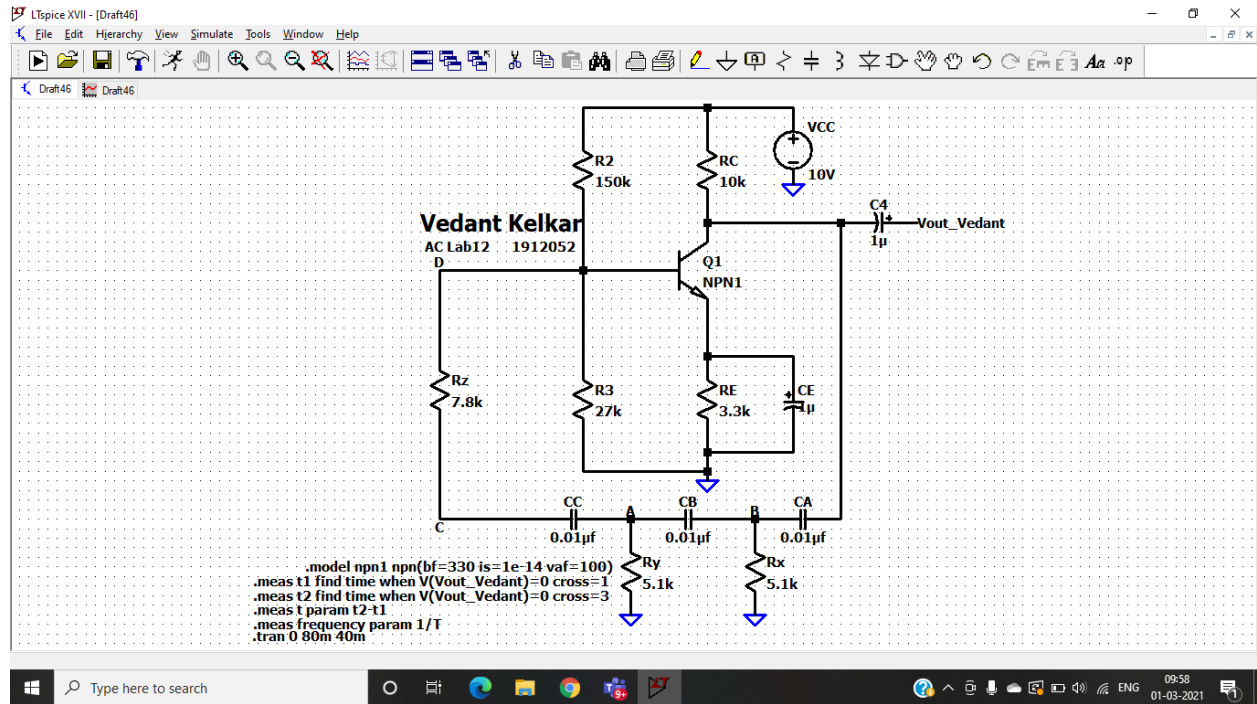


100m

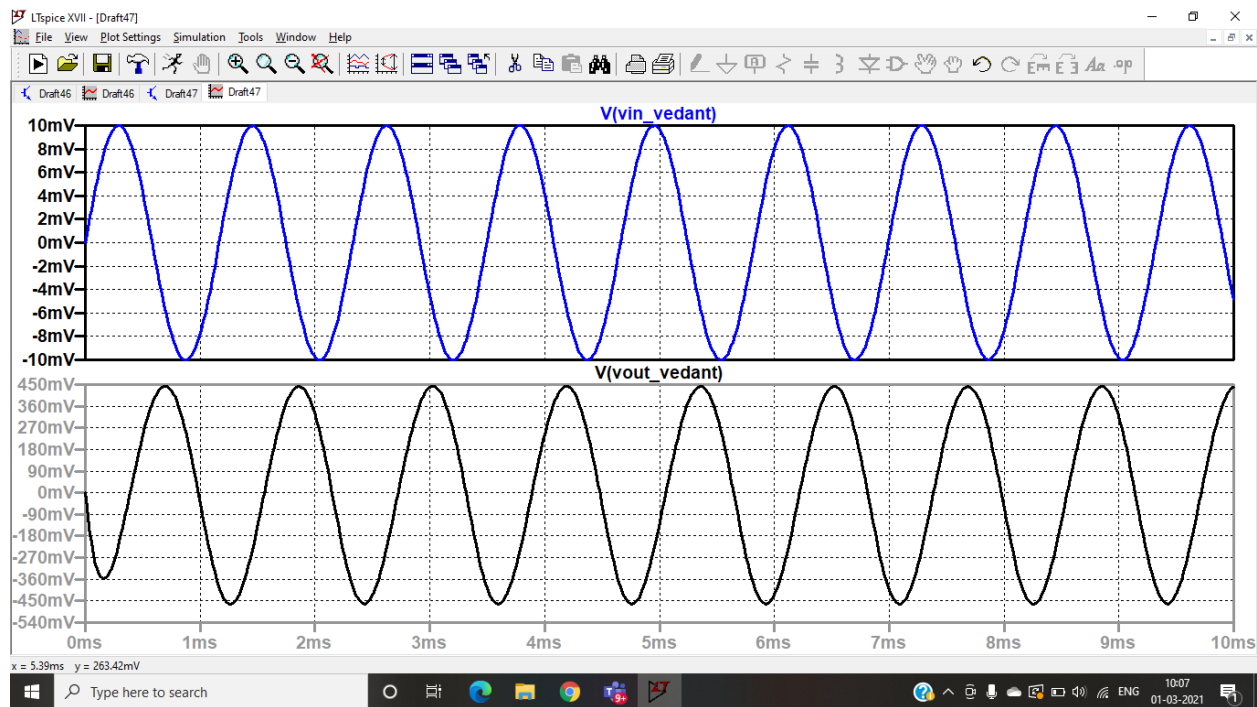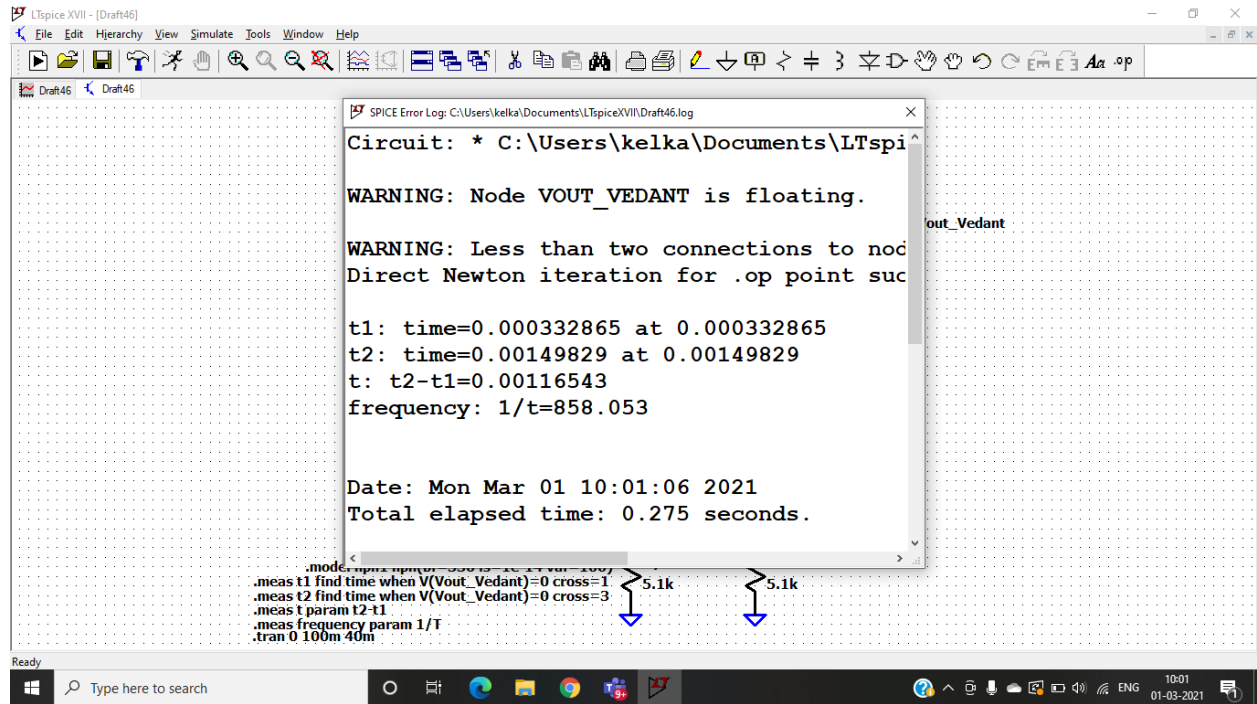


Parameters	Calculated	Simulated
------------	------------	-----------

fo	838.748 Hz	858.053Hz
A.K	Less than 1 (at the start)	$44.4867 * 0.0675263 = 3$



Amplifier Gain

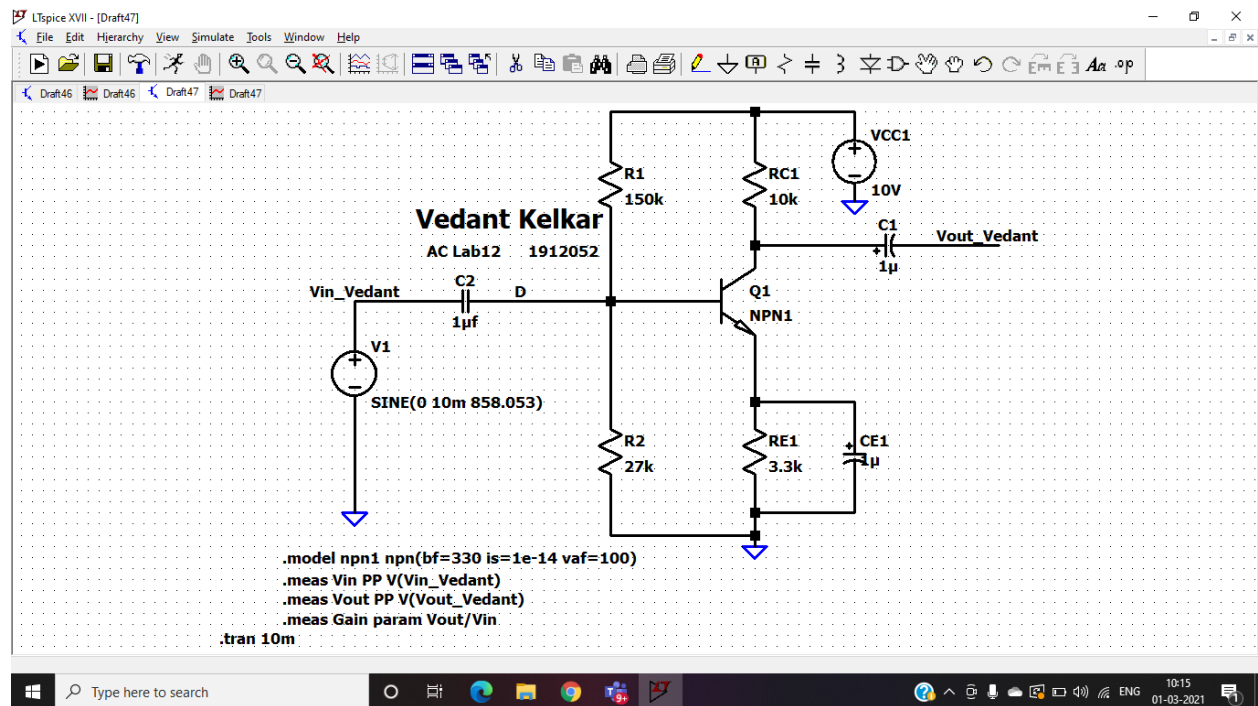


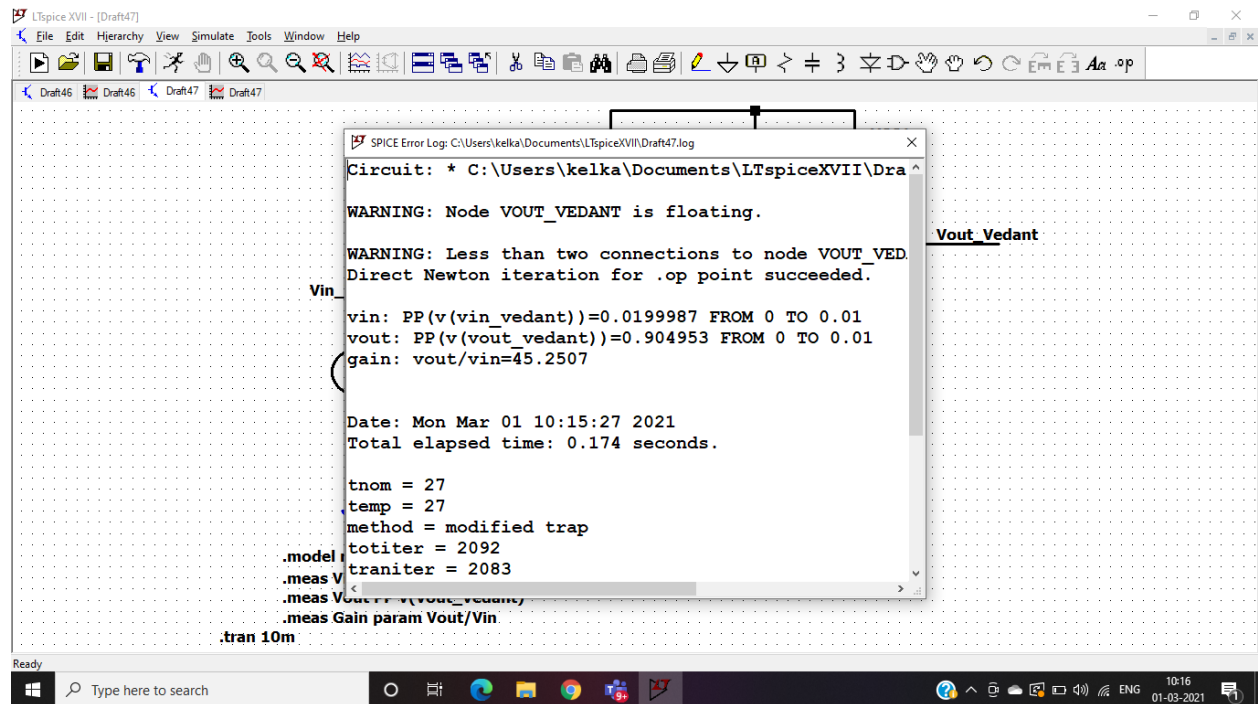

Parameter	Simulated
A (amplifier gain)	45.2507



Feedback

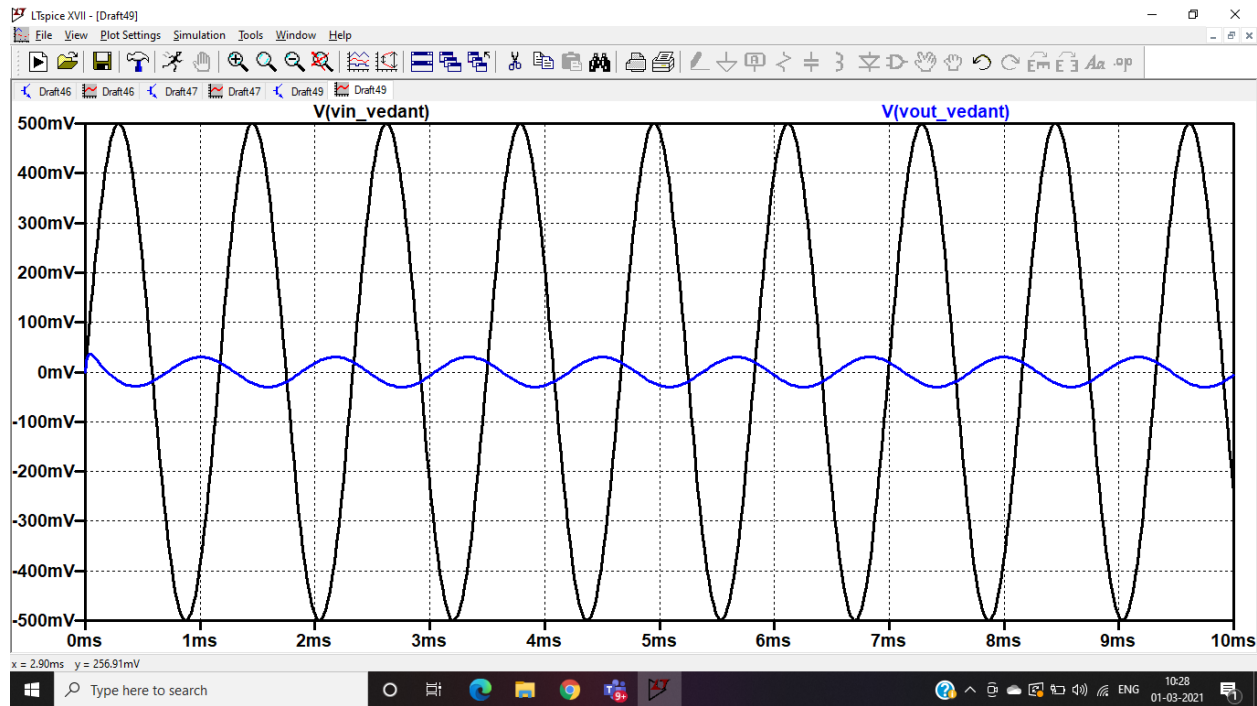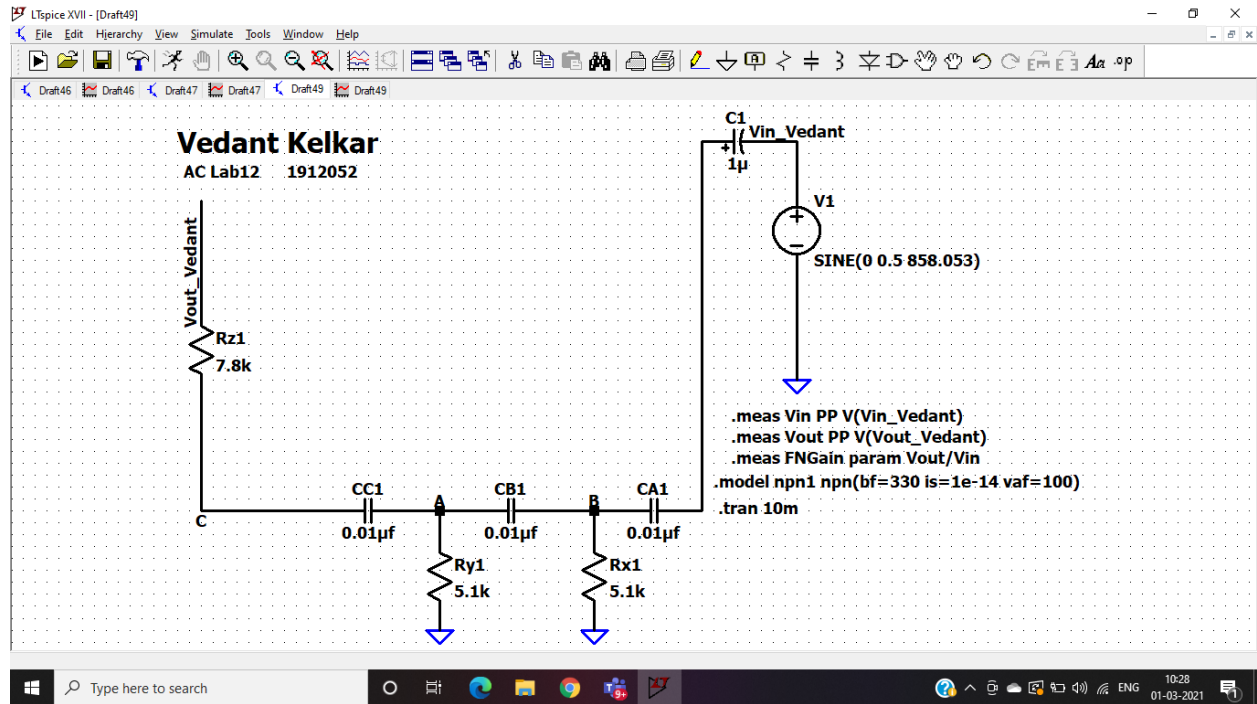

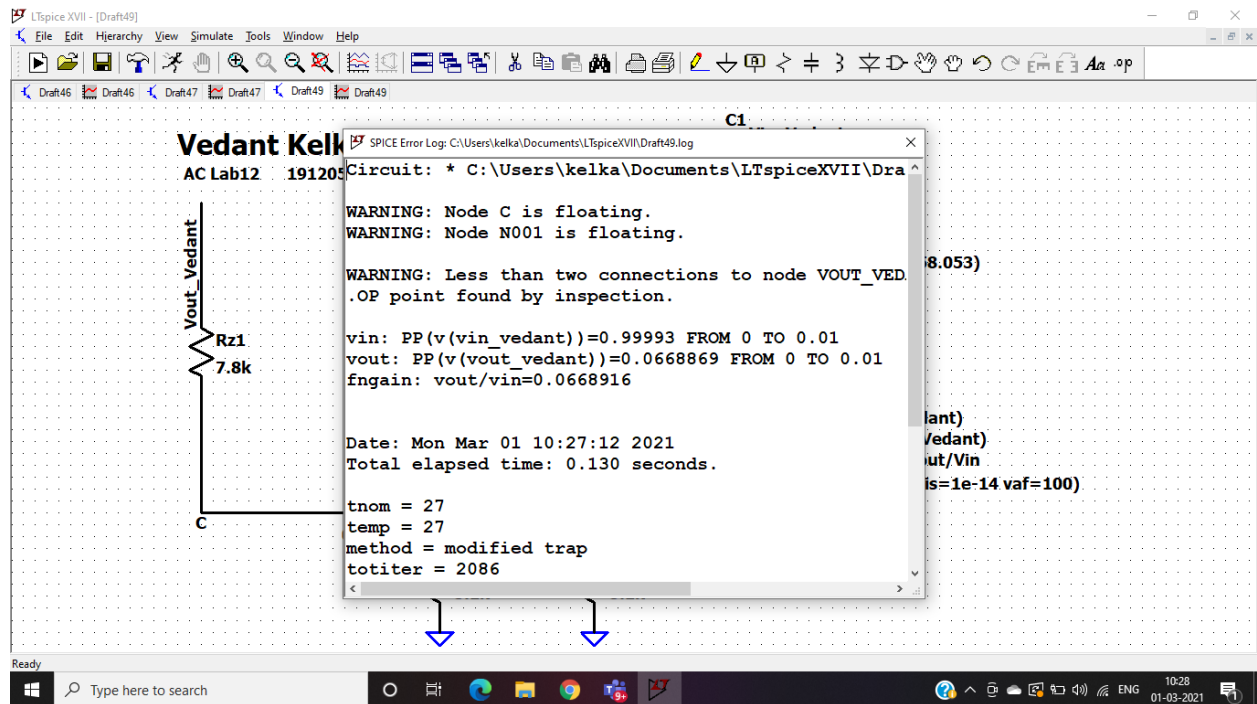

Parameter	Simulated
K (feedback factor)	0.0668916

12 B)
Colpitts Oscillator

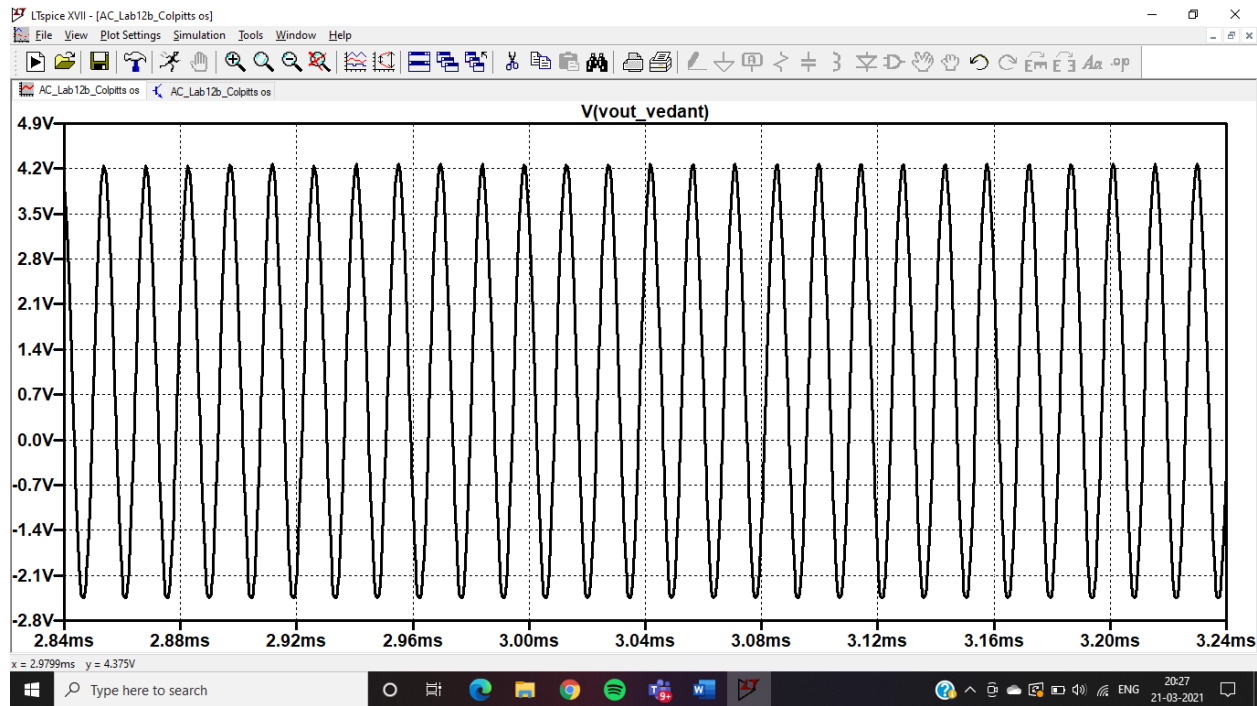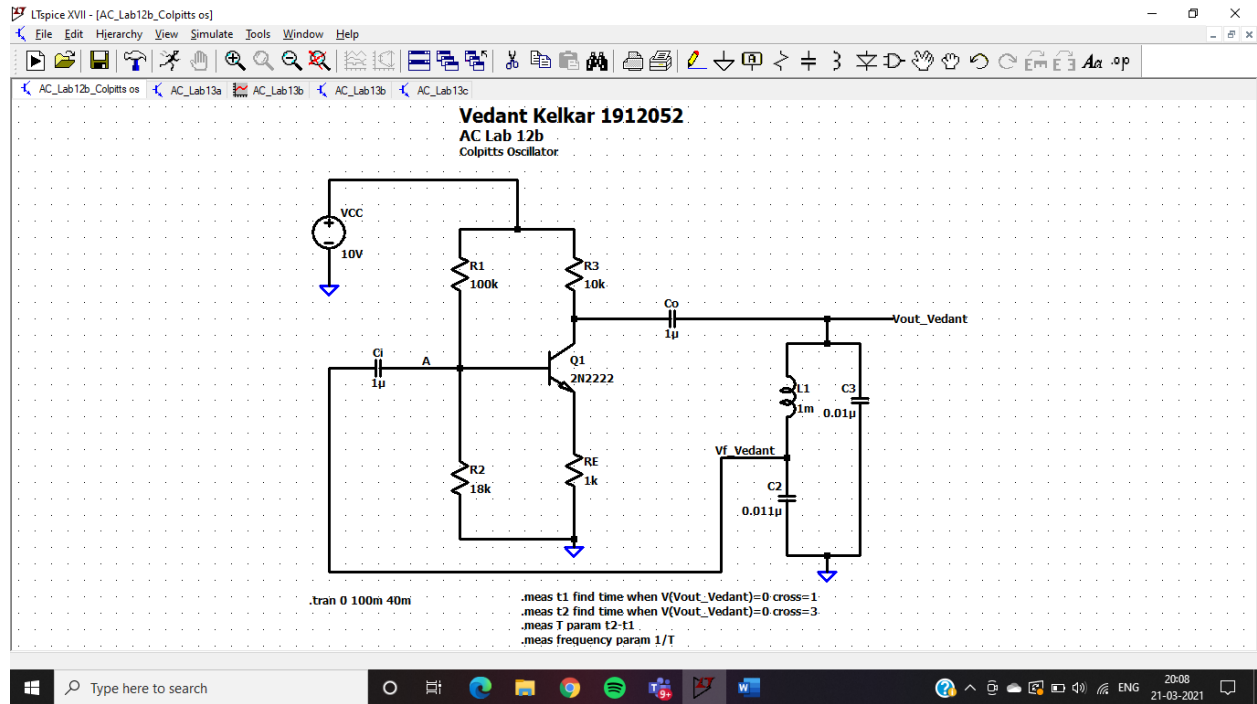

Direct Newton iteration for .op point succeeded

t1: time=6.96968e-006 at 6.96968e-006

t2: time=2.14429e-005 at 2.14429e-005

t: t2-t1=1.44733e-005

frequency: 1/t=69092.9

Parameter	Calculated	Simulated
fo	69.54 KHz	69.0929 KHz

AC LAB 12 is approved: Inderjit Singh Dhanjal