

AUDIT COURSE ELECTRONIC CIRCUITS 1: SIMULATION BASED STUDY

LAB 10

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 1/9/2020

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of WEEK 5 DAY 2 is 40 MINUTES


Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.

Follow these instruction strictly:


- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of WEEK 5 DAY 2



You are entitled for 1 CREDIT per Lab only if you follow above instruction to the details

STUDENTS WORK AREA STARTS HERE.

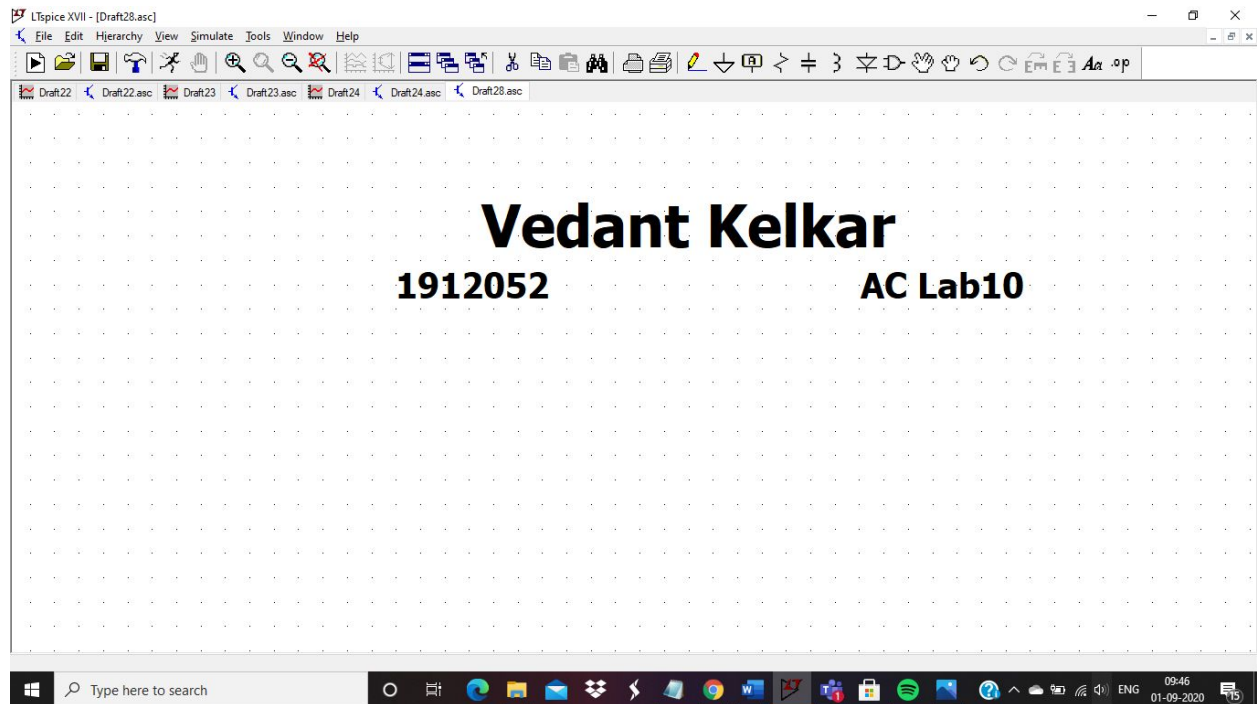

OUTPUT CHARACTERISTICS

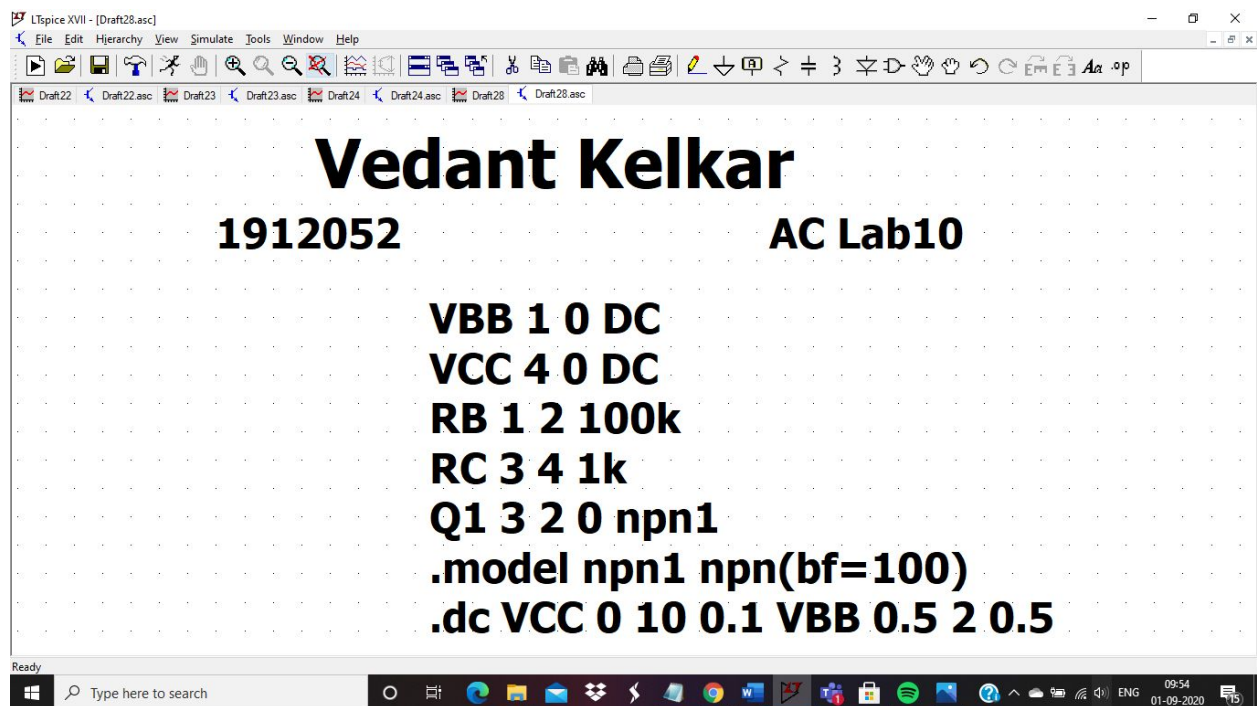

 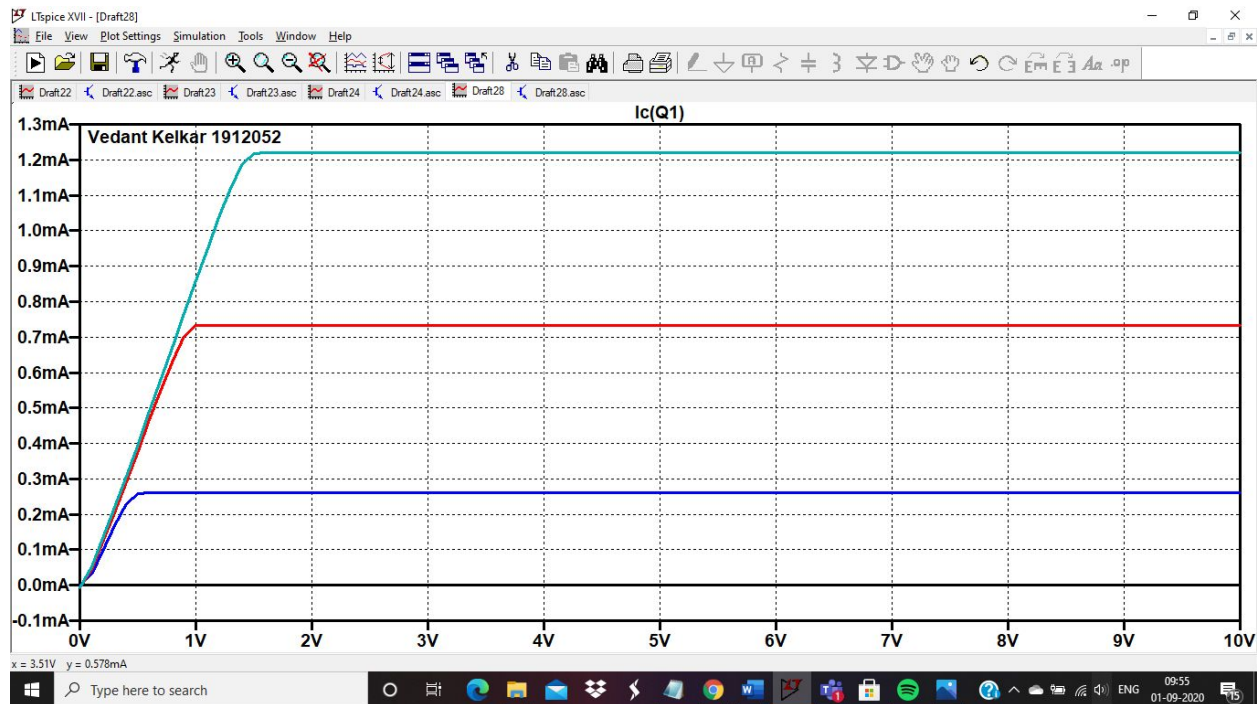




0

0

100mV	234.59uA
200mV	702.03uA
300mV	733.28uA
500mV	734.13uA
1V	0.736mA
3V	0.736mA
5V	0.736mA
8V	0.736mA

INPUT CHARACTERISTICS

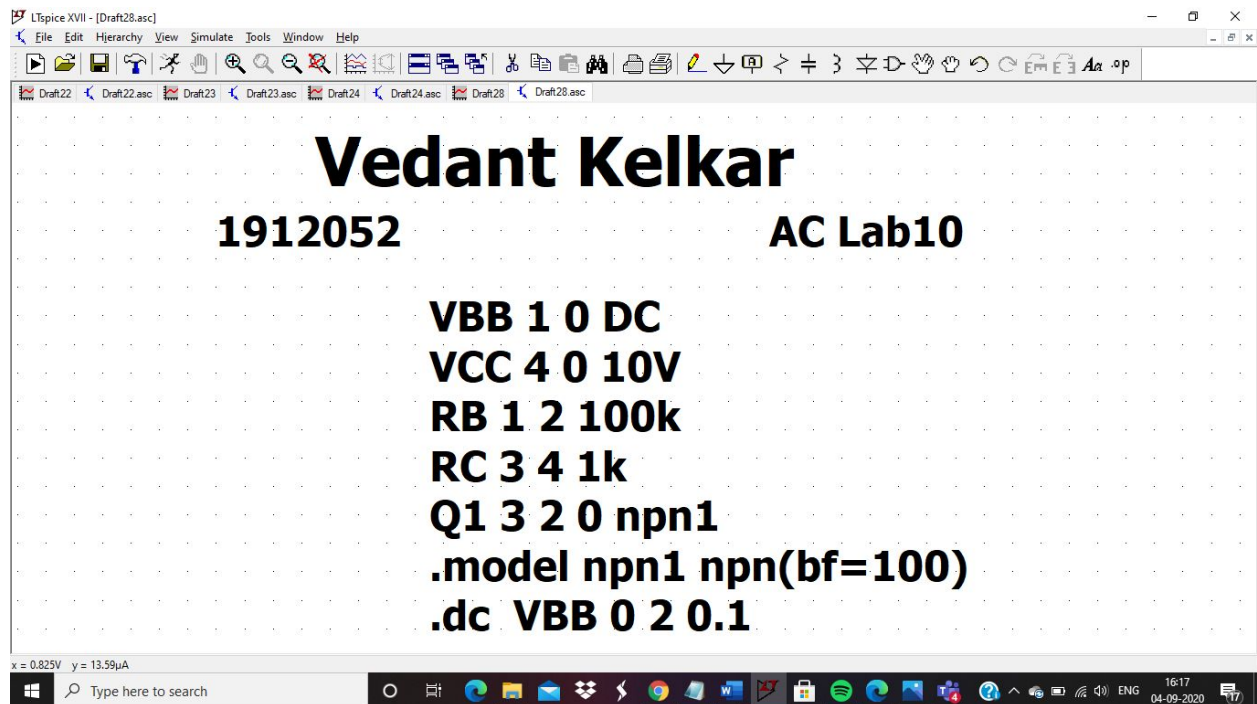

  

VBE	IB
-----	----

0	0
200mV	-9.5963748pA
400mV	-1.702713pA
600mV	16.775463nA
700mV	669.39401nA
750mV	3.9821223μA
760mV	5.8757558μA
770mV	8.6556765μA

AC LAB 10 is approved: Inderjit Singh Dhanjal