

# **AUDIT COURSE ELECTRONIC CIRCUITS 1: SIMULATION BASED STUDY**

## **LAB 15**

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

**Date: 28/9/2020**

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

**Time slot allotted to you all for the completion of WEEK 8 DAY 1 is 40 MINUTES**



**Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.**



**Follow these instruction strictly:**

- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen ( time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of WEEK 8 DAY 1


**You are entitled for 1 CREDIT per Lab only if you follow above instruction to the details**

**STUDENTS WORK AREA STARTS HERE**

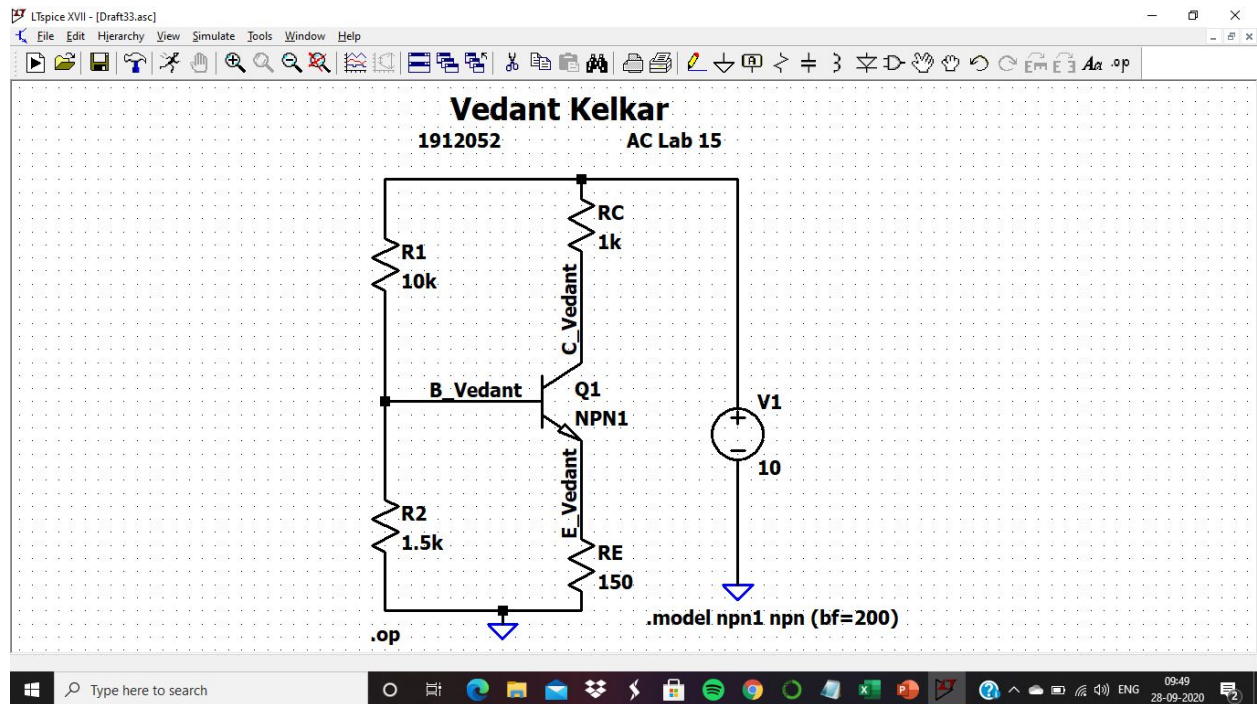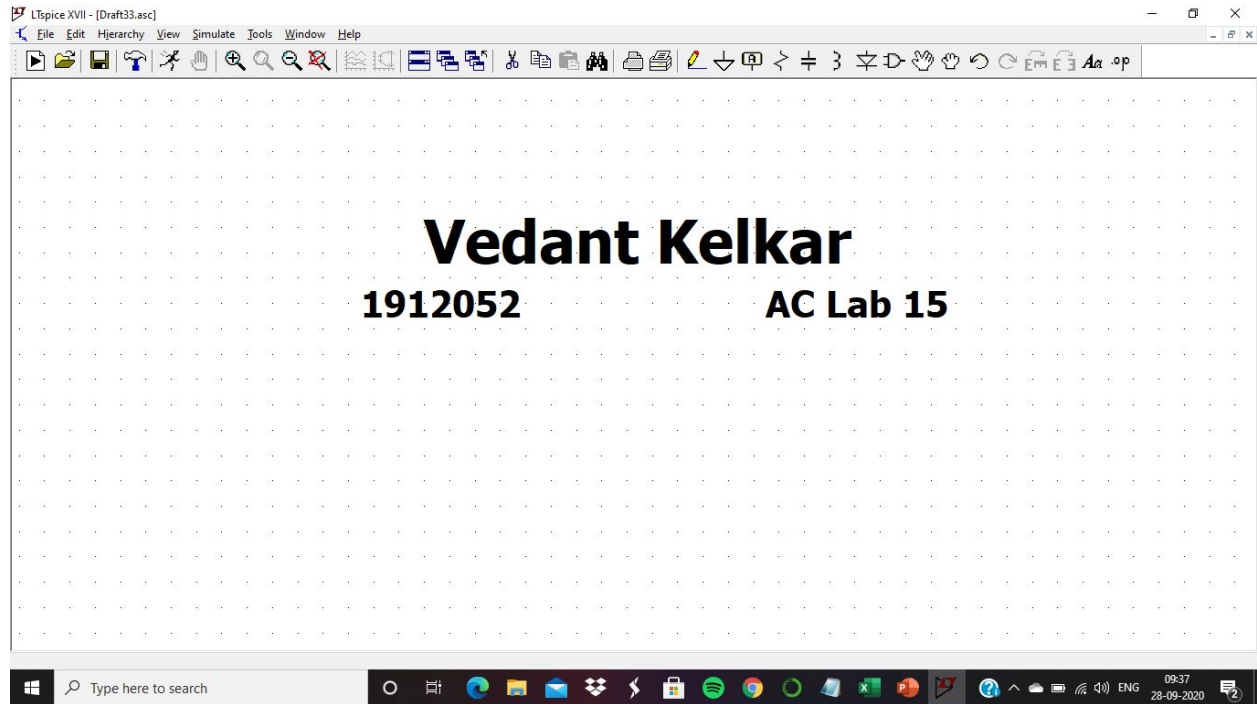

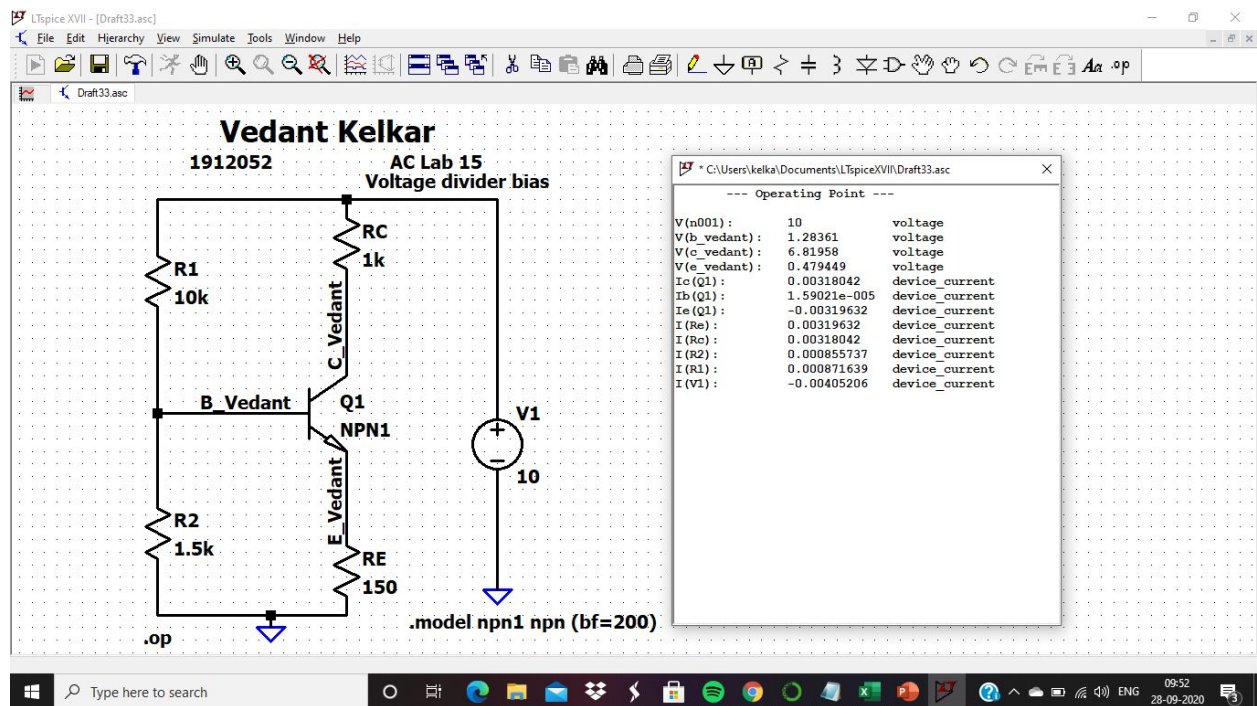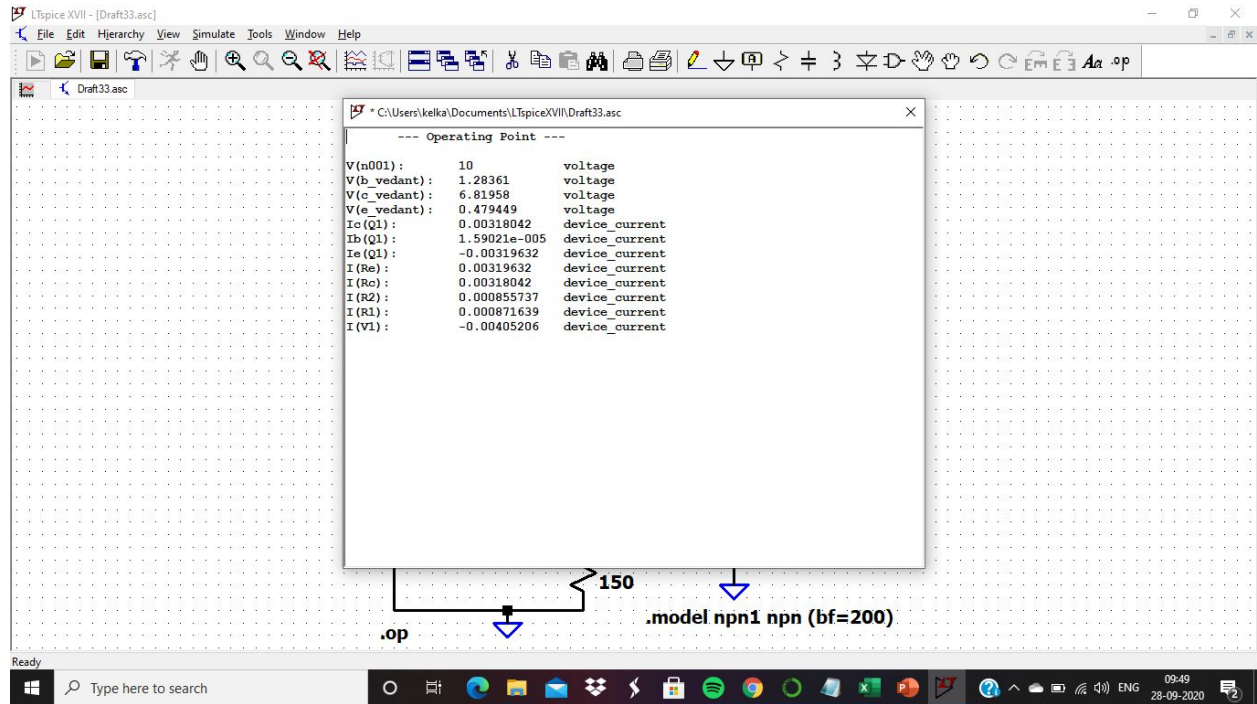


2N222 TRANSISTER  
B=200

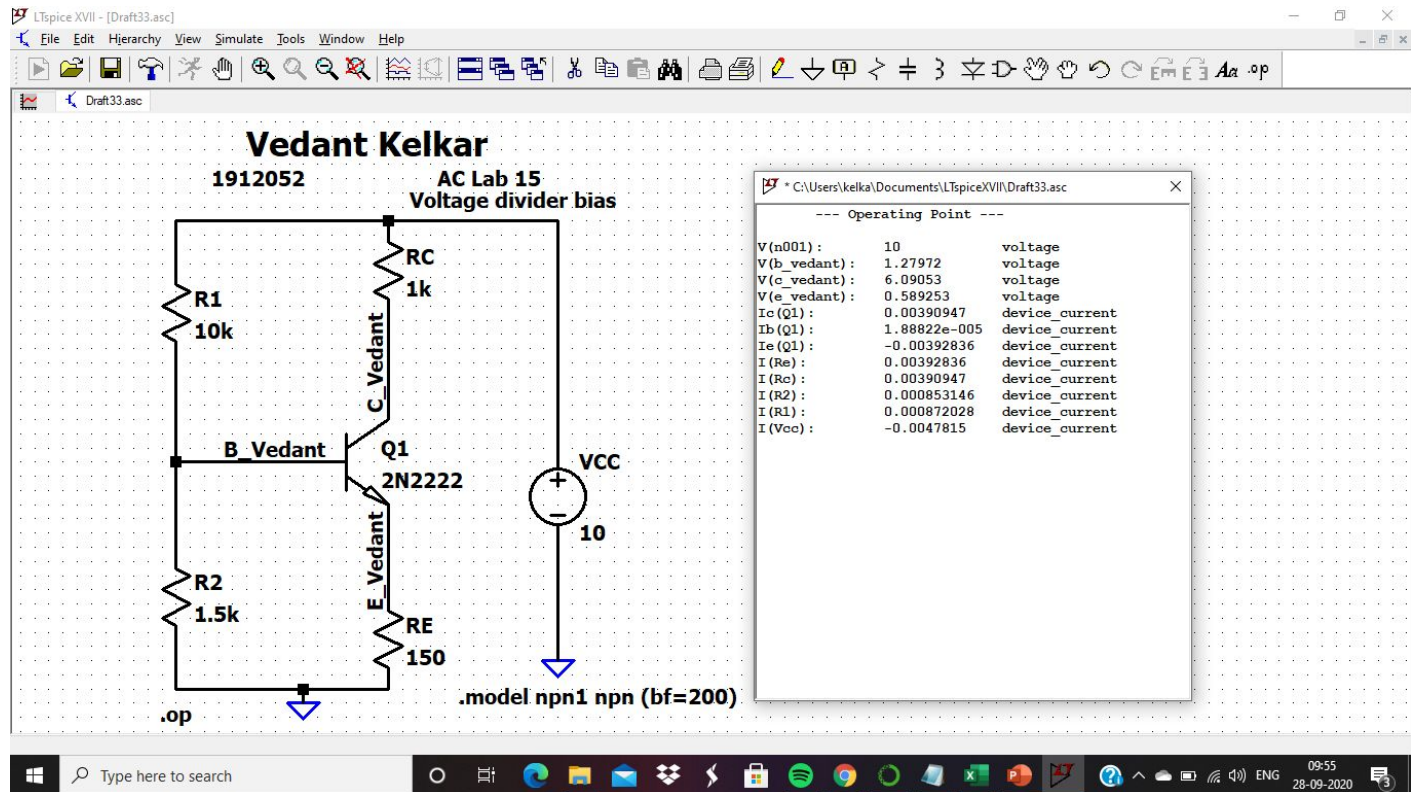


**V(n001): 10 voltage**  
**V(b\_vedant): 1.27972 voltage**  
**V(c\_vedant): 6.09053 voltage**  
**V(e\_vedant): 0.589253 voltage**  
**Ic(Q1): 0.00390947 device\_current**  
**Ib(Q1): 1.88822e-005 device\_current**  
**Ie(Q1): -0.00392836 device\_current**  
**I(Re): 0.00392836 device\_current**  
**I(Rc): 0.00390947 device\_current**  
**I(R2): 0.000853146 device\_current**  
**I(R1): 0.000872028 device\_current**  
**I(Vcc): -0.0047815 device\_current**

IBQ Simulted	IBQ Calculated	ICQ Simulted	ICQ Calculated	VCEQ Simulted	VCEQ Calculated
18.88uA	19.2uA	3.909uA	3.84uA	5.501V	5.584V

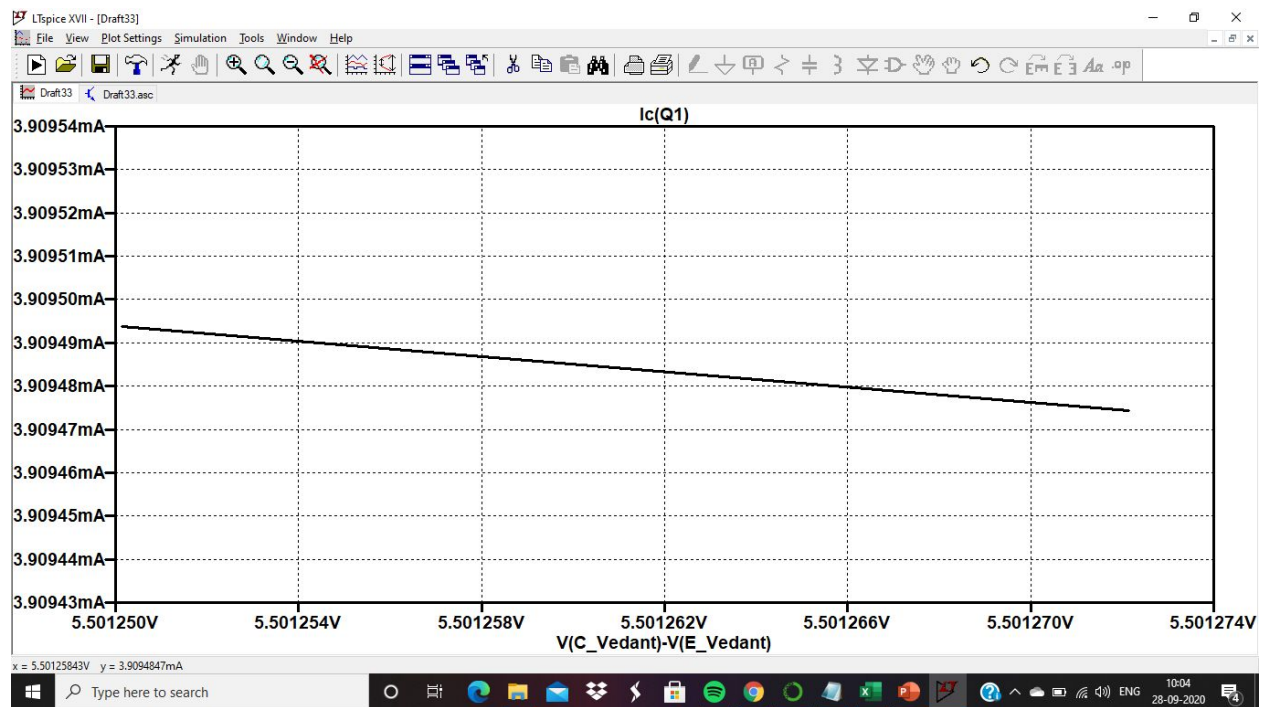


**2N3904 TRANSISTER**  
**B=300**



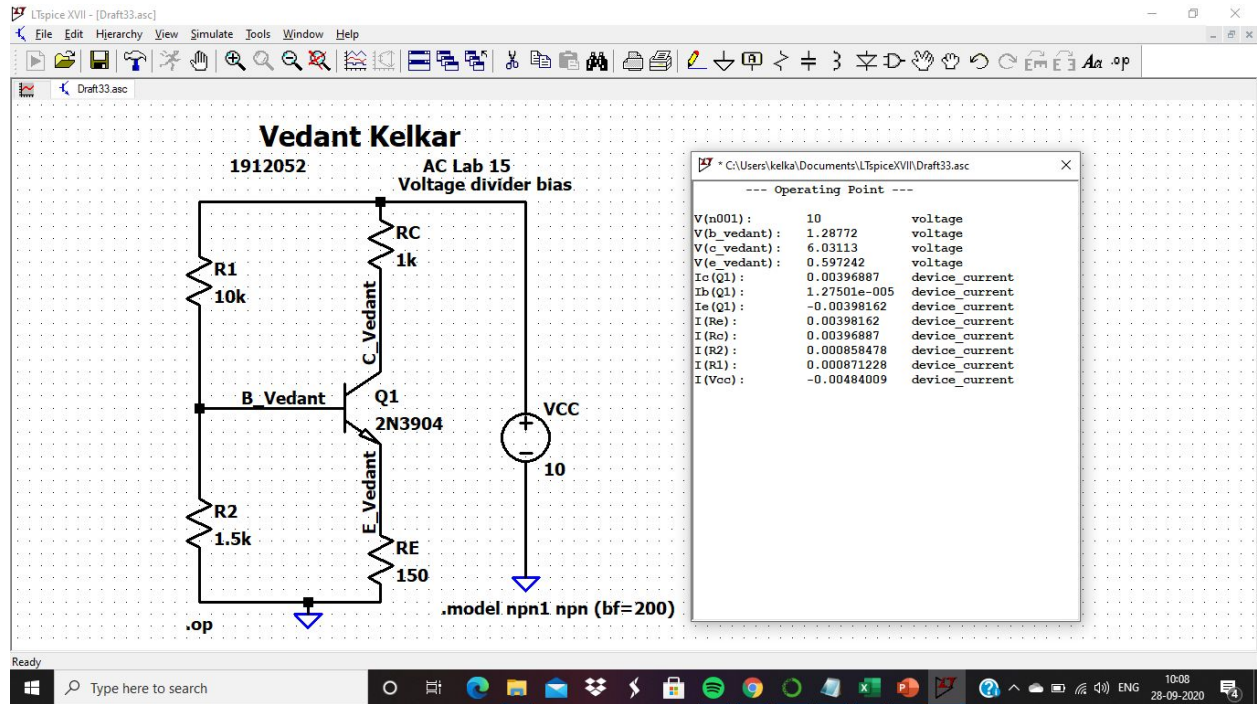

**V(n001): 10 voltage**  
**V(b\_vedant): 1.28772 voltage**  
**V(c\_vedant): 6.03113 voltage**  
**V(e\_vedant): 0.597242 voltage**  
**Ic(Q1): 0.00396887 device\_current**  
**Ib(Q1): 1.27501e-005 device\_current**  
**Ie(Q1): -0.00398162 device\_current**  
**I(Re): 0.00398162 device\_current**  
**I(Rc): 0.00396887 device\_current**  
**I(R2): 0.000858478 device\_current**  
**I(R1): 0.000871228 device\_current**  
**I(Vcc): -0.00484009 device\_current**

**BVW60A TRANSISTER**  
**B=120**

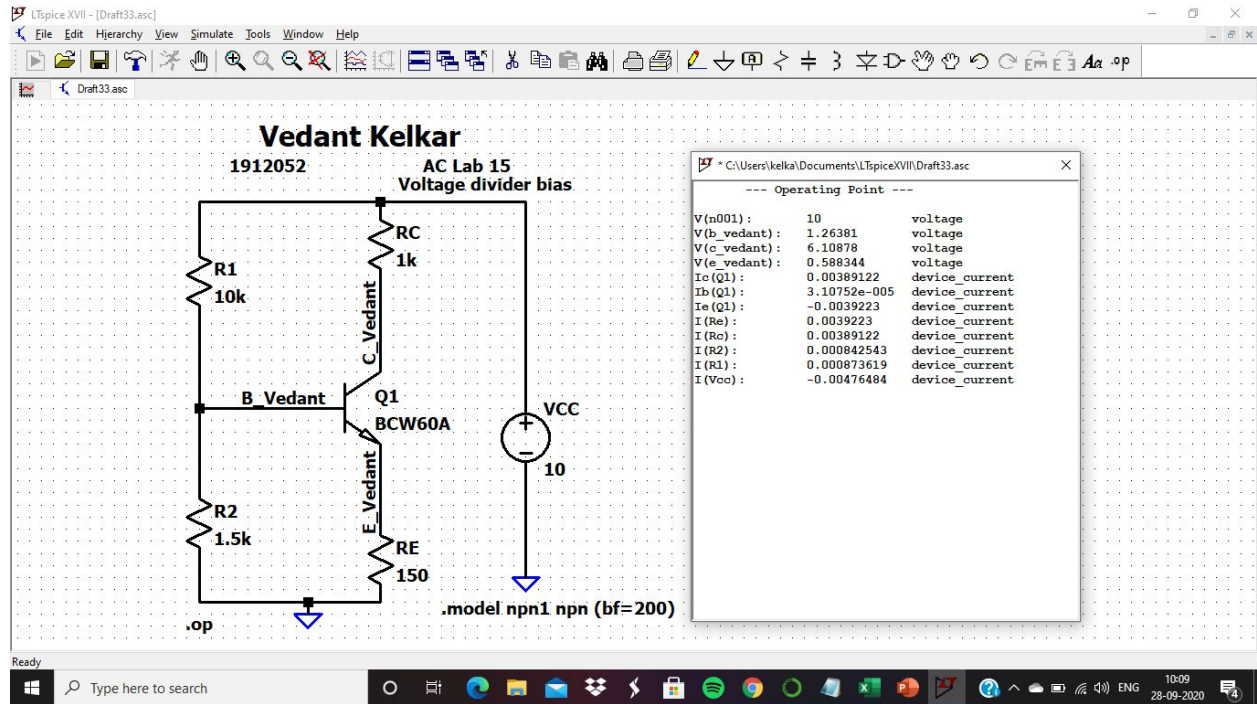

**V(n001): 10 voltage**  
**V(b\_vedant): 1.26381 voltage**  
**V(c\_vedant): 6.10878 voltage**  
**V(e\_vedant): 0.588344 voltage**  
**Ic(Q1): 0.00389122 device\_current**  
**Ib(Q1): 3.10752e-005 device\_current**  
**Ie(Q1): -0.0039223 device\_current**  
**I(Re): 0.0039223 device\_current**  
**I(Rc): 0.00389122 device\_current**  
**I(R2): 0.000842543 device\_current**  
**I(R1): 0.000873619 device\_current**  
**I(Vcc): -0.00476484 device\_current**

B	ICQ	VCQ
120	3.8912mA	5.521V
200	3.909mA	5.5008V
300	3.968mA	5.4338V

Day \_\_\_\_\_

Date \_\_\_\_\_

syng

Thevinin at B

1912052

$$R_{th} = R_1 || R_2$$

$$R_{th} = \frac{10 \times 10^3 \times 1.5 \times 10^3}{10 \times 10^3 + 1.5 \times 10^3}$$

$$= 1.304 \text{ k}\Omega$$

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{cc} = \frac{1.5}{1.5 + 10} \times 100 = 1.304 \text{ V}$$

KVL at BE.

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$I_{BQ} = 19.202 \text{ }\mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 200 \times 19.202 \times 10^{-6}$$

$$I_{CQ} = 3.84 \text{ mA}$$



**AC LAB 15 is approved: Inderjit Singh Dhanjal**