

Audit Course Session 2

AUDIT COURSE ELECTRONIC CIRCUITS 2: SIMULATION BASED STUDY

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 19/1/2021

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of Session 1 is 40 MINUTES



Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.



Follow these instruction strictly:

- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of Session 1

You are entitled for 1 CREDIT per session only if you follow above instruction to the details

STUDENTS WORK AREA STARTS HERE

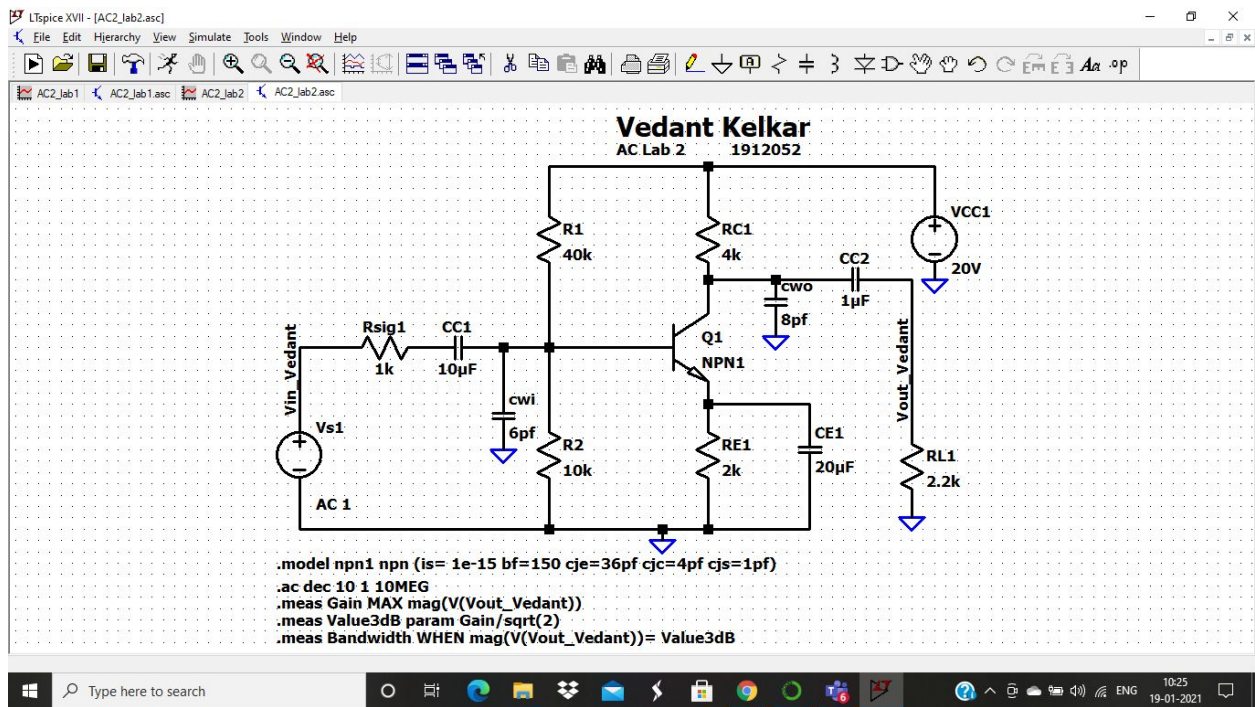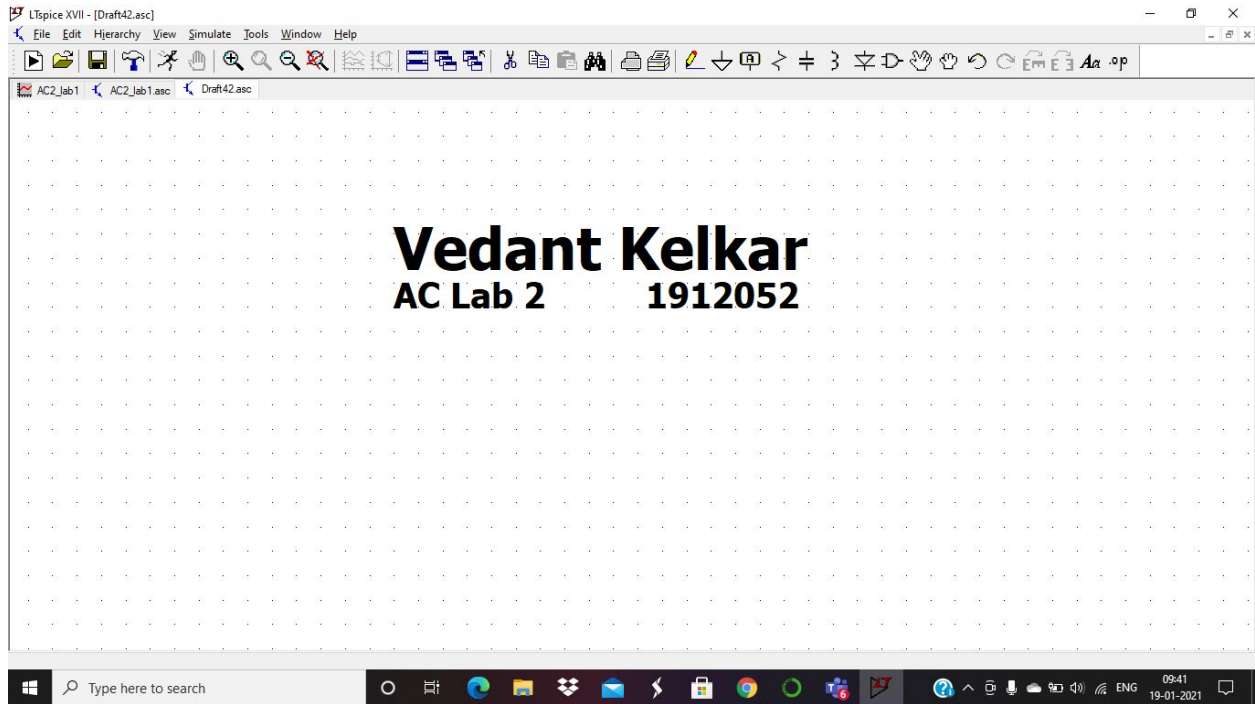

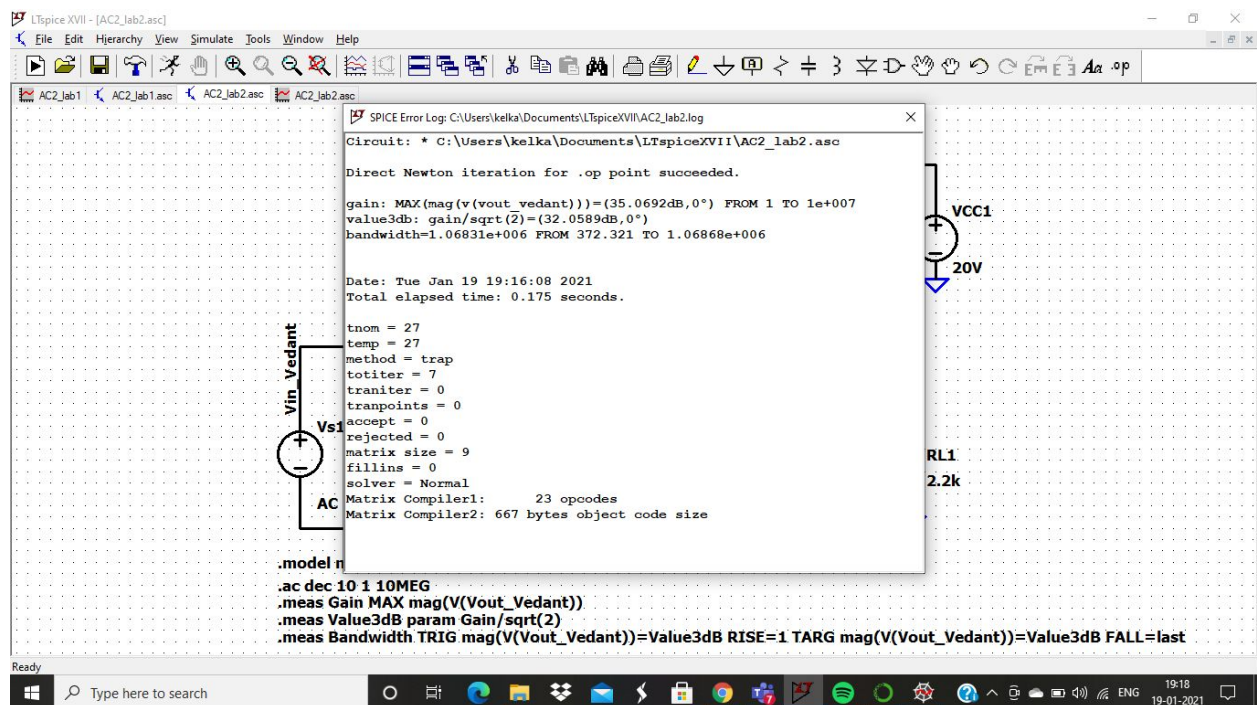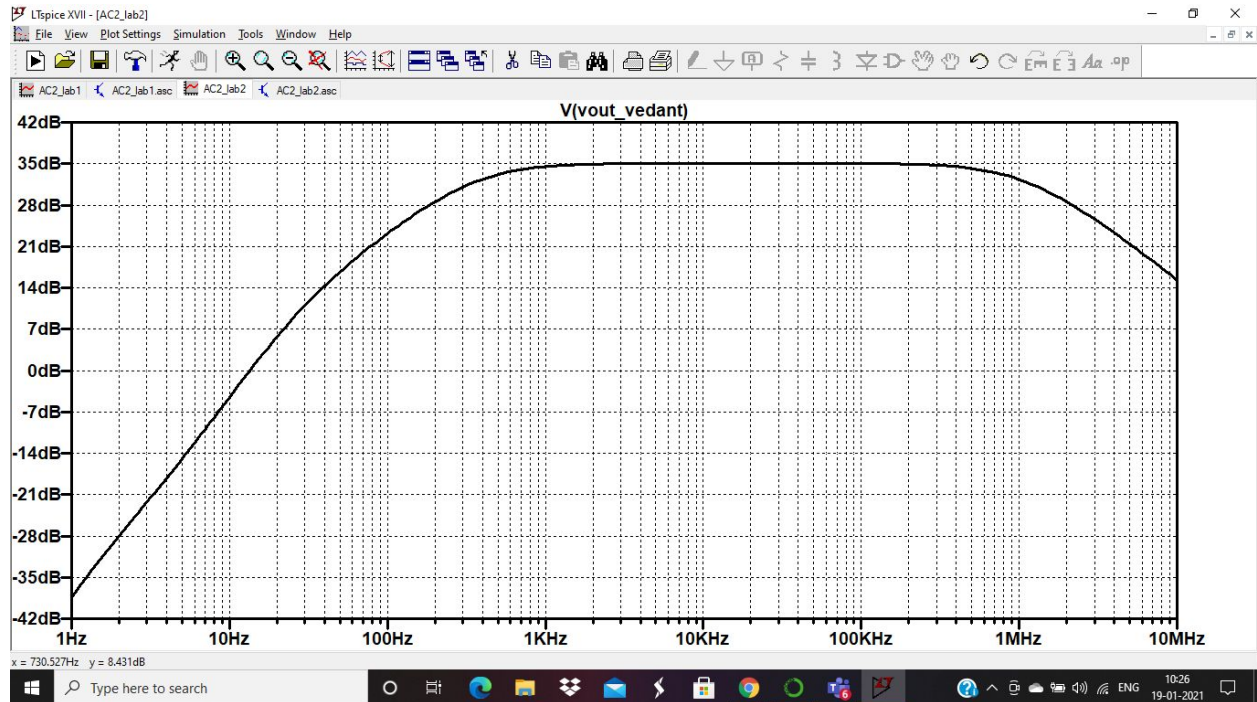

LTspice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2.asc AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.log

Circuit: * C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.asc

Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- Bipolar Transistors ---

Name:	q1
Model:	npn1
Ib:	1.06e-05
Ic:	1.58e-03
Vbe:	7.27e-01
Vbc:	-9.75e+00
Vce:	1.05e+01
BetaDC:	1.50e+02
Gm:	6.12e-02
Rpi:	2.45e+03
Rx:	0.00e+00
Ro:	0.00e+00
Cbe:	5.93e-11
Cbc:	1.67e-12
Cjs:	1.00e-12
BetaAC:	1.50e+02
Cbx:	0.00e+00
Ft:	1.60e+08

Vin Vedant
 Vs1
 AC 1
 Rsig1
 1k
 1

```

.model npn1 npn (is=
.ac dec 10 1 10MEG
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
.op
  
```



Ready

Type here to search

18:55
26-01-2021

BW sim	BW calc
1.06831MHz	1.2895MHz

Ex1

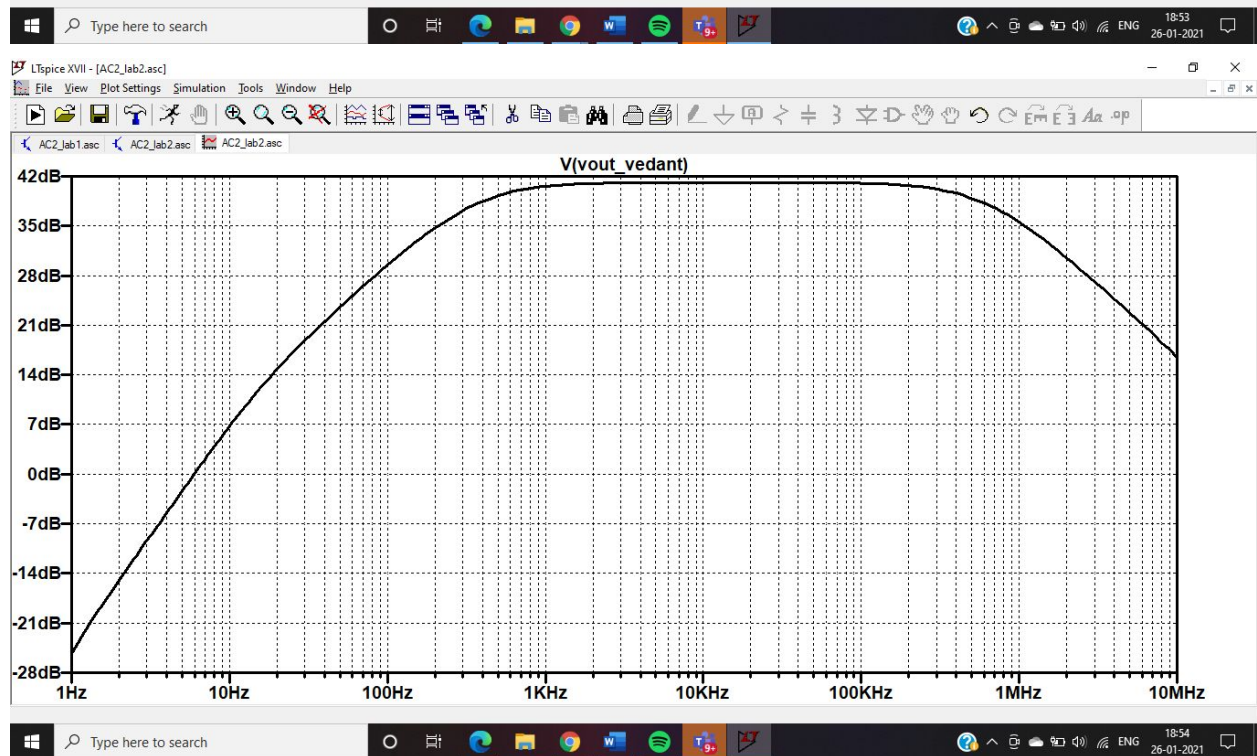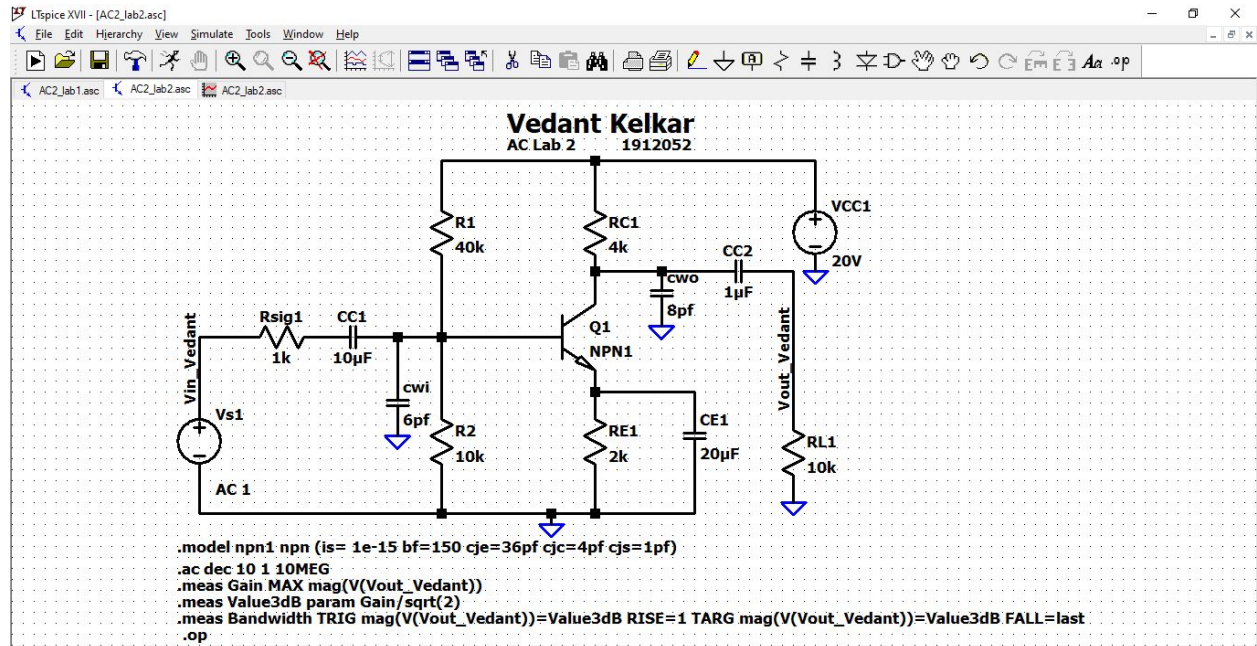

LTspice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2.asc AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.log

Circuit: * C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.asc

Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- Bipolar Transistors ---

Name: q1
Model: npn1
Ib: 1.06e-05
Ic: 1.58e-03
Vbe: 7.27e-01
Vbc: -9.75e+00
Vce: 1.05e+01
BetaDC: 1.50e+02
Gm: 6.12e-02
Rpi: 2.45e+03
Rx: 0.00e+00
Ro: 0.00e+00
Cbe: 5.93e-11
Cbc: 1.67e-12
Cjs: 1.00e-12
BetaAC: 1.50e+02
Cbx: 0.00e+00
Ft: 1.60e+08

Vin Vredant
 Vs1
 AC 1
 Rsig1
 1k
 1

.model npn1 npn (is=
 .ac dec 10 1 10MEG
 .meas Gain MAX mag(V(Vout_Vedant))
 .meas Value3dB param Gain/sqrt(2)
 .meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
 .op

Ready

Type here to search

18:54
26-01-2021

LTspice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2.asc AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.log

Ft: 1.60e+08

gain: MAX(mag(v(vout_vedant)))=(41.1458dB,0°) FROM 1 TO 1e+007
 value3db: gain/sqrt(2)=(38.1355dB,0°)
 bandwidth=612429 FROM 370.856 TO 612800

Date: Tue Jan 26 18:53:35 2021
 Total elapsed time: 0.126 seconds.

tnom = 27
 temp = 27
 method = trap
 totiter = 7
 traniter = 0
 tranpoints = 0
 accept = 0
 rejected = 0
 matrix size = 9
 fillins = 0
 solver = Normal
 Matrix Compiler1: 23 opcodes
 Matrix Compiler2: 667 bytes object code size

Vin Vredant
 Vs1
 AC 1
 Rsig1
 1k
 1

.model npn1 npn (is=
 .ac dec 10 1 10MEG
 .meas Gain MAX mag(V(Vout_Vedant))
 .meas Value3dB param Gain/sqrt(2)
 .meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
 .op

Ready

Type here to search

18:54
26-01-2021

BW sim	BW calc
612429Hz	613.52KHz

Ex2

LTSpice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2.asc AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTSpiceXVII\AC2_lab2.log

BetaAC: 1.50e+02
Cbx: 0.00e+00
Ft: 1.61e+08

gain: MAX(mag(v(vout_vedant)))=(35.0692dB,0°) FROM 1 TO 1e+007
value3db: gain/sqrt(2)=(32.0589dB,0°)
bandwidth=1.28252e+006 FROM 372.344 TO 1.28289e+006

Date: Tue Jan 26 18:49:31 2021
Total elapsed time: 0.145 seconds.

tnom = 27
temp = 27
method = trap
totiter = 7
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 9
fillins = 0
solver = Normal
Matrix Compiler1: 23 opcodes
Matrix Compiler2: 667 bytes object code size

.model npn1 npn (is=1e-15
.ac dec 10 1 10MEG
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
.op

Ready

Type here to search

18:50
26-01-2021

LTSpice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2.asc AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTSpiceXVII\AC2_lab2.log

Circuit: * C:\Users\kelka\Documents\LTSpiceXVII\AC2_lab2.asc

Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- Bipolar Transistors ---

Name: q1
Model: npn1
Ib: 1.06e-05
Ic: 1.58e-03
Vbe: 7.27e-01
Vbc: -9.75e+00
Vce: 1.05e+01
BetaDC: 1.50e+02
Gm: 6.12e-02
Rpi: 2.45e+03
Rx: 0.00e+00
Ro: 0.00e+00
Cbe: 5.93e-11
Cbc: 1.26e-12
Cjs: 1.00e-12
BetaAC: 1.50e+02
Cbx: 0.00e+00
Ft: 1.61e+08


gain: MAX(mag(v(vout_vedant)))=(35.0692dB,0°) FROM 1 TO 1e+007
value3db: gain/sqrt(2)=(32.0589dB,0°)

.model npn1 npn (is=1e-15
.ac dec 10 1 10MEG
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
.op

Ready



Type here to search

18:52
26-01-2021

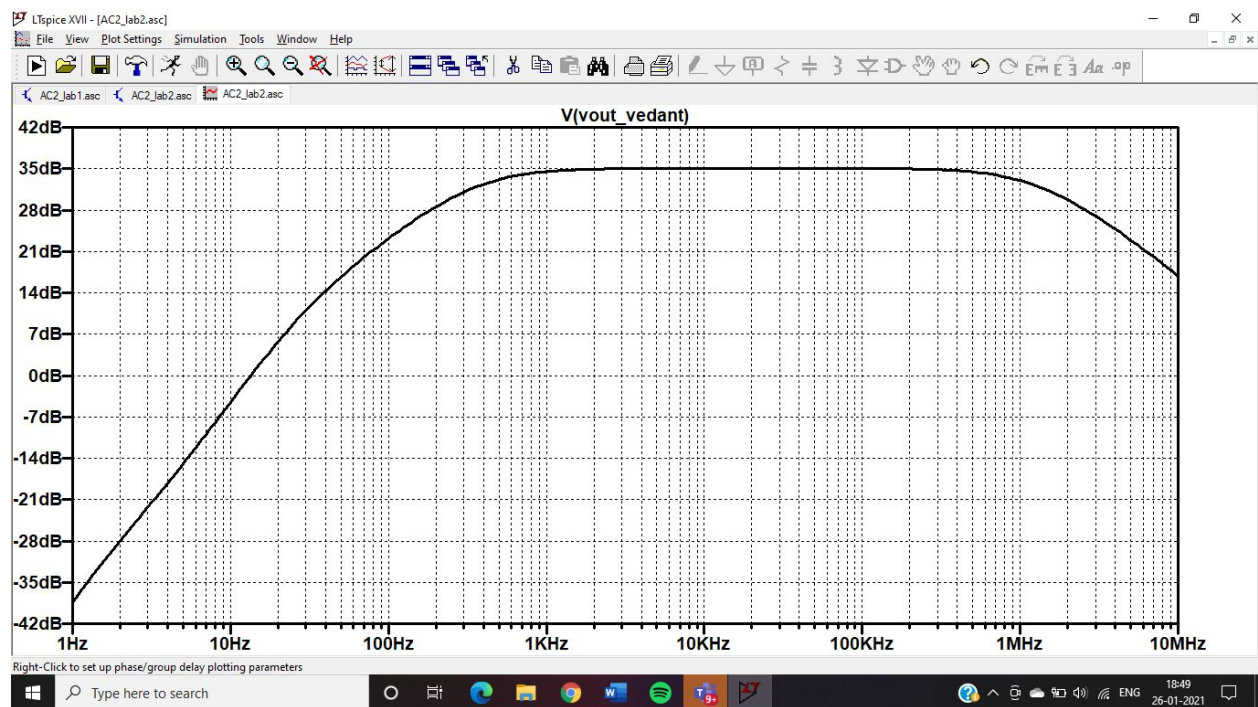

BW sim	BW calc
1.28252MHz	1.3021MHz

Ex3

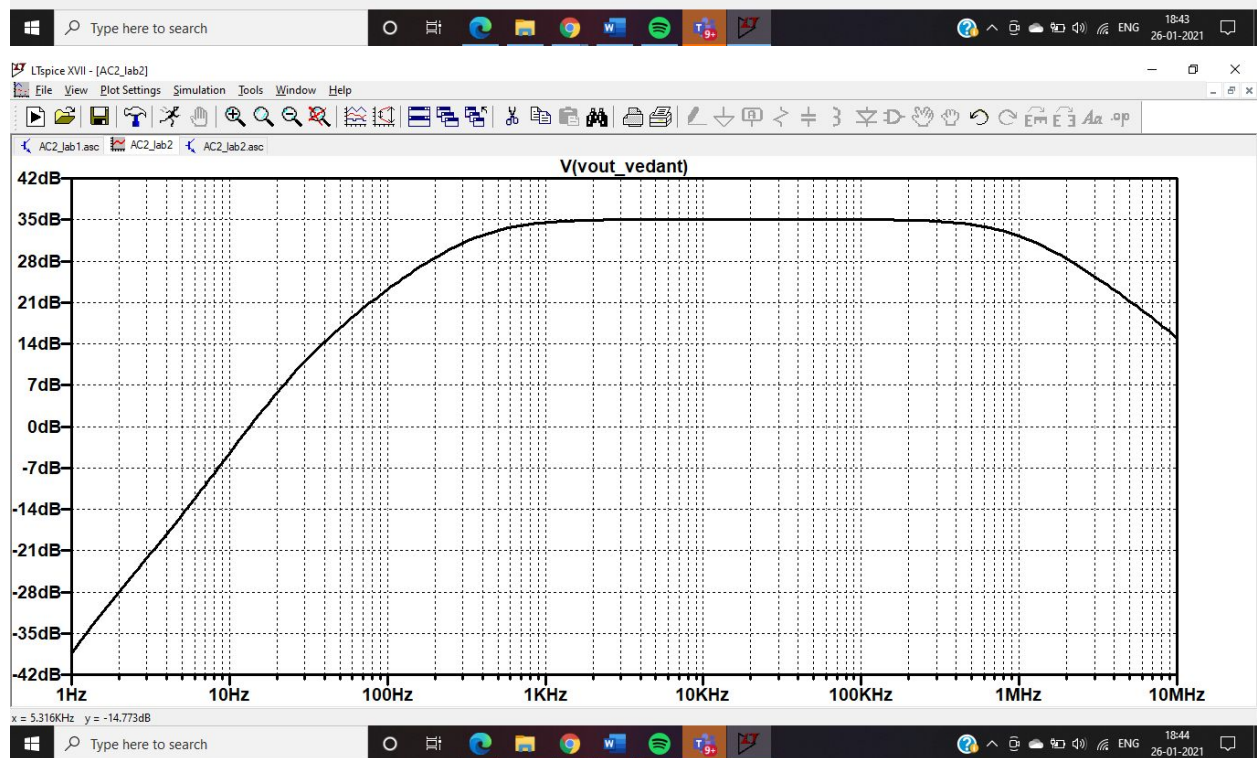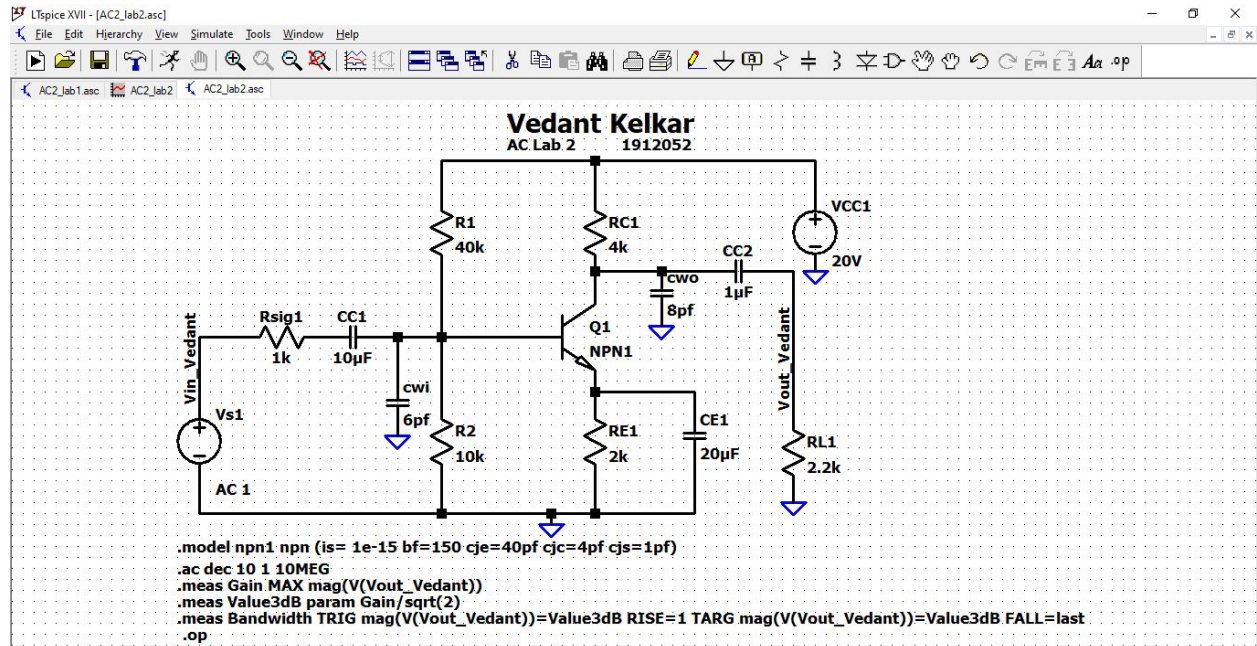

LTspice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2 AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.log

BetaAC: 1.50e+02
Cbx: 0.00e+00
Ft: 1.44e+08

gain: MAX(mag(v(vout_vedant)))=(35.0692dB,0°) FROM 1 TO 1e+007
value3db: gain/sqrt(2)=(32.0589dB,0°)
bandwidth=1.03959e+006 FROM 372.318 TO 1.03996e+006

Date: Tue Jan 26 18:42:56 2021
Total elapsed time: 0.078 seconds.

tnom = 27
temp = 27
method = trap
totiter = 7
traniter = 0
tranpoints = 0
accept = 0
rejected = 0
matrix size = 9
fillins = 0
solver = Normal
Matrix Compiler1: 23 opcodes
Matrix Compiler2: 667 bytes object code size

Vin_Vedant
Vs1
AC 1
Rsig1
1k

```

.model npn1 npn (is=
.ac dec 10 1 10MEG
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
.op

```

Ready

Type here to search

18:44
26-01-2021

LTspice XVII - [AC2_lab2.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab1.asc AC2_lab2 AC2_lab2.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.log

Circuit: * C:\Users\kelka\Documents\LTspiceXVII\AC2_lab2.asc

Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- Bipolar Transistors ---

Name: q1
Model: npn1
Ib: 1.06e-05
Ic: 1.58e-03
Vbe: 7.27e-01
Vbc: -9.75e+00
Vce: 1.05e+01
BetaDC: 1.50e+02
Gm: 6.12e-02
Rpi: 2.45e+03
RX: 0.00e+00
Ro: 0.00e+00
Cbe: 6.58e-11
Cbc: 1.67e-12
Cjs: 1.00e-12
BetaAC: 1.50e+02
Cbx: 0.00e+00
Ft: 1.44e+08

Vin_Vedant
Vs1
AC 1
Rsig1
1k

```

.model npn1 npn (is=
.ac dec 10 1 10MEG
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas Bandwidth TRIG mag(V(Vout_Vedant))=Value3dB RISE=1 TARG mag(V(Vout_Vedant))=Value3dB FALL=last
.op

```

Ready

Type here to search

18:43
26-01-2021

BW sim	BW calc
1.03959MHz	1.1364MHz

Your AC LAB 2 is approved: Inderjit Singh Dhanjal