

AUDIT COURSE ELECTRONIC CIRCUITS 1: SIMULATION BASED STUDY

LAB 18

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 06/10/2020

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of WEEK 9 DAY 2 is 40 MINUTES


Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.

Follow these instruction strictly:

- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of WEEK 9 DAY 2

You are entitled for 1 CREDIT per Lab only if you follow above instruction to the details

STUDENTS WORK AREA STARTS HERE

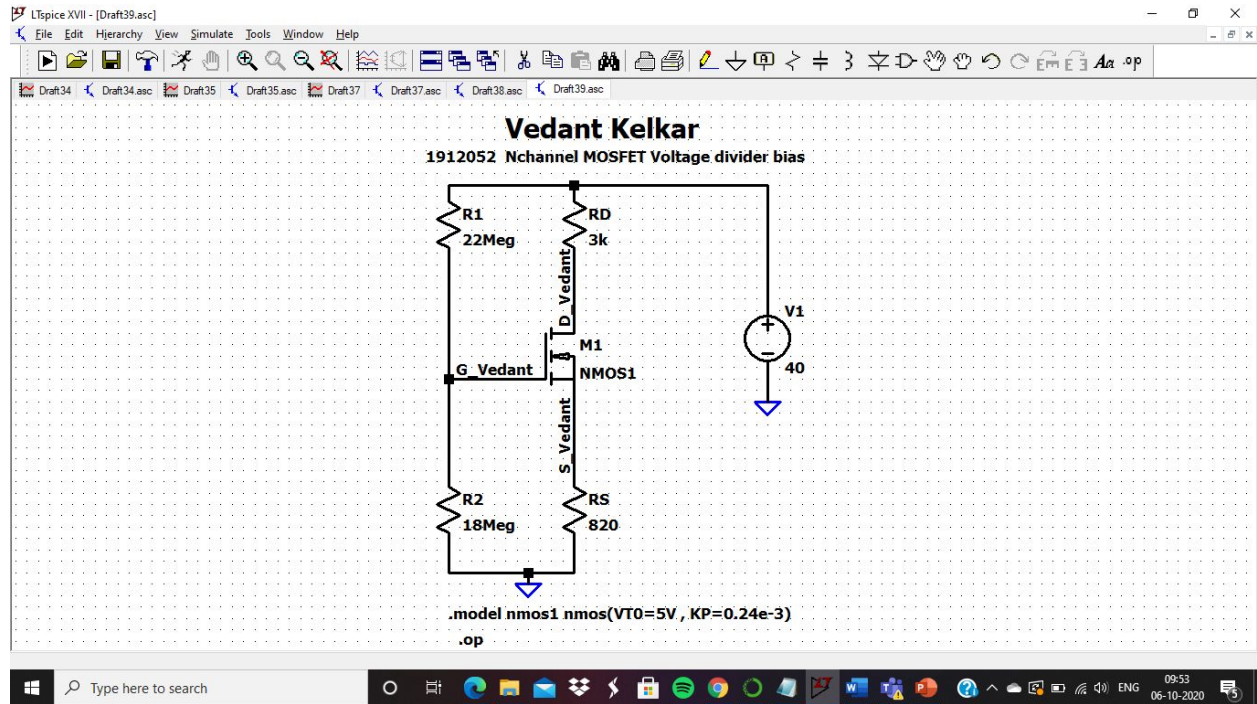

V(d_vedant): 19.8263 voltage

V(g_vedant): 18 voltage

V(s_vedant): 5.51414 voltage

V(n001): 40 voltage

Id(M1): 0.00672457 device_current

Ig(M1): 0 device_current

Ib(M1): -1.43222e-011 device_current

Is(M1): -0.00672457 device_current

I(Rs): 0.00672457 device_current

I(R2): 1e-006 device_current

I(R1): 1e-006 device_current

I(Rd): 0.00672457 device_current

I(V1): -0.00672557 device_current

ta

Day _____

Date _____

syngenta

1912052.

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{18 \times 10^6}{18 \times 10^6 + 22 \times 10^6} \times 40 = 18V$$

$$k_n = \frac{I_{D(on)}}{[V_{GS(on)} - V_{GS(th)}]^2} = \frac{3 \times 10^{-3}}{(10-5)^2} = 0.12 \text{ mA/V}^2$$

$$\boxed{k_n = 0.12 \text{ mA/V}^2}$$

$$V_{GS} = V_G - V_S = V_G - I_D R_S = 18 - I_D (820) \quad \text{--- (1)}$$

for saturation region

$$I_D = k_n (V_{GS} - V_{GS(th)})^2 = 0.12 \times 10^{-3} (V_{GS} - 5)^2$$

$$V_{GS} = 18 - 820 \times 0.12 \times 10^{-3} \times (V_{GS} - 5)^2$$

$$0.0984 (V_{GS}^2) + 0.016 V_{GS} - 15.54 = 0$$

$$V_{GS} = \frac{12.48 \text{ V}}{\checkmark} \quad / \quad V_{GS} = \frac{-12.64 \text{ V}}{\times}$$

Day _____

Date _____

syngenta

19/2052

$$I_D = K_n (V_{GS} - 5)^2 = 0.12 \times 10^{-3} \times (12.48 - 5)^2$$

$$I_D = 6.72 \text{ mA}$$

$$Q_{\text{point}} = (V_{DSQ}, I_{DQ}) = (12.48 \text{ V}, 6.72 \text{ mA})$$

$$V_{DS} = V_{DD} - I_{DQ} (R_D + R_S)$$

$$= 40 - 6.72 \times 10^{-3} (3 \text{ k}\Omega + 820)$$

$$= \underline{14.32}$$

I _D		V _{GS}		V _{DS}	
Sim	Calc	Sim	Calc	Sim	Calc
6.724mA	6.72mA	12.4858V	12.48V	14.31V	14.32V

AC LAB 18 is approved: Inderjit Singh Dhanjal