

Audit Course Session 3

AUDIT COURSE ELECTRONIC CIRCUITS 2: SIMULATION BASED STUDY

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 25/1/2021

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of Session 1 is 40 MINUTES



Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.



Follow these instruction strictly:


- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of Session 3

You are entitled for 1 CREDIT per session only if you follow above instruction to the details

STUDENTS WORK AREA STARTS HERE

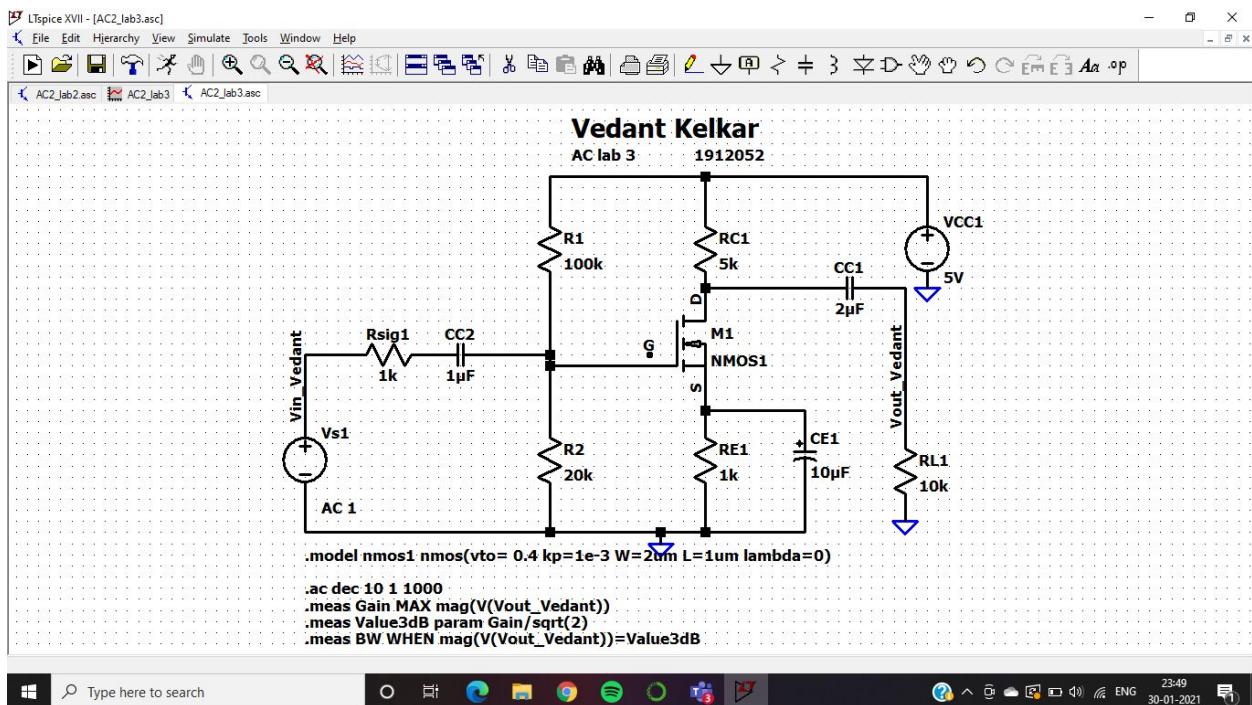
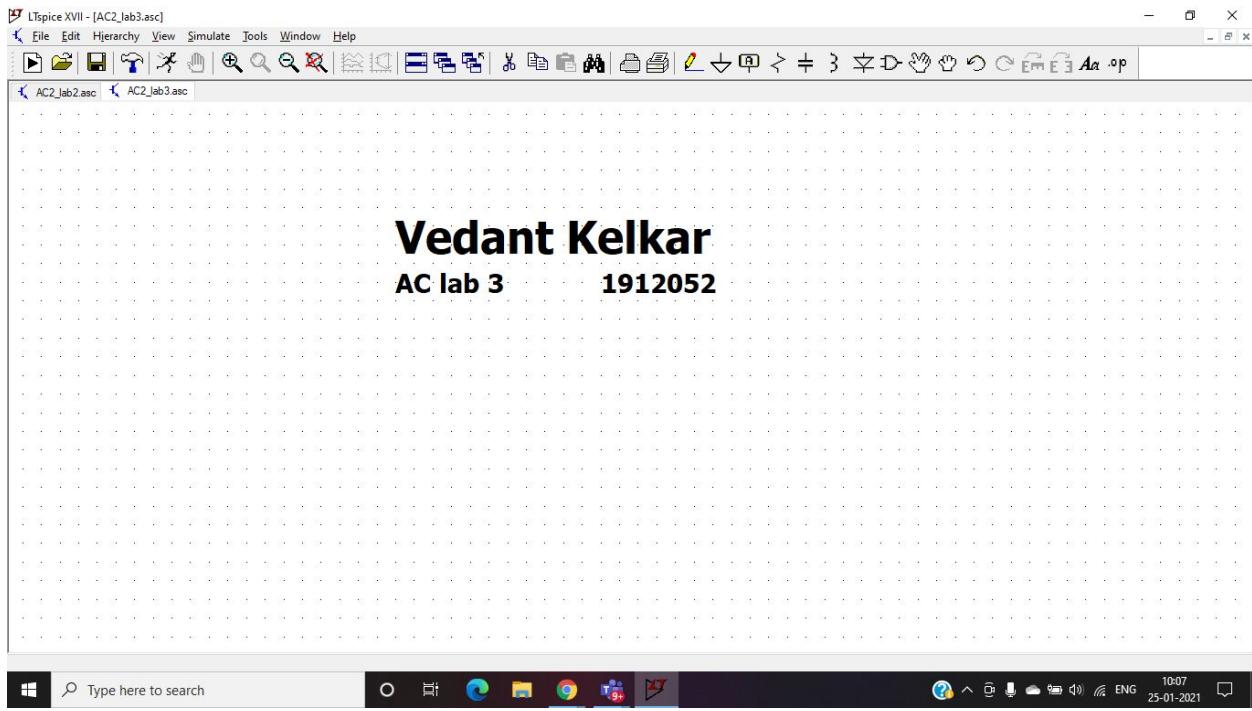


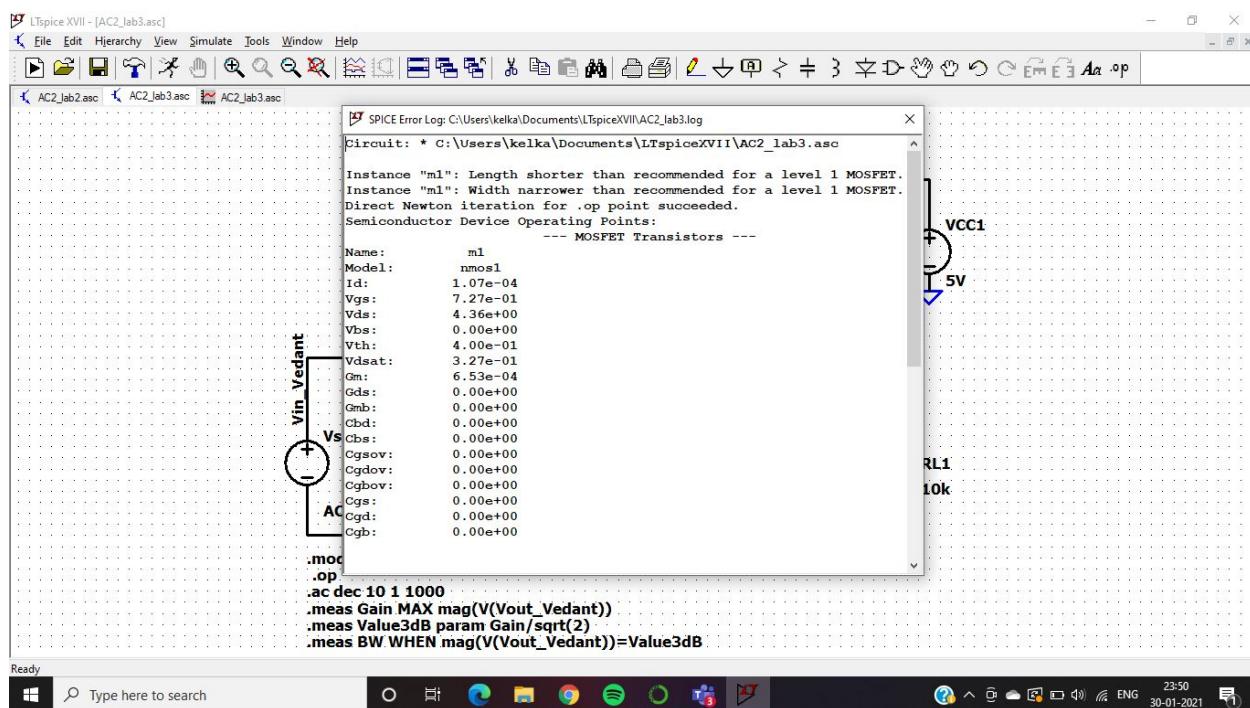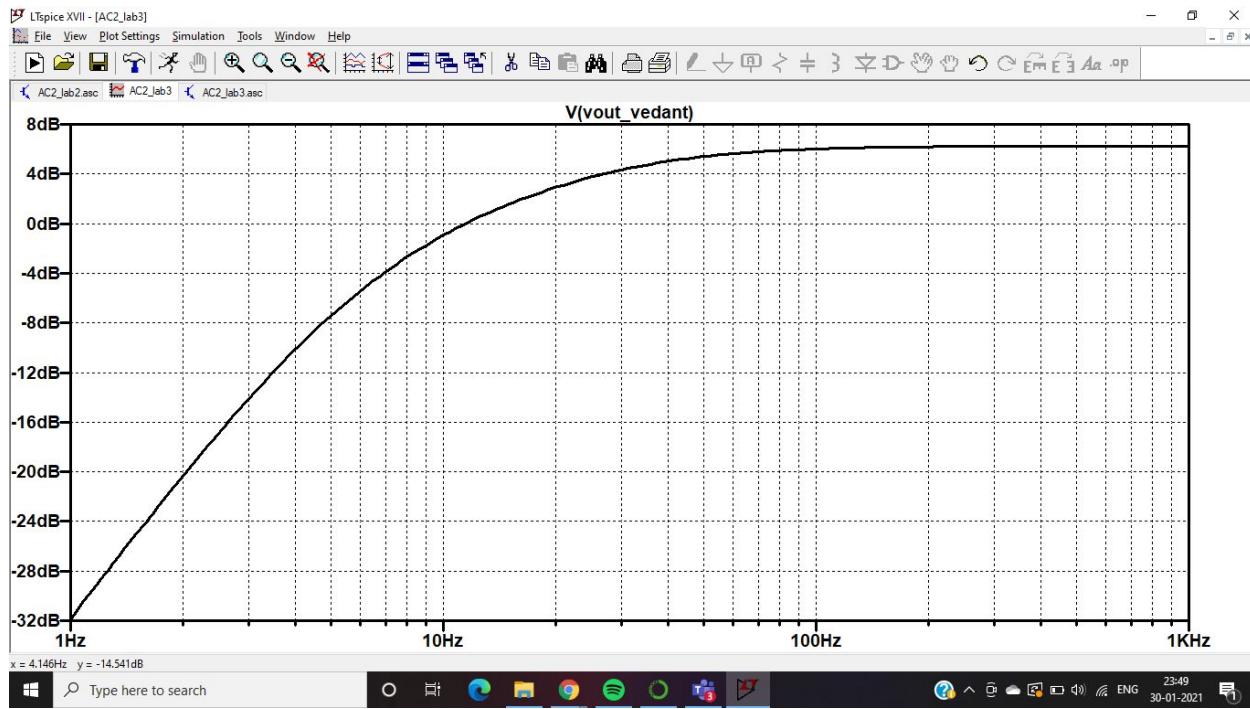

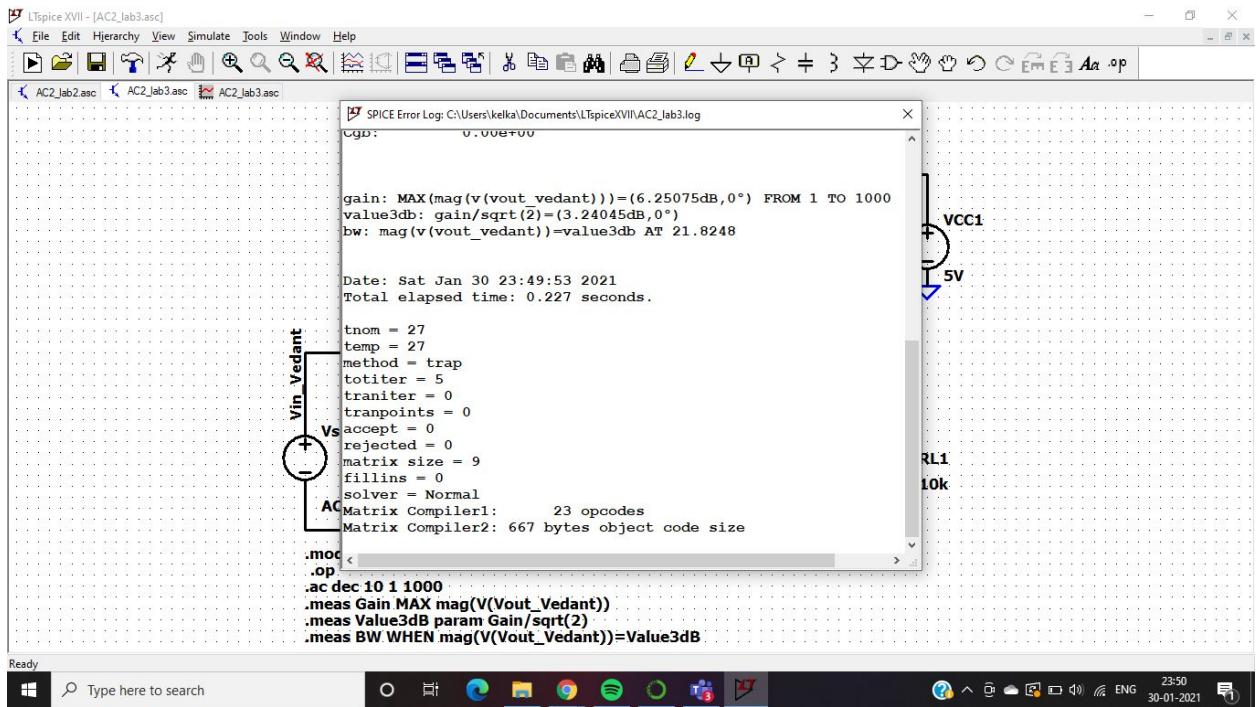

	SIM
Id	107 A
Vgs	0.727 V
gm	653 mA/V
fL	21.8248 Hz
Avmid	6.25075 dB

EX1

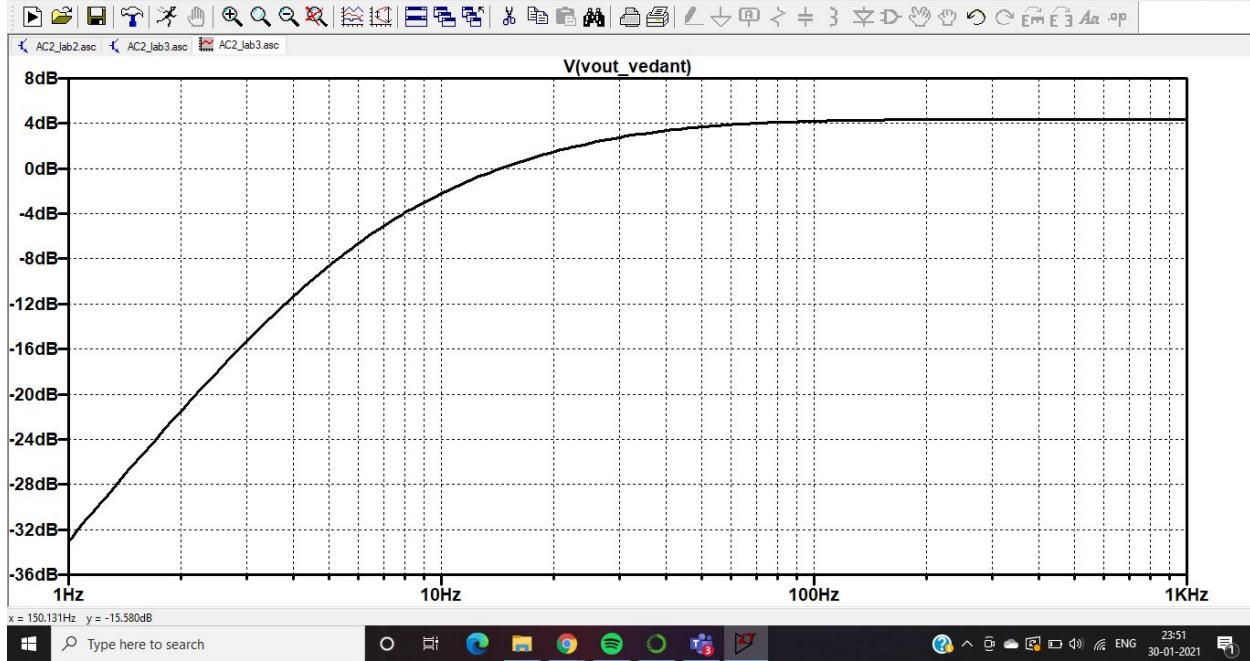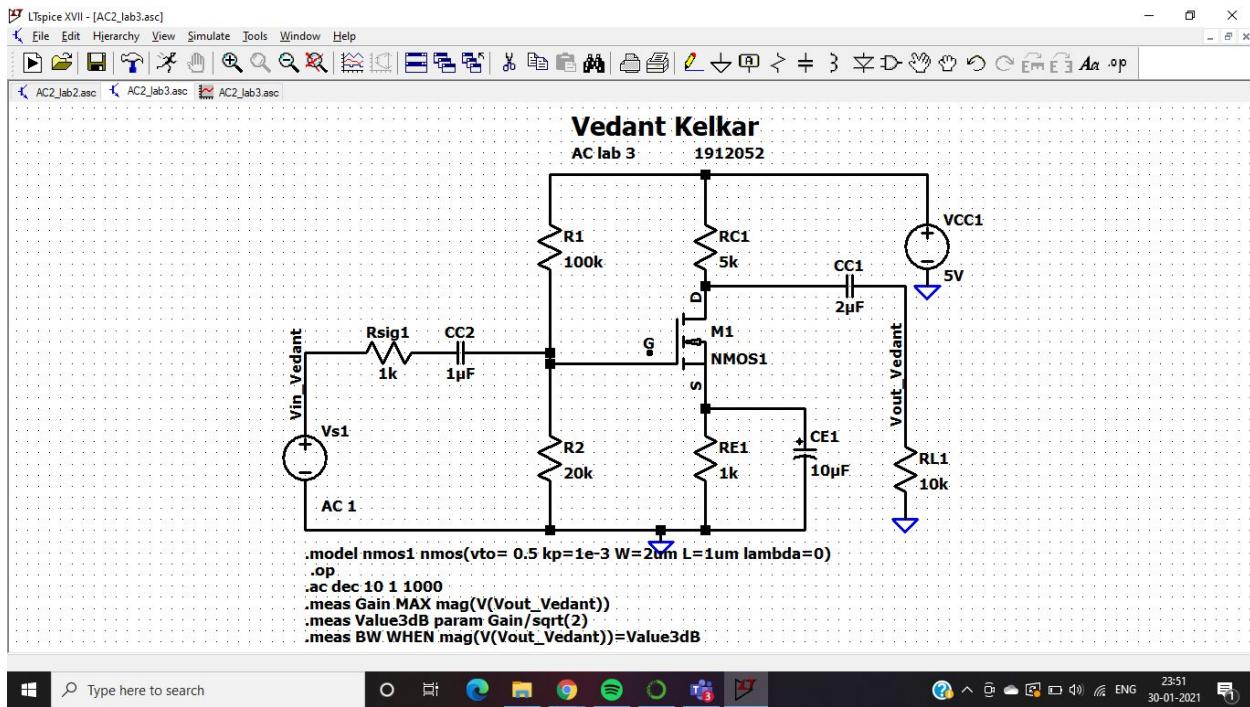

Ltspice XVII - [AC2_lab3.asc]

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.log

Circuit: * C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.asc

Instance "m1": Length shorter than recommended for a level 1 MOSFET.
 Instance "m1": Width narrower than recommended for a level 1 MOSFET.
 Direct Newton iteration for .op point succeeded.
 Semiconductor Device Operating Points:
 --- MOSFET Transistors ---

Name:	m1
Model:	nmos1
Id:	6.96e-05
Vgs:	7.64e-01
Vds:	4.58e+00
Vbs:	0.00e+00
Vth:	5.00e-01
Vdsat:	2.64e-01
Gm:	5.28e-04
Gds:	0.00e+00
Gmb:	0.00e+00
Cbd:	0.00e+00
Cbs:	0.00e+00
Cgsov:	0.00e+00
Cgdov:	0.00e+00
Cgbov:	0.00e+00
Cgs:	0.00e+00
Cgd:	0.00e+00
Cgb:	0.00e+00

```
.mod nmos1
.op
.ac dec 10 1 1000
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas BW WHEN mag(V(Vout_Vedant))=Value3dB
```

Ready

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.log

cgd: v.vout=vvv

gain: MAX(mag(v(vout_vedant)))=(4.39413dB,0°) FROM 1 TO 1000
 value3db: gain/sqrt(2)=(1.38383dB,0°)
 bw: mag(v(vout_vedant))=value3db AT 19.5324

Date: Sat Jan 30 23:51:54 2021
 Total elapsed time: 0.215 seconds.

tnom = 27
temp = 27
method = trap
totiter = 5
tranriter = 0
trapoints = 0
accept = 0
rejected = 0
matrix size = 9
fillins = 0
solver = Normal
Matrix Compiler1: 23 opcodes
Matrix Compiler2: 667 bytes object code size



```
.mod nmos1
.op
.ac dec 10 1 1000
.meas Gain MAX mag(V(Vout_Vedant))
.meas Value3dB param Gain/sqrt(2)
.meas BW WHEN mag(V(Vout_Vedant))=Value3dB
```

Ready

Avmid

4.3941dB

EX2

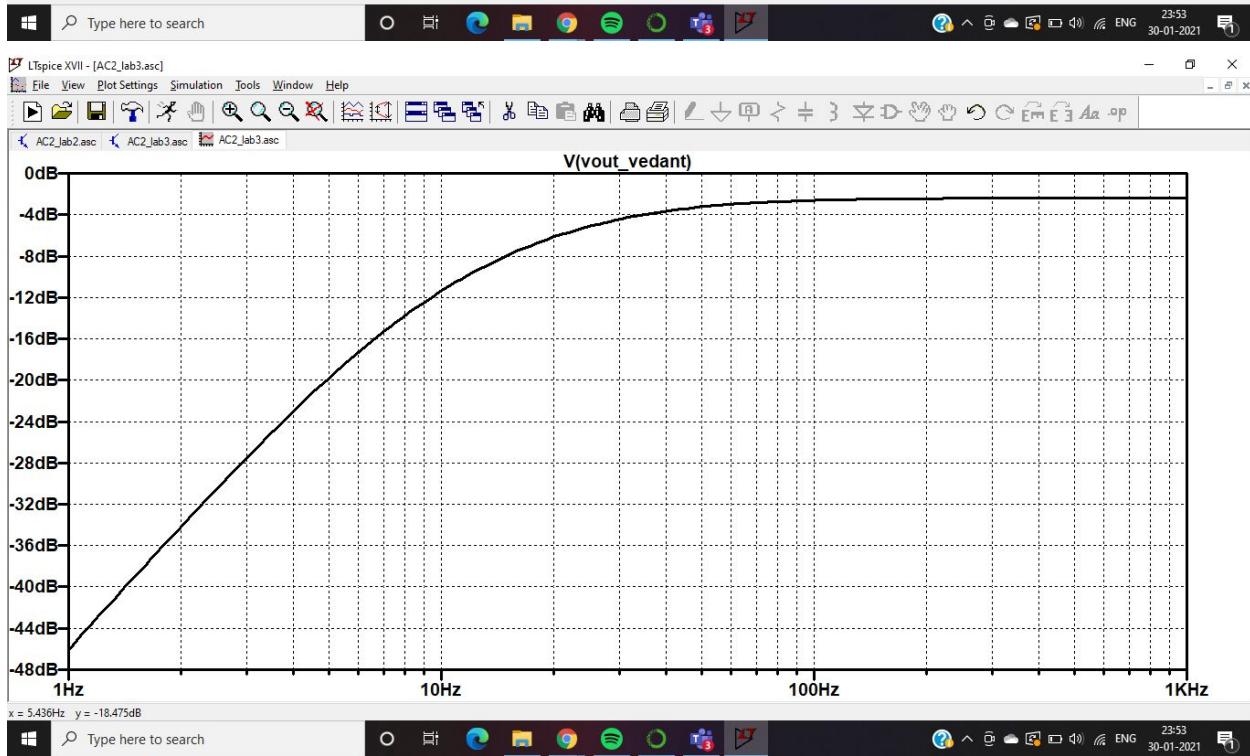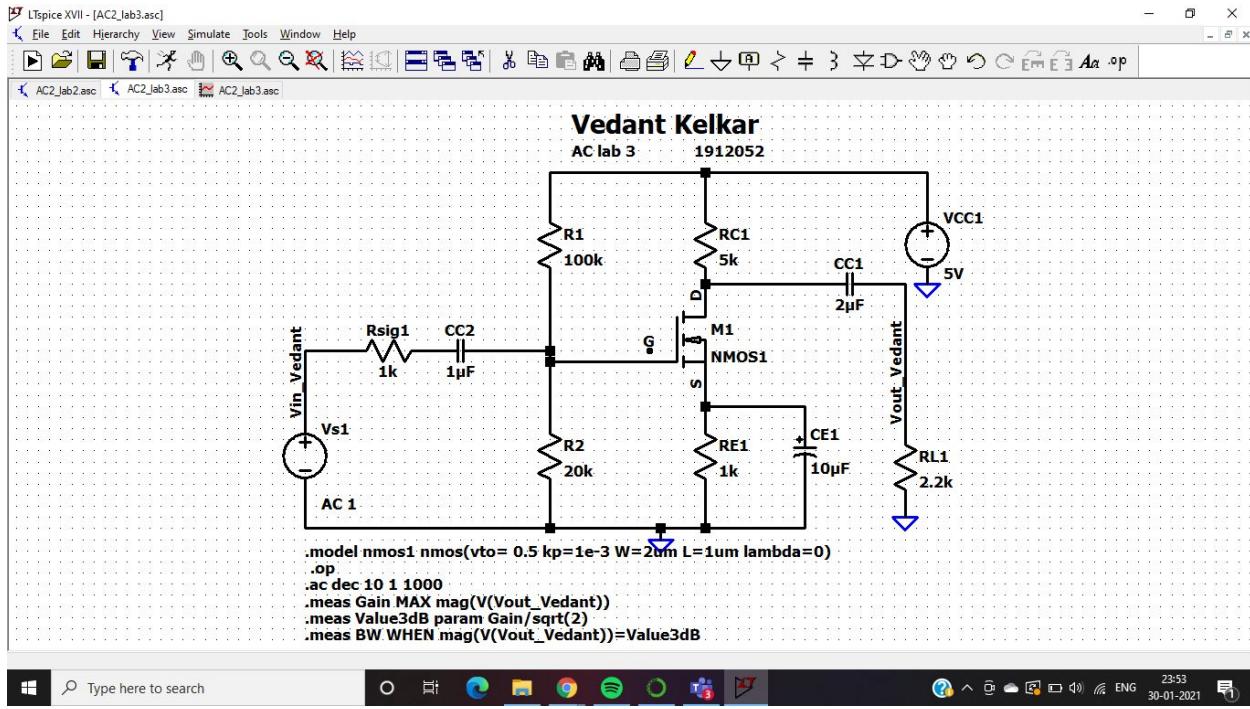

Ltspice XVII - [AC2_lab3.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab2.asc AC2_lab3.asc AC2_lab3.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.log

Circuit: * C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.asc

Instance "m1": Length shorter than recommended for a level 1 MOSFET.
 Instance "m1": Width narrower than recommended for a level 1 MOSFET.
 Direct Newton iteration for .op point succeeded.
 Semiconductor Device Operating Points:
 --- MOSFET Transistors ---

Name: m1
 Model: nmos1
 Id: 6.96e-05
 Vgs: 7.64e-01
 Vds: 4.58e+00
 Vbs: 0.00e+00
 Vth: 5.00e-01
 Vdsat: 2.64e-01
 Gm: 5.28e-04
 Gds: 0.00e+00
 Gmb: 0.00e+00
 Cbd: 0.00e+00
 Cbs: 0.00e+00
 Cgsov: 0.00e+00
 Cgdov: 0.00e+00
 Cgbov: 0.00e+00
 Cgs: 0.00e+00
 Cgd: 0.00e+00
 Cgb: 0.00e+00

.mod
 .op
 .ac dec 10 1 1000
 .meas Gain MAX mag(V(Vout_Vedant))
 .meas Value3dB param Gain/sqrt(2)
 .meas BW WHEN mag(V(Vout_Vedant))=Value3dB

Vin Vedant

+ Vs -

AC

VCC1 5V

R1 2.2k

Ready

Type here to search

23:53 30-01-2021

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.log

Cgs: 0.00e+00
 Cgd: 0.00e+00
 Cgb: 0.00e+00

gain: MAX(mag(v(vout_vedant)))=(-2.38265dB,0°) FROM 1 TO 1000
 value3db: gain/sqrt(2)=(-5.39295dB,0°)
 bw: mag(v(vout_vedant))=value3db AT 23.5548

Date: Sat Jan 30 23:53:20 2021
 Total elapsed time: 0.194 seconds.

tnom = 27
 temp = 27
 method = trap
 totitter = 5
 trainter = 0
 traptops = 0
 accept = 0
 rejected = 0
 matrix size = 9
 fillins = 0
 solver = Normal
 Matrix Compiler1: 23 opcodes
 Matrix Compiler2: 667 bytes object code size

.mod
 .op
 .ac dec 10 1 1000
 .meas Gain MAX mag(V(Vout_Vedant))
 .meas Value3dB param Gain/sqrt(2)
 .meas BW WHEN mag(V(Vout_Vedant))=Value3dB

Vin Vedant

+ Vs -

AC

VCC1 5V

R1 2.2k


Ready

Type here to search

23:53 30-01-2021

Avmid	-2.3826dB
-------	-----------

EX3

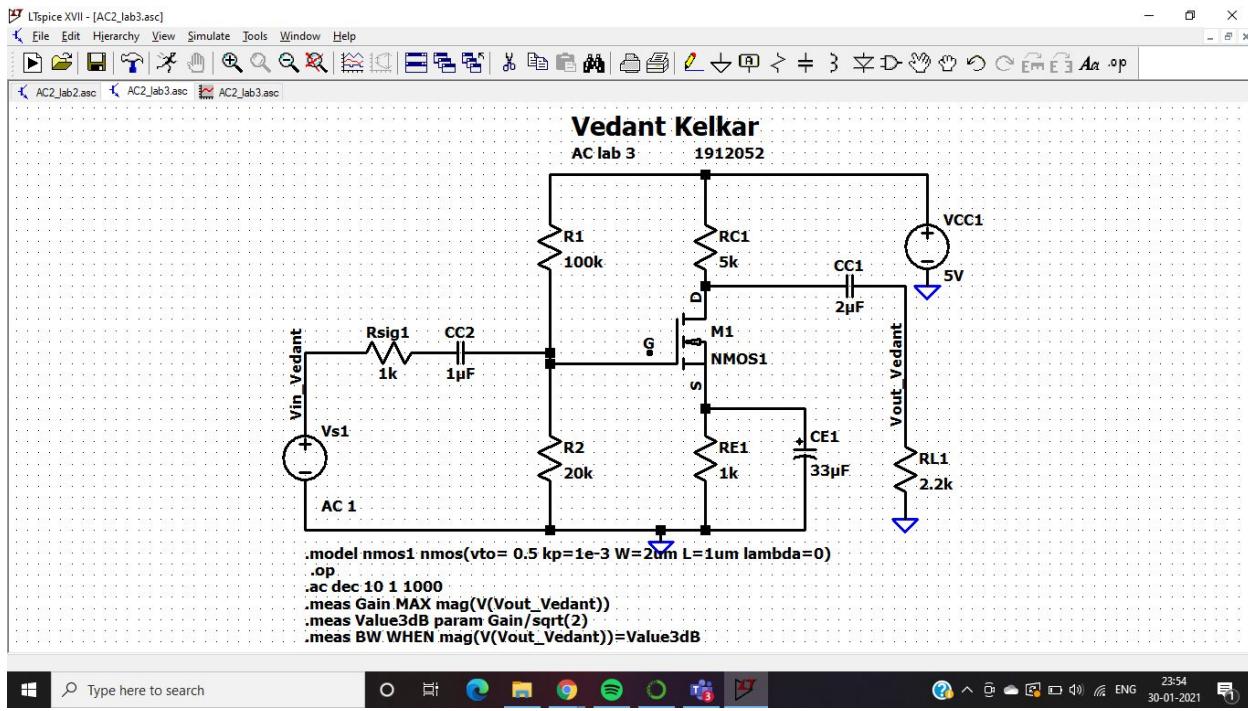

LTspice XVII - [AC2_lab3.asc]

File Edit Hierarchy View Simulate Tools Window Help

AC2_lab3.asc AC2_lab3.asc AC2_lab3.asc

SPICE Error Log: C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.log

Circuit: * C:\Users\kelka\Documents\LTspiceXVII\AC2_lab3.asc

Instance "m1": Length shorter than recommended for a level 1 MOSFET.

Instance "m1": Width narrower than recommended for a level 1 MOSFET.

Direct Newton iteration for .op point succeeded.

Semiconductor Device Operating Points:

--- MOSFET Transistors ---

Name: m1
 Model: nmos1
 Id: 6.96e-05
 Vgs: 7.64e-01
 Vds: 4.58e+00
 Vbs: 0.00e+00
 Vth: 5.00e-01
 Vdsat: 2.64e-01
 Gm: 5.28e-04
 Gds: 0.00e+00
 Gmb: 0.00e+00
 Cbd: 0.00e+00
 Cbs: 0.00e+00
 Cgsov: 0.00e+00
 Cgdov: 0.00e+00
 Cgbov: 0.00e+00
 Cgs: 0.00e+00
 Cgd: 0.00e+00
 Cgb: 0.00e+00

.model nmos1 nmos(vto= 0.5 kp=1e-3 W=2um L=1um lambda=0)

.op

.ac dec 10 1 1000

.meas Gain MAX mag(V(Vout_Vedant))


.meas Value3dB param Gain/sqrt(2)



.meas BW WHEN mag(V(Vout_Vedant))=Value3dB


Avmid

-2.381dB

EX4

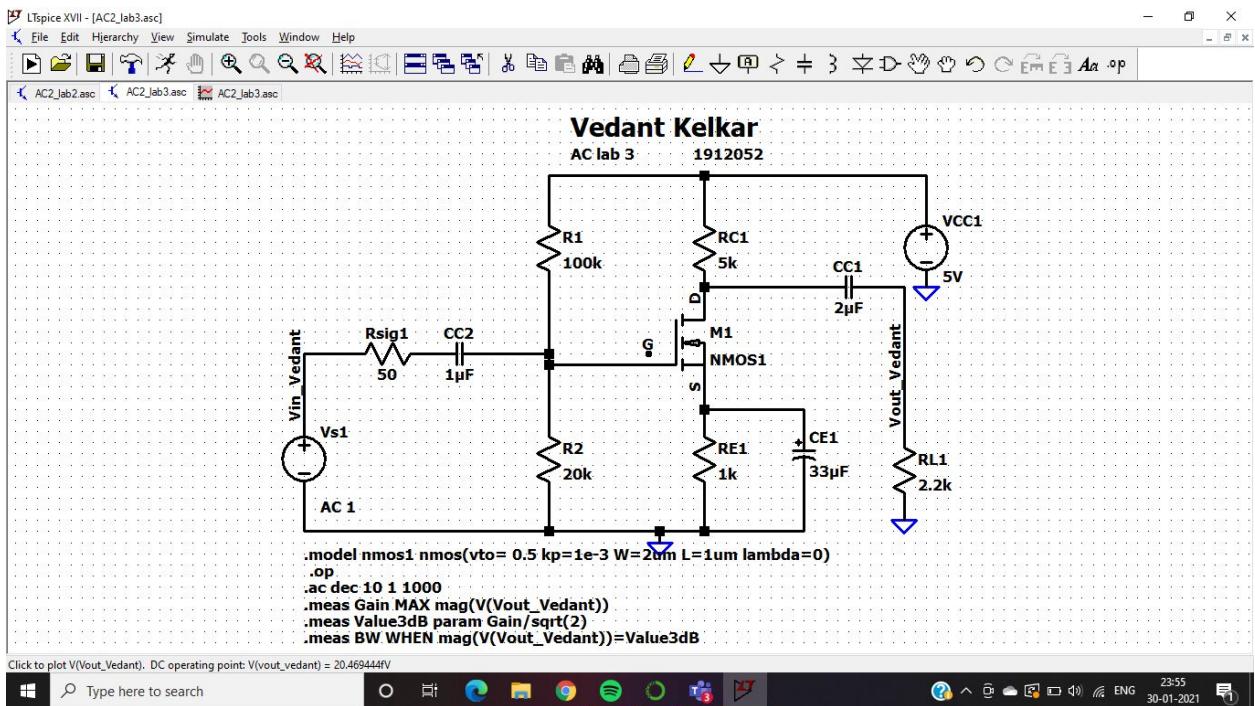

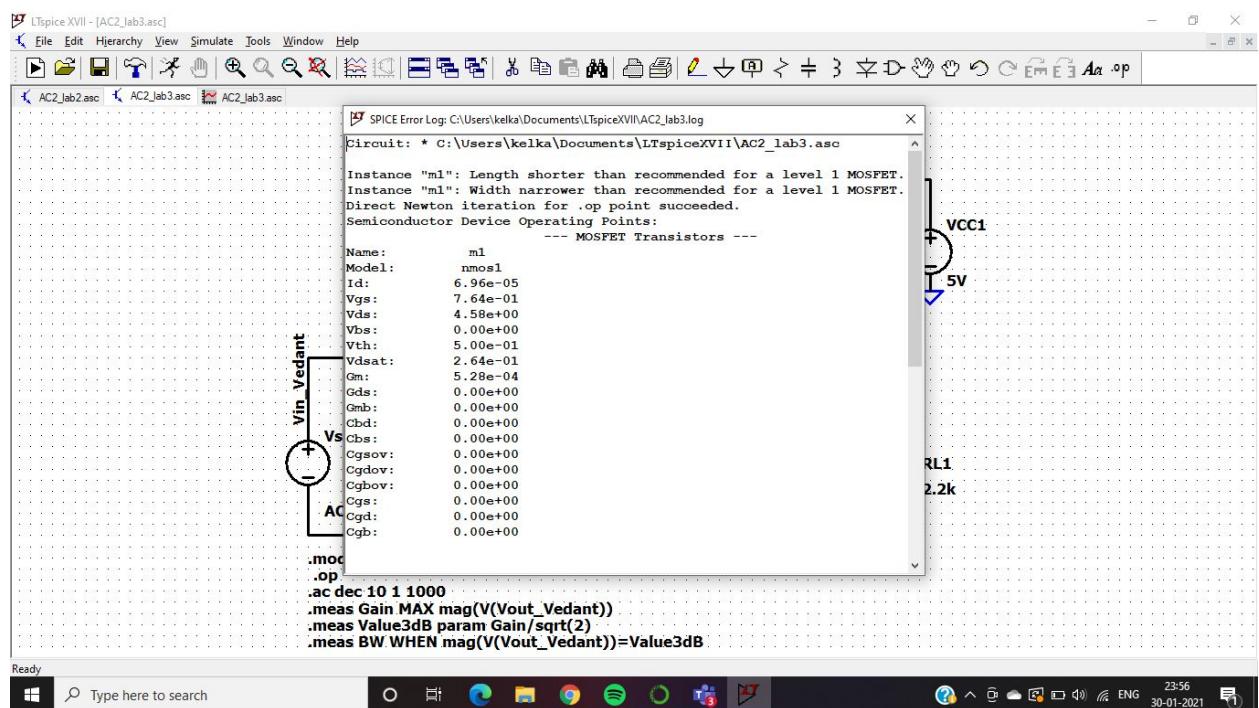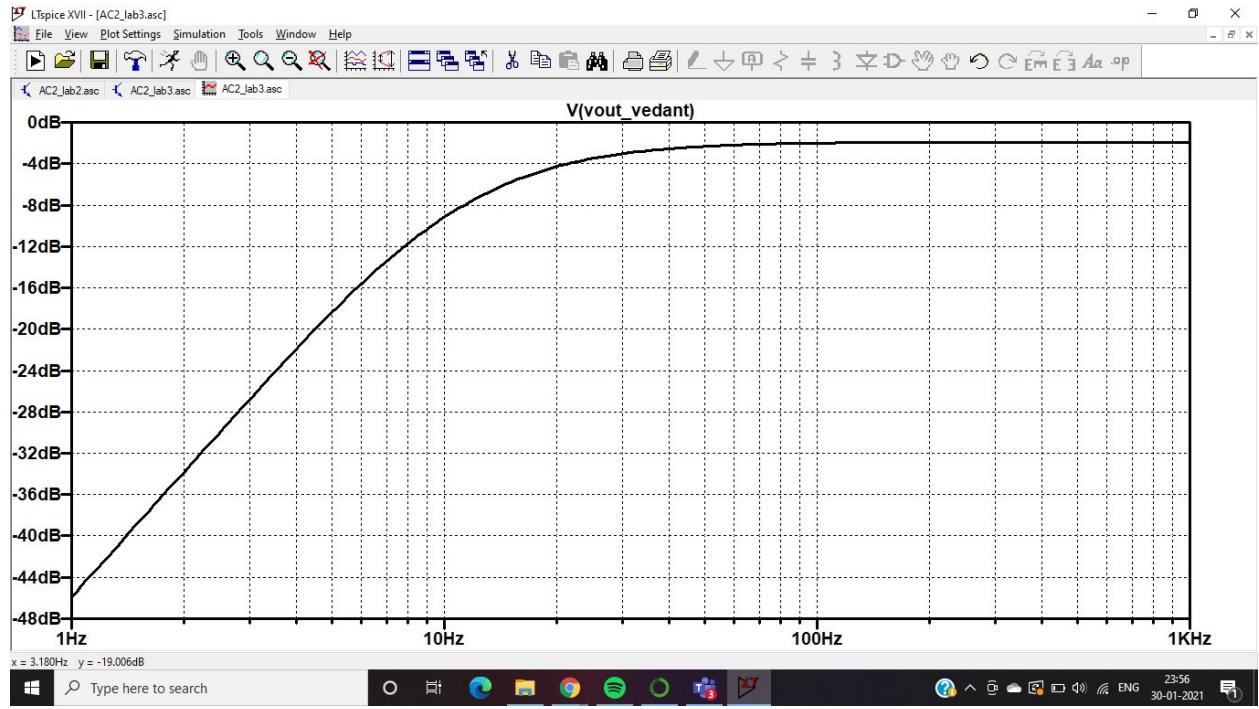

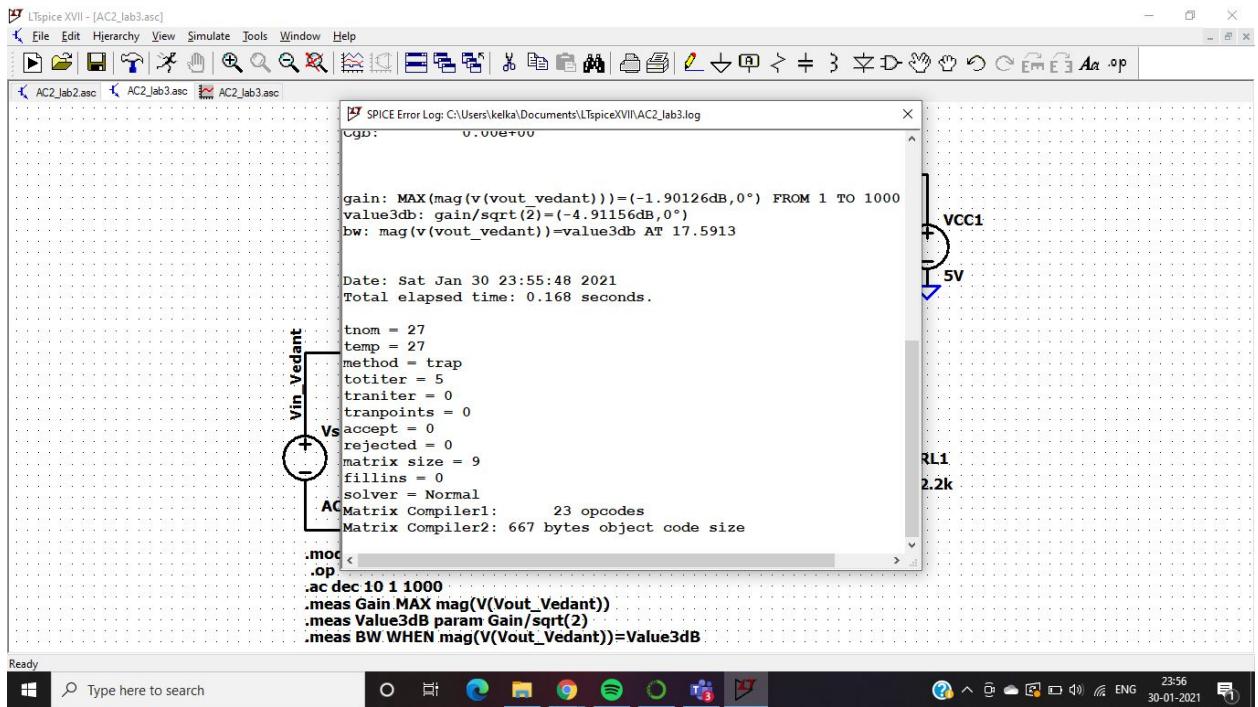

Avmid	-1.9012dB
-------	-----------

As we change the various values according to the given exercises some of the involved parameters change(increase or decrease) . We can notice the significant change in the fl fh and the bandwidth.

Suggestions: Write (few lines) what the changes in Exercise have effect on the amplifier.

AC LAB 3 is approved with suggestions: Inderjit Singh Dhanjal