

Audit Course Session 7

AUDIT COURSE ELECTRONIC CIRCUITS 2: SIMULATION BASED STUDY

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 9/2/2021

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of Session 7 is 40 MINUTES



Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.

Follow these instruction strictly:

- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of Session 7

You are entitled for 10 points per session only if you follow above instruction to the details


STUDENTS WORK AREA STARTS HERE

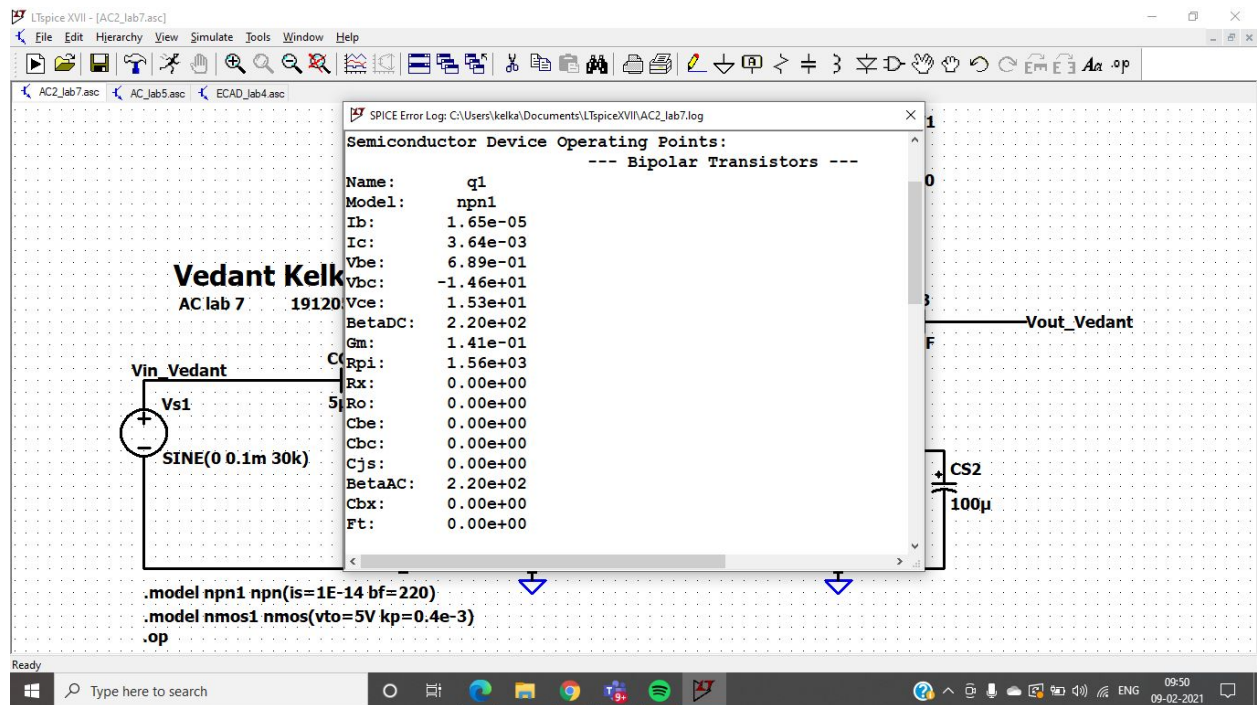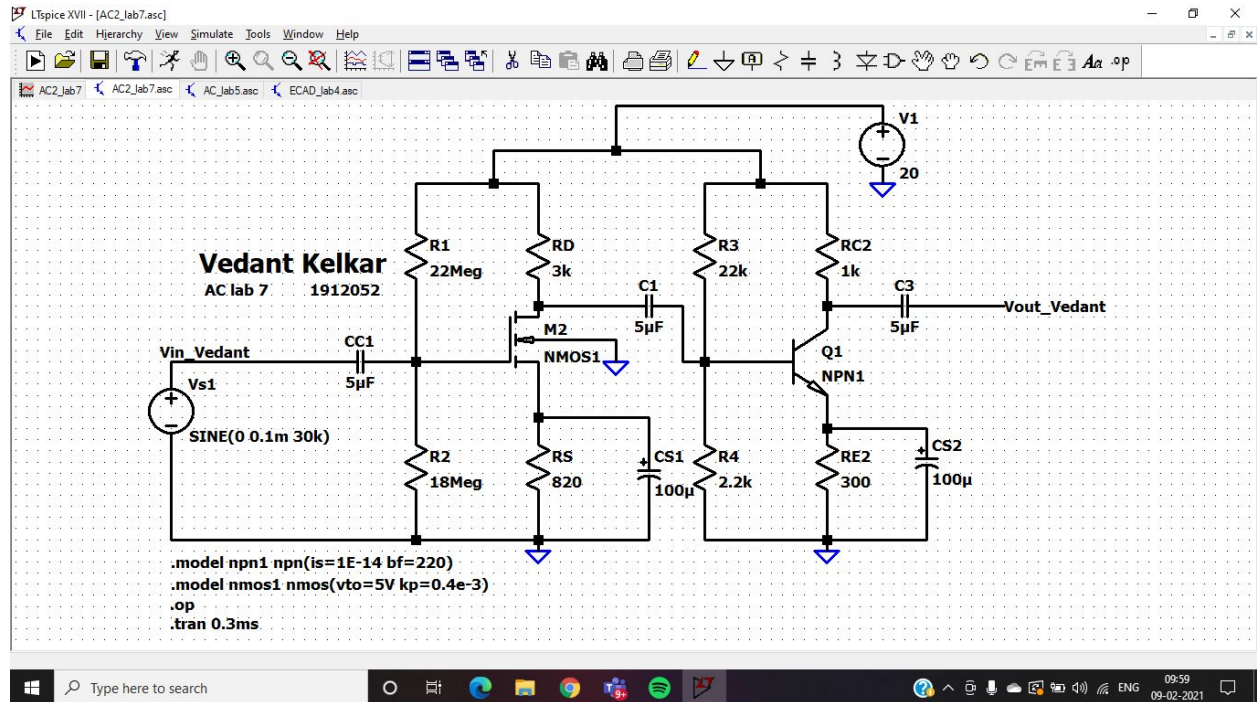

Ib: 1.65e-05
Ic: 3.64e-03
Vbe: 6.89e-01
Vbc: -1.46e+01
Vce: 1.53e+01
BetaDC: 2.20e+02
Gm: 1.41e-01

Rpi: 1.56e+03
Rx: 0.00e+00
Ro: 0.00e+00
Cbe: 0.00e+00
Cbc: 0.00e+00
Cjs: 0.00e+00
BetaAC: 2.20e+02
Cbx: 0.00e+00
Ft: 0.00e+00


Ib	1.65e-05
Ic	3.64e-03
Vbe	6.89e-01
Vbc	-1.46e+01
Vce	1.53e+01
BetaDC	2.20e+02
Gm	1.41e-01
Rpi	1.56e+03
BetaAC	2.20e+02


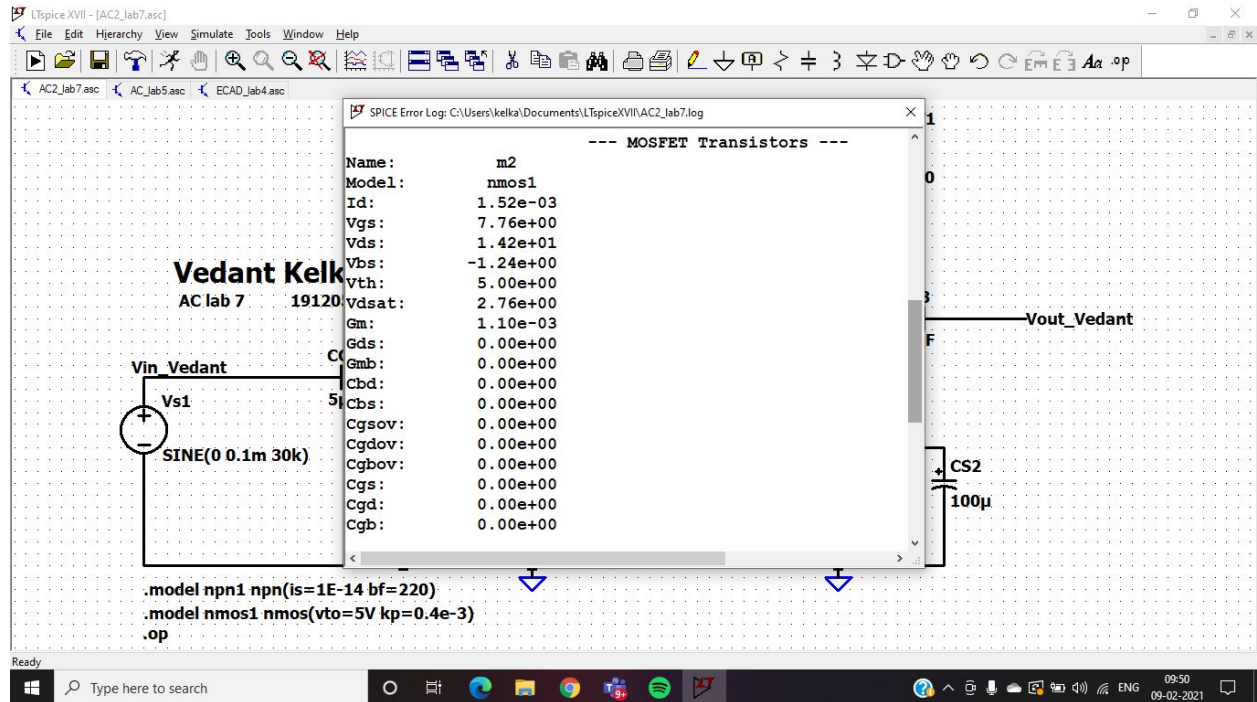


Id: 1.52e-03
Vgs: 7.76e+00
Vds: 1.42e+01
Vbs: -1.24e+00
Vth: 5.00e+00
Vdsat: 2.76e+00
Gm: 1.10e-03
Gds: 0.00e+00
Gmb: 0.00e+00
Cbd: 0.00e+00
Cbs: 0.00e+00
Cgsov: 0.00e+00
Cgdov: 0.00e+00
Cgbov: 0.00e+00
Cgs: 0.00e+00
Cgd: 0.00e+00
Cgb: 0.00e+00

Id	1.52e-03
Vgs	7.76e+00
Vds	1.42e+01

Vth	5.00e+00
Vdsat	2.76e+00
Gm	1.10e-03
Vbs	-1.24e+00


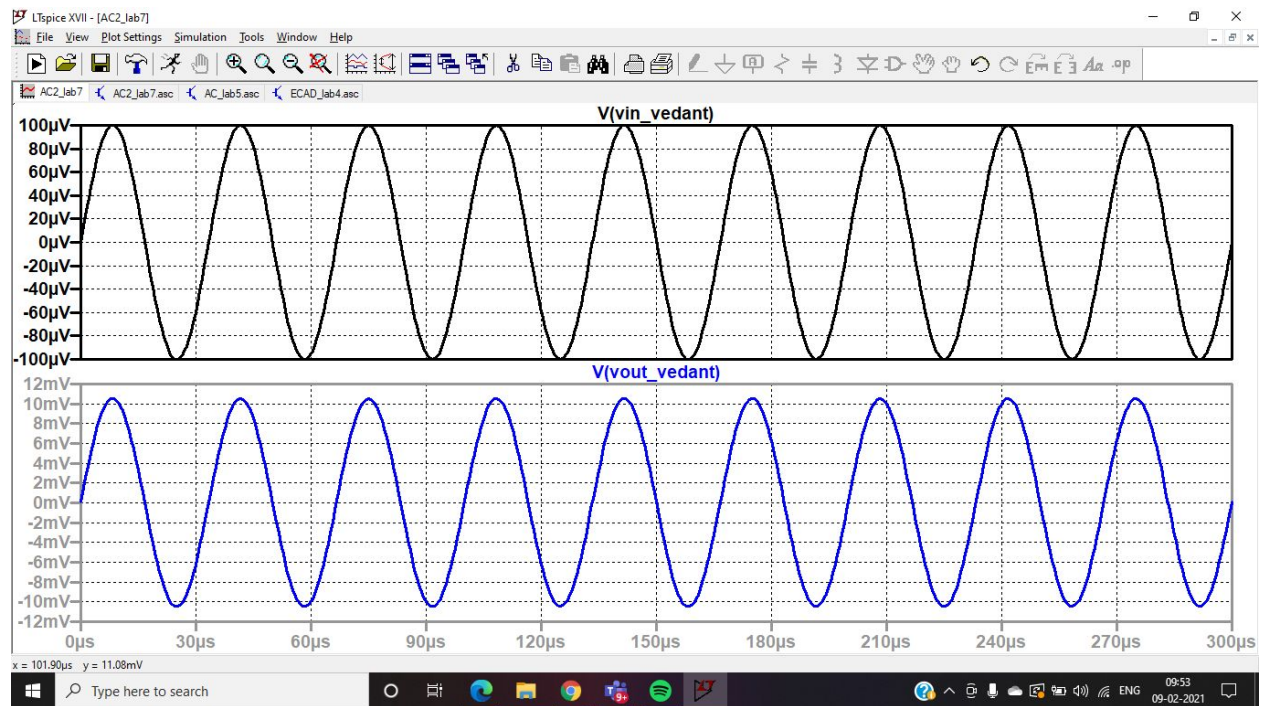


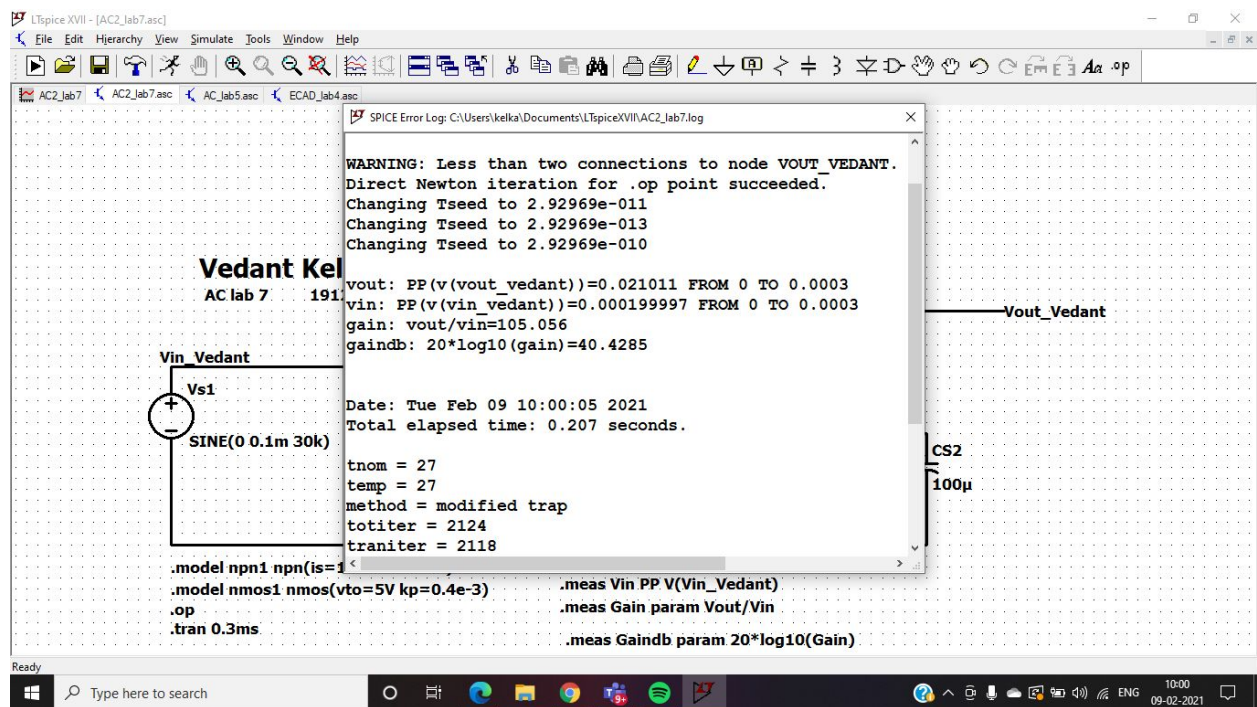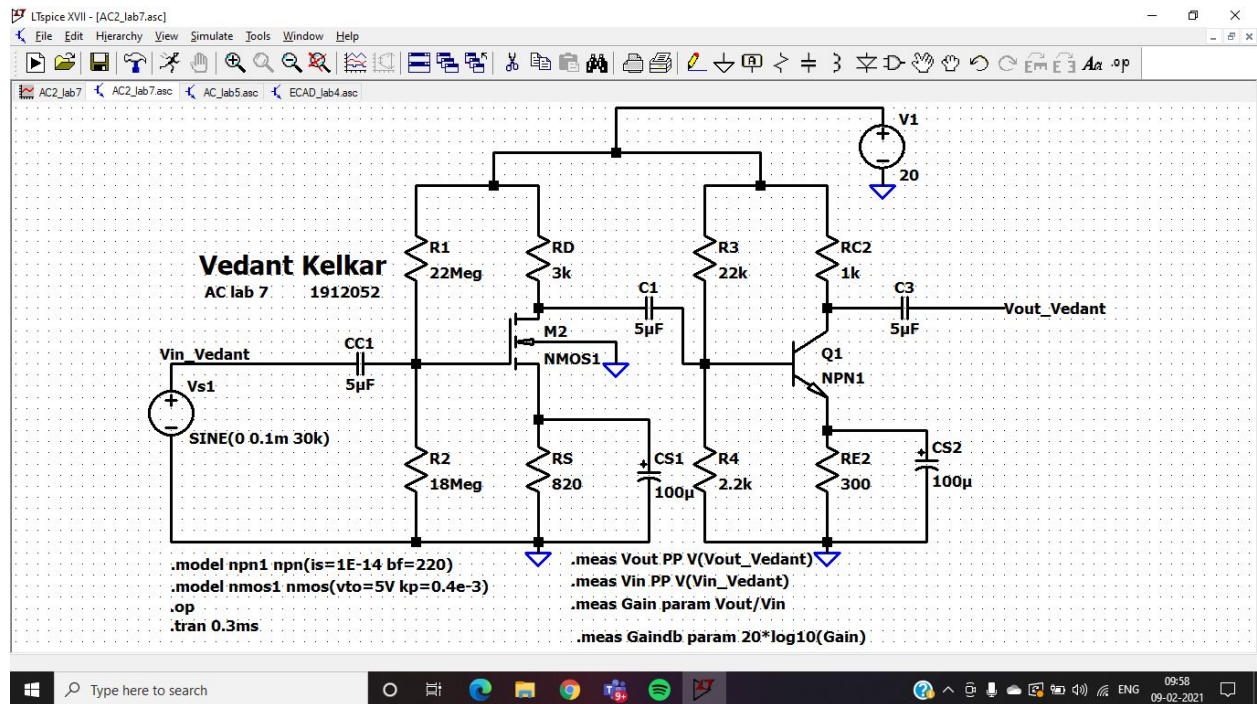

vout: PP(v(vout_vedant))=0.021011 FROM 0 TO 0.0003
vin: PP(v(vin_vedant))=0.000199997 FROM 0 TO 0.0003
gain: vout/vin=105.056
gaindb: 20*log10(gain)=40.4285



Gain	105.056
------	---------

Zin

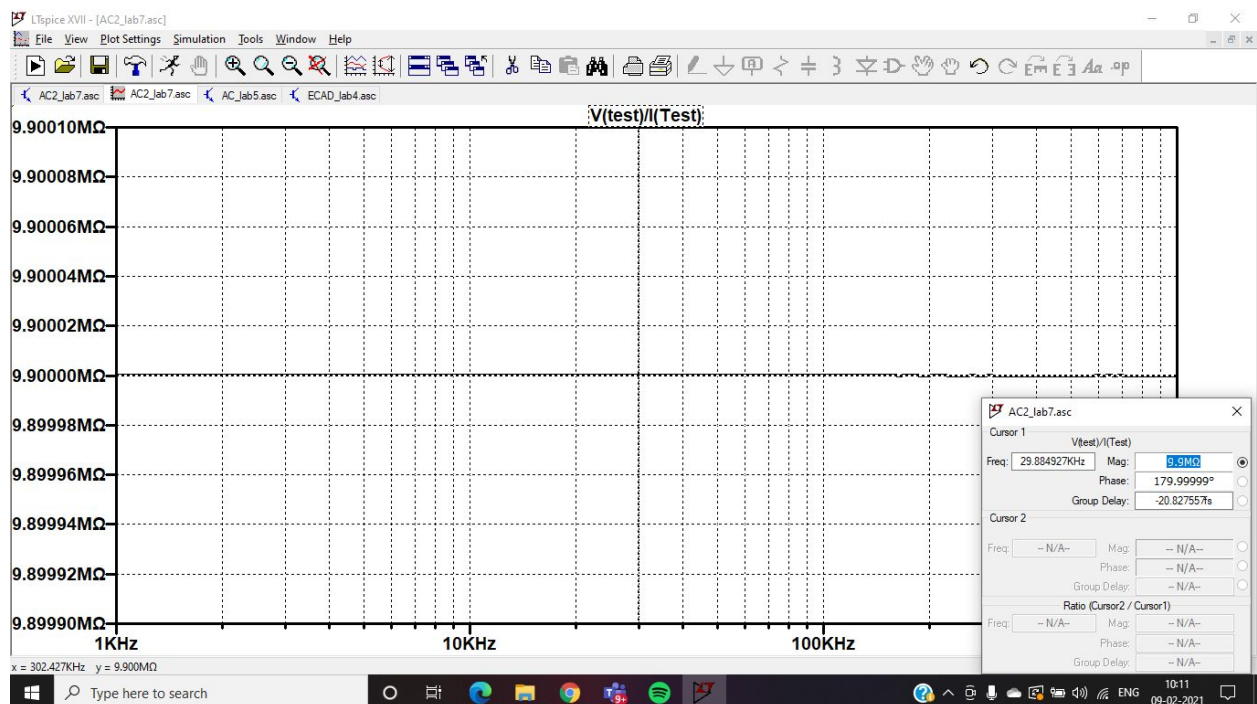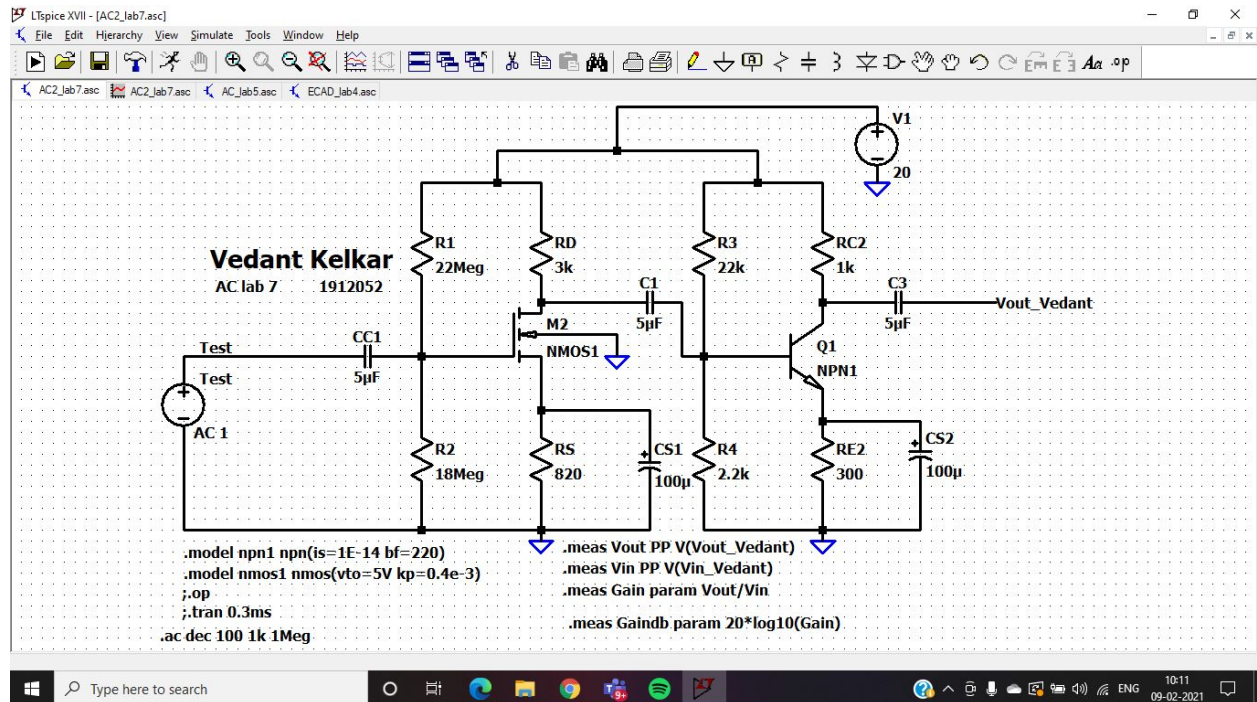

9.9MΩ

Zout

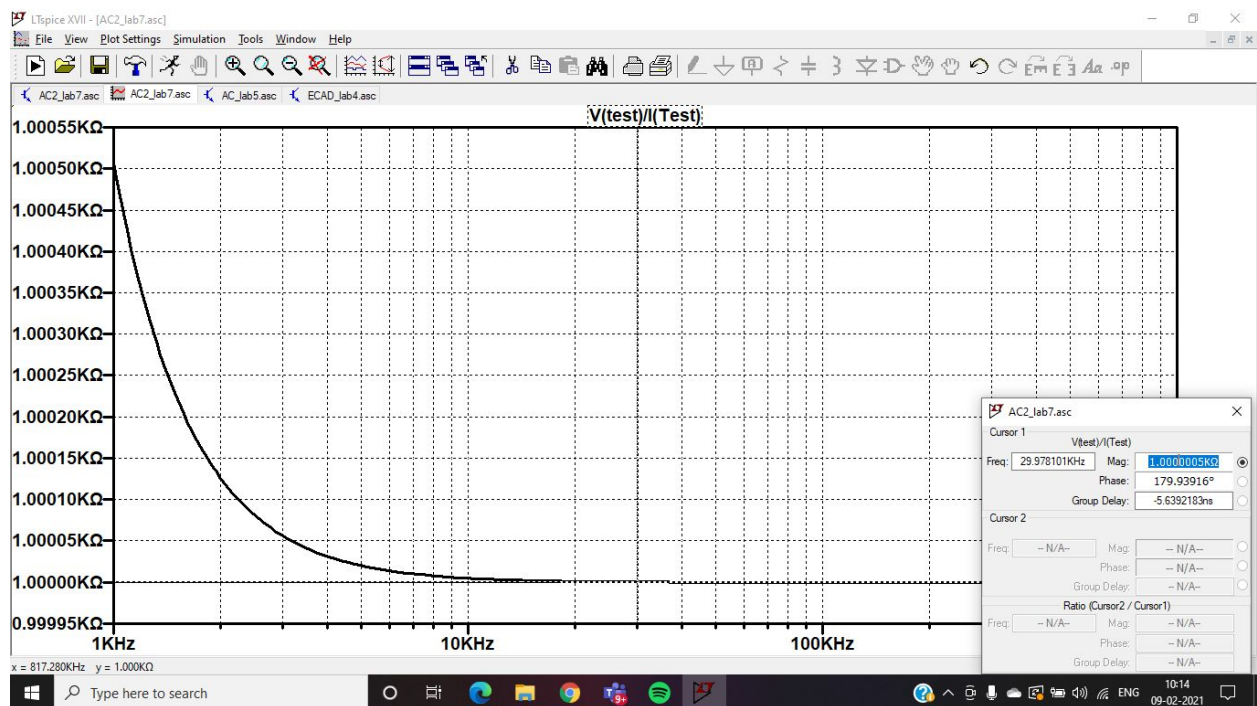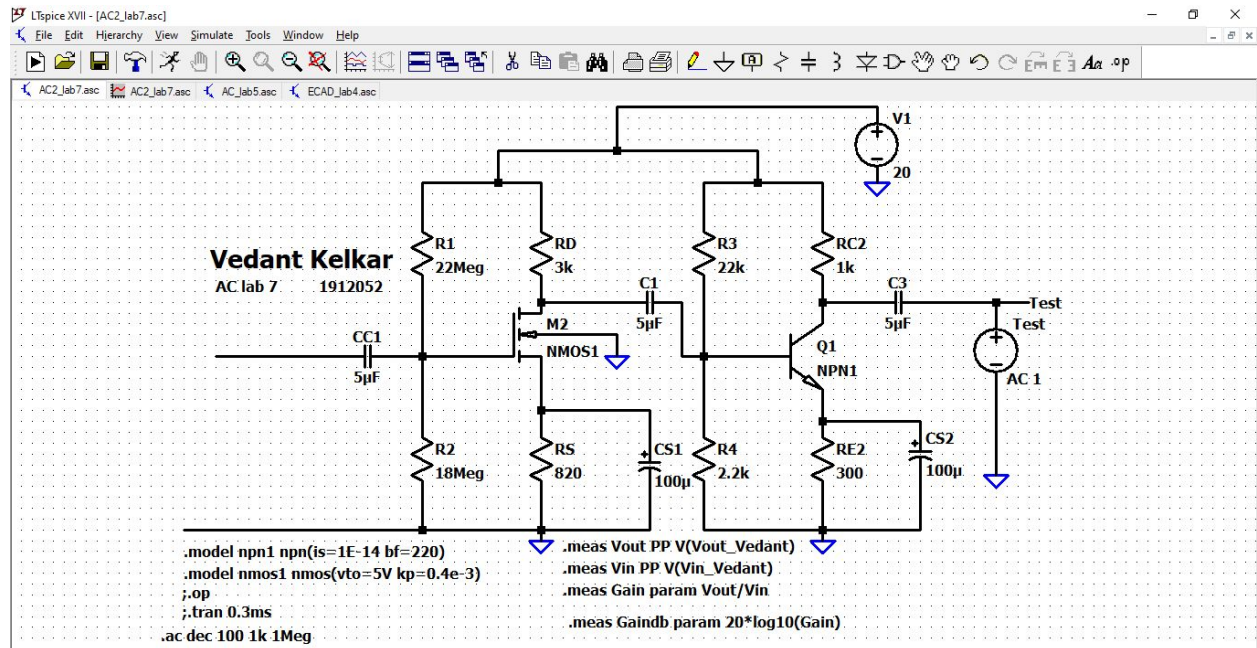

1.0000005KOhm



Zin	Zout
-----	------

9.9M Ω

1.0000005K Ω



EX1 RD=1.8k

Zin

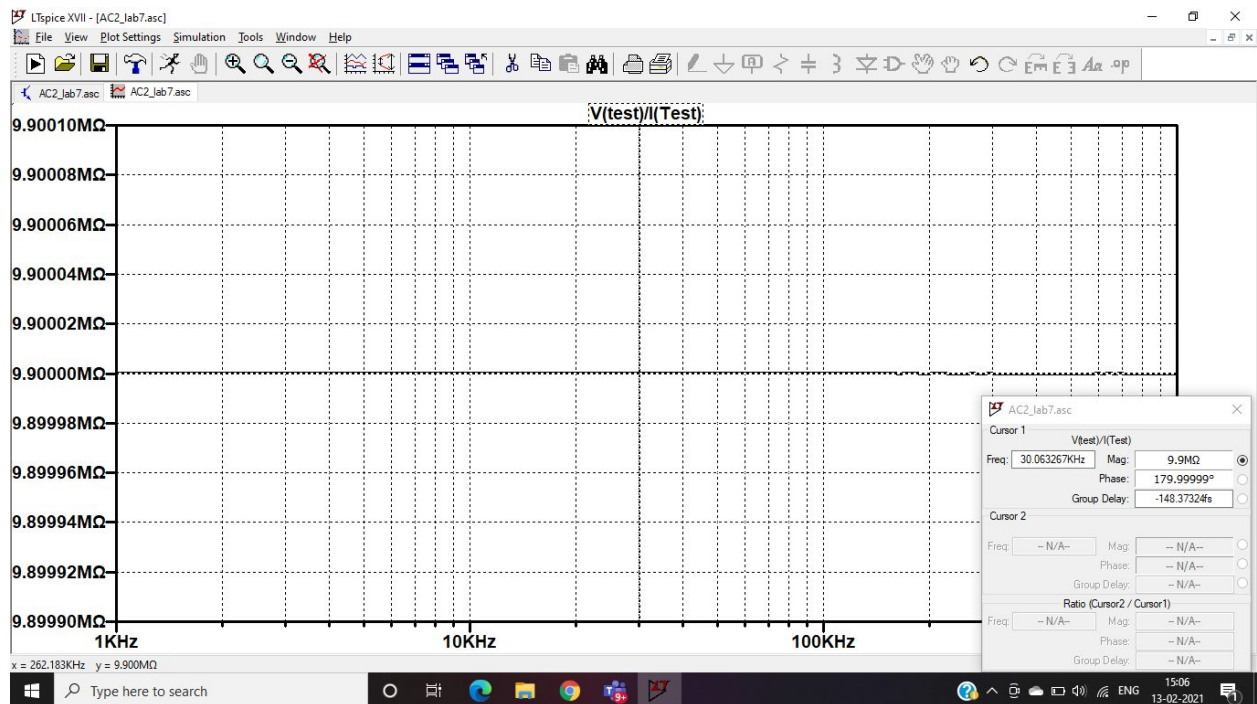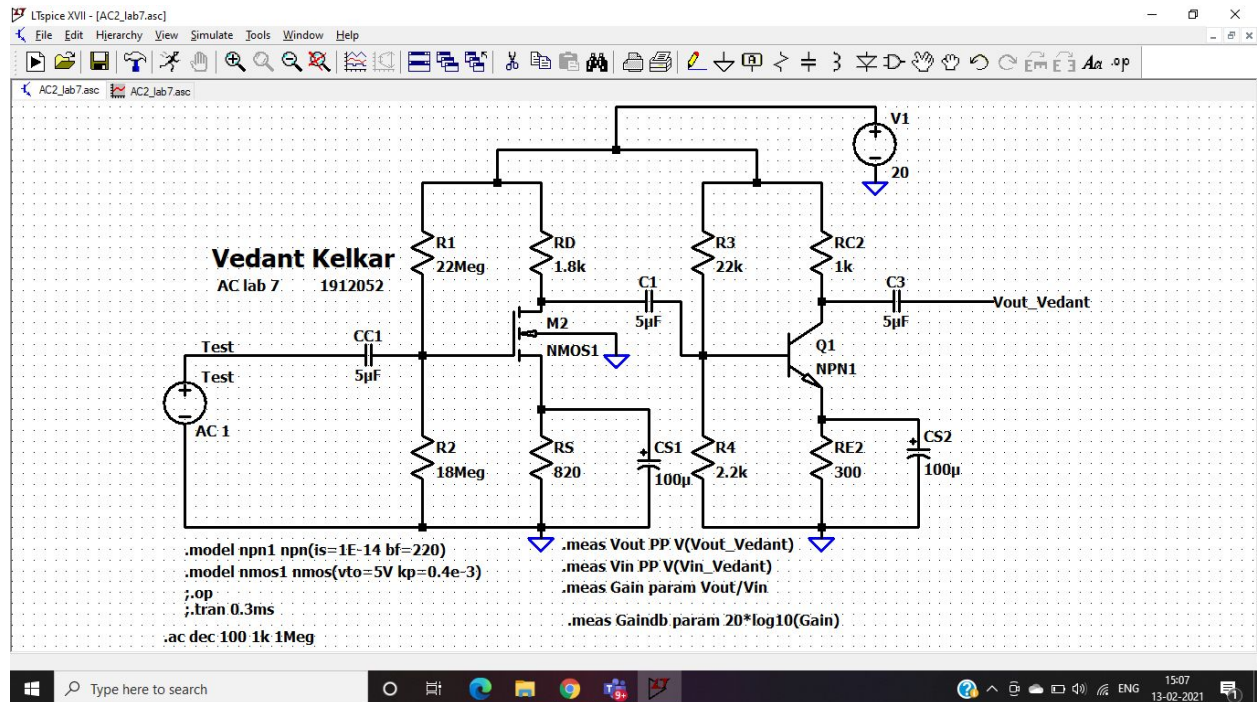

9.9M Ω m

Zout

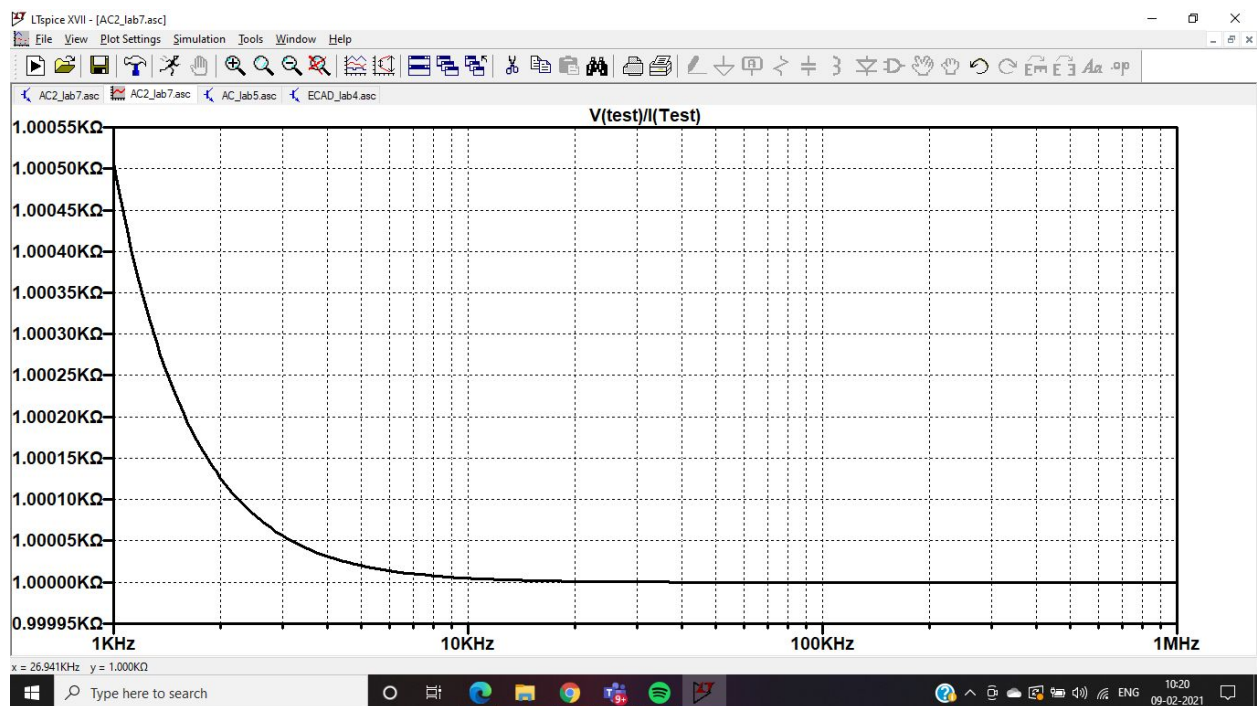
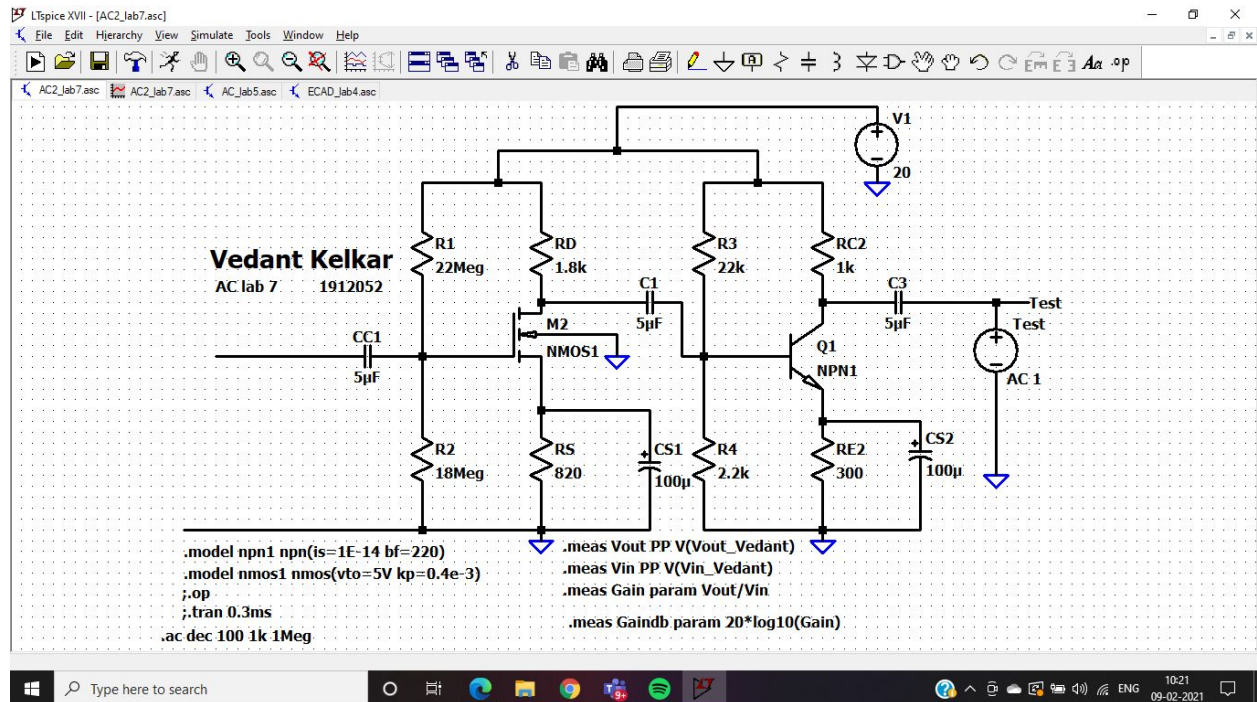


1.0000005K Ω m

Zin	Zout
9.9MOhm	1.0000005KOhm



EX2 RC=1.8k

Zin

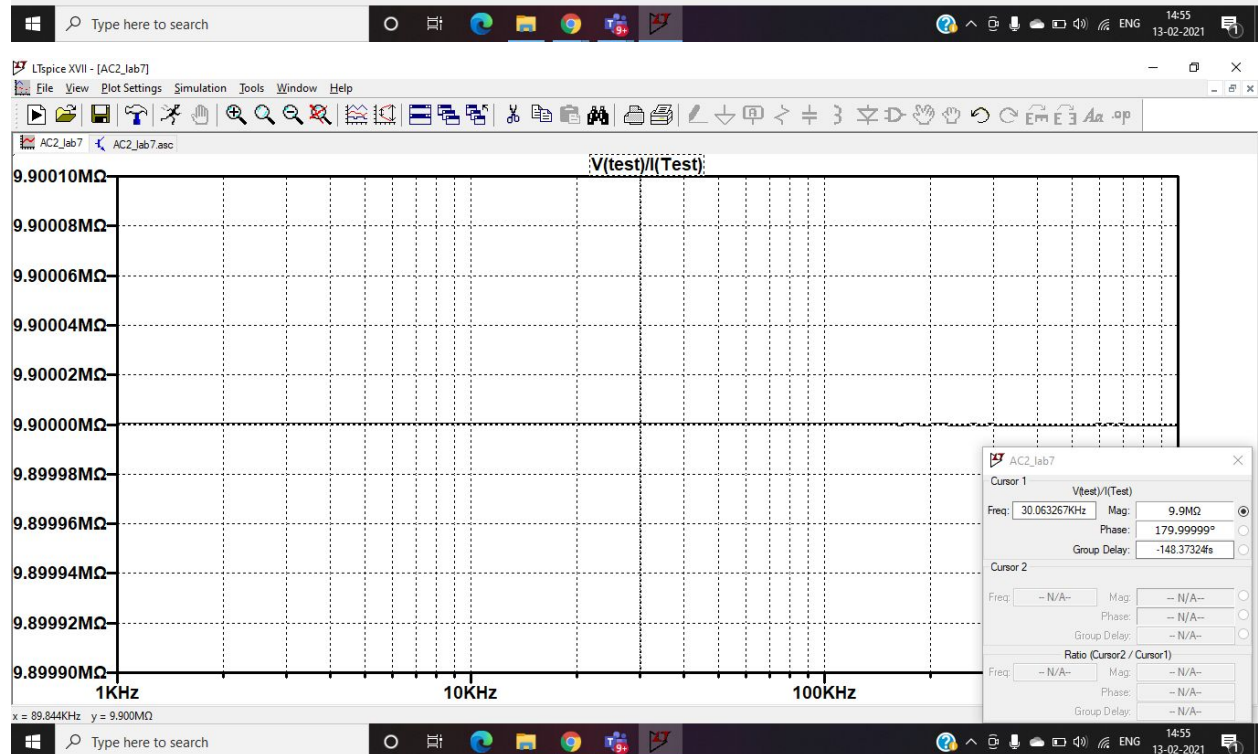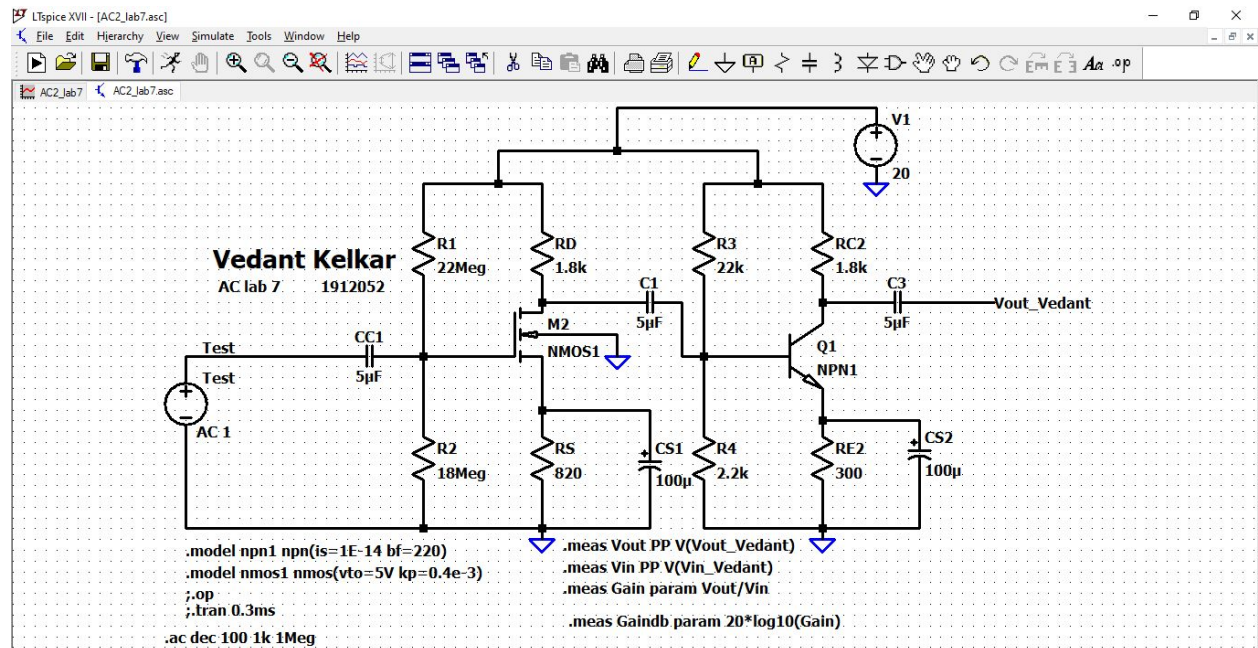

9.9M Ω m

Zout

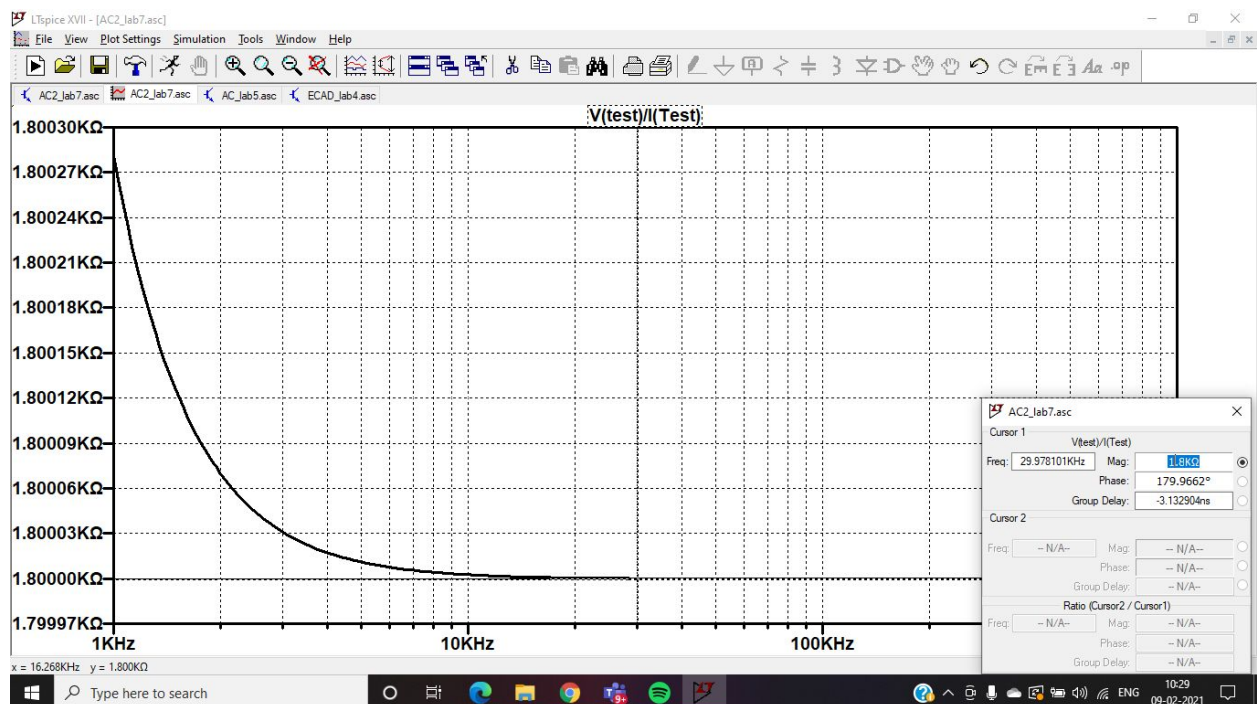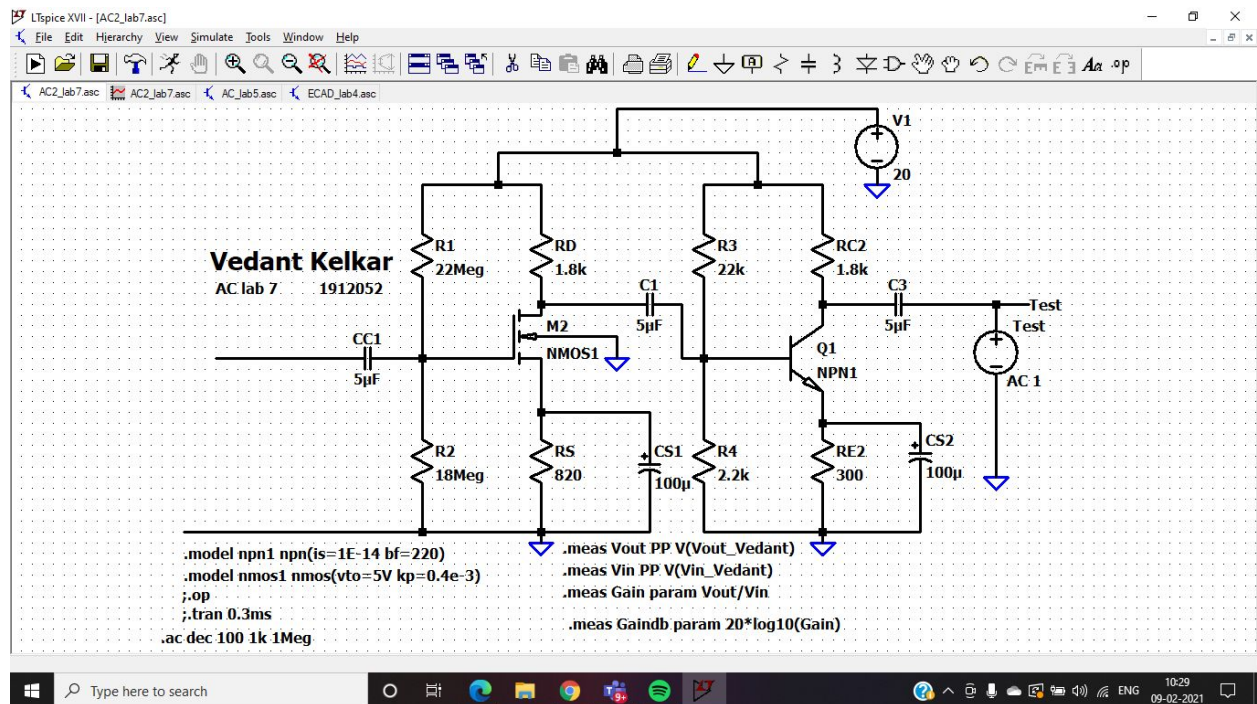

1.8K Ω m

Zin	Zout
-----	------

9.9MΩ	1.8KΩ
-------	-------

Suggestions: add inferences from exercise

AC LAB 7 is approved with suggestions: Inderjit Singh Dhanjal