

AUDIT COURSE
ELECTRONIC CIRCUITS 1: SIMULATION BASED STUDY

LAB 7

Kindly update your name and roll no, once this document is shared with you

Time slot to complete your work is **40 MINUTES**

Date: 24/8/2020

Kindly upload your schematic & waveform images here, every 10 minutes, indicating your progress and intention to completion of WORK within time slot allotted

Time slot allotted to you all for the completion of WEEK 4 DAY 1 is 40 MINUTES



Kindly upload your work (only circuit schematic & waveform in LTSpice) in the shared google doc between this time slot only.



Follow these instruction strictly:

- 1, Start sharp ON TIME, by posting your name and roll no and **screenshot of your LT spice work screen (time and date MUST BE VISIBLE)**
2. Upload your work every 10 minutes, i.e LT spice work screen
3. This means you will upload LT spice work screen 4 times during this time slot.
4. Point 3 indicates your readiness and presences for completion of WEEK 4 DAY 1



You are entitled for 1 CREDIT per Lab only if you follow above instruction to the details


STUDENTS WORK AREA STARTS HERE

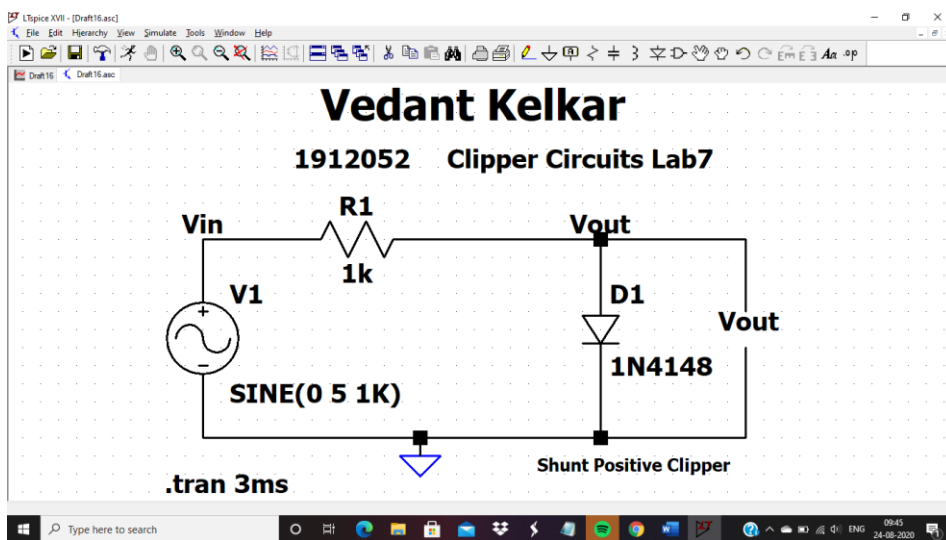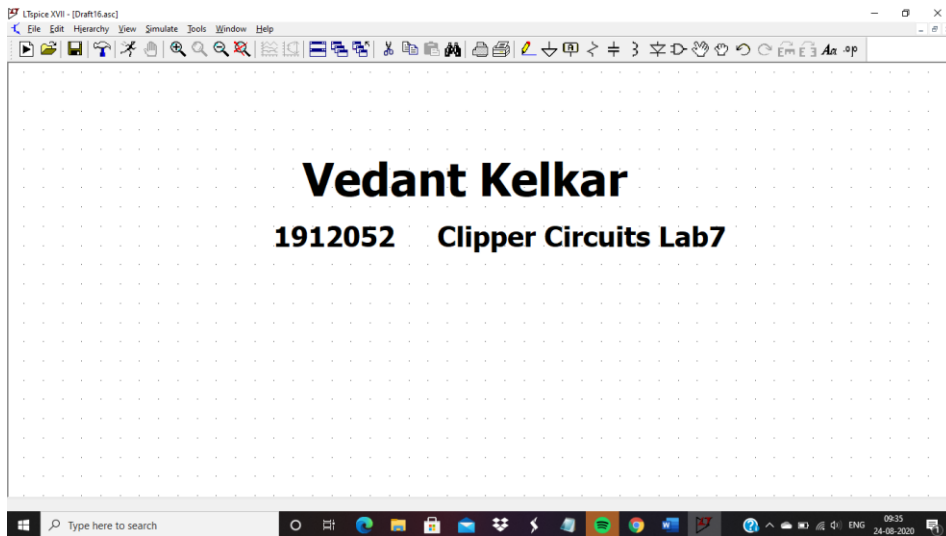

  




Parametric Sweep for R1

 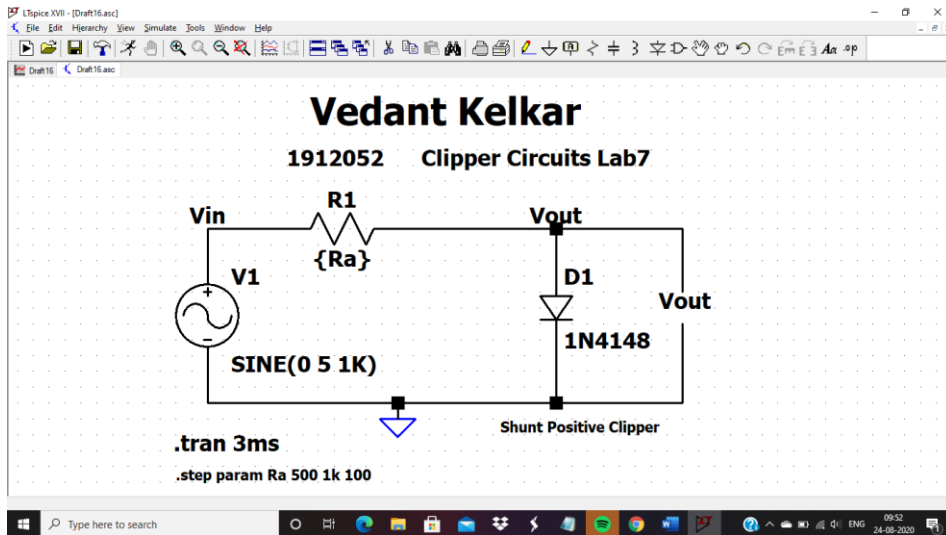


 



CIRCUIT 2

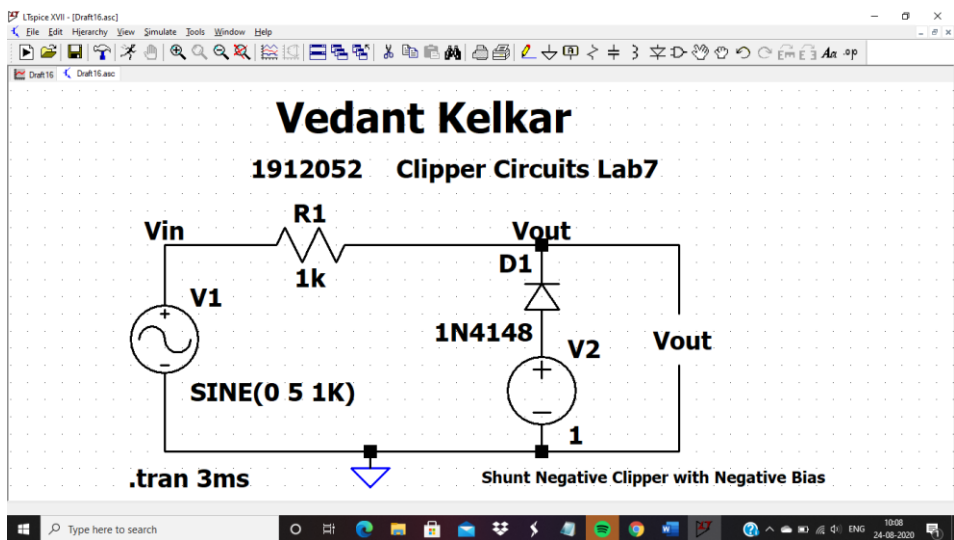

  




PARAMETRIC SWEEP FOR R1

 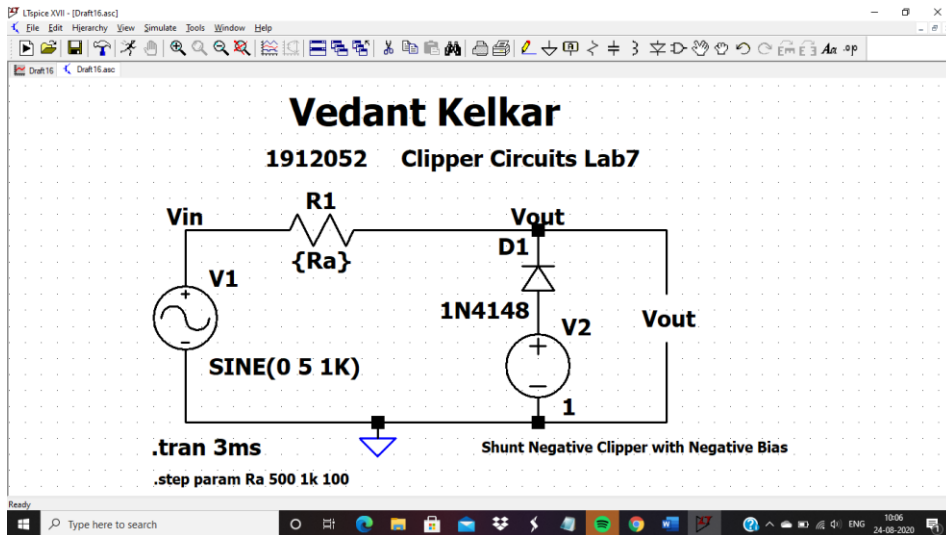


 



CIRCUIT 3

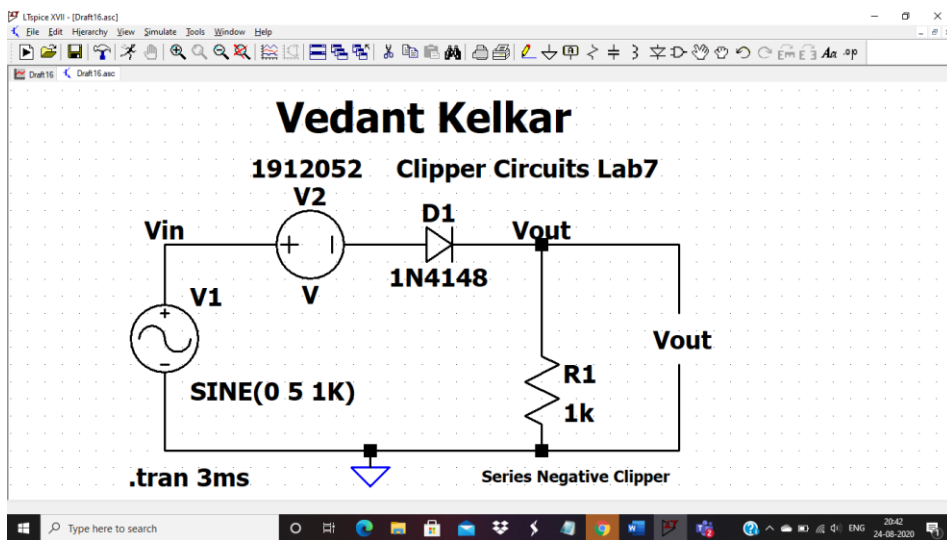

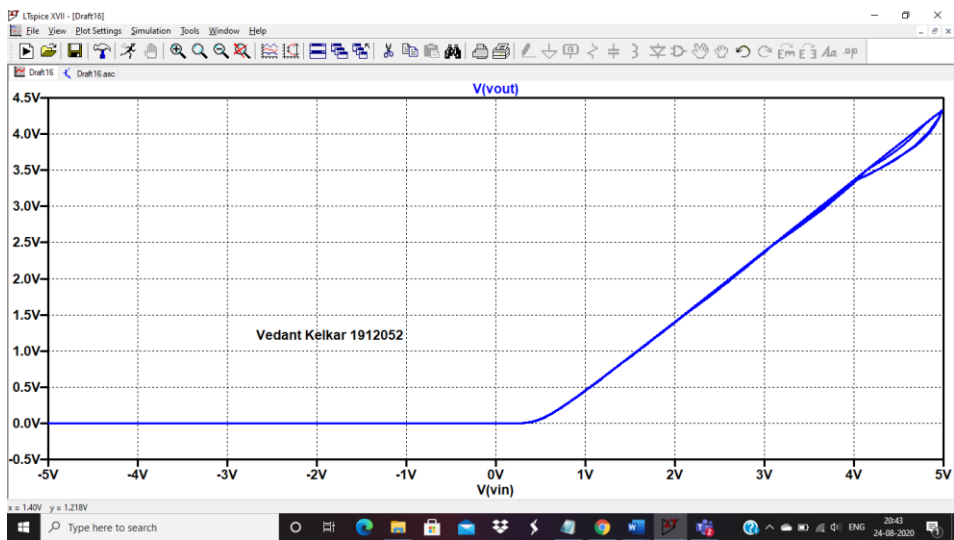 




PARAMETRIC SWEEP FOR R1

 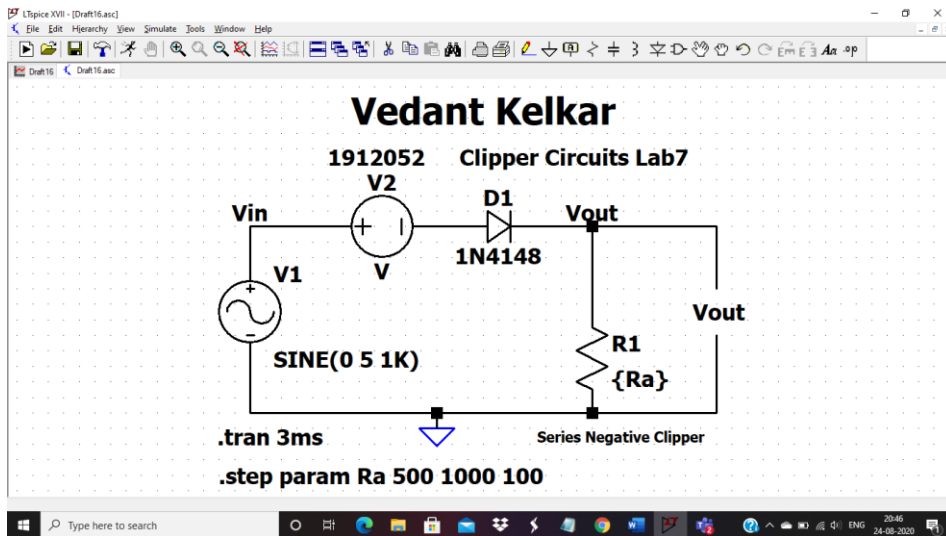


 



CIRCUIT 4

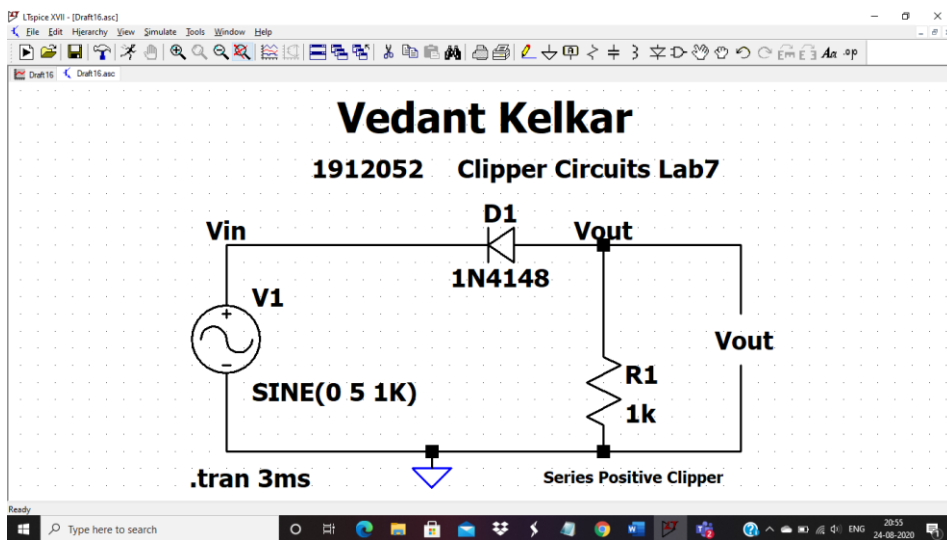

  

PARAMETRIC SWEEP FOR R1

 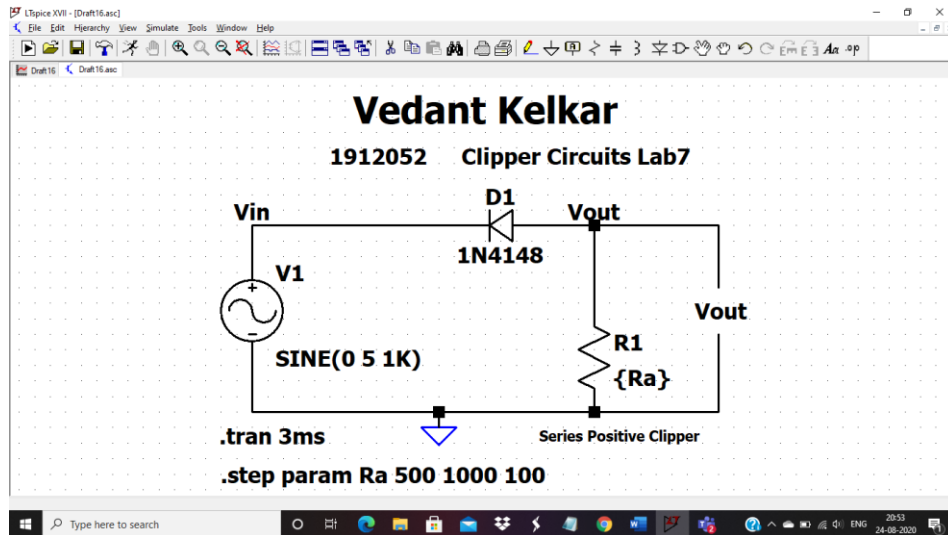

 

AC LAB 7 is approved: Inderjit Singh Dhanjal

Commented [1]: AC LAB 7 is approved